


Stepper Motors

- DC motors with permanent magnets and multiple coils around the body.
- Coils are turned on and off in sequence to cause the motor to turn.
- Because the coils are turned on and off they are easy to control with microcomputer and digital circuits. At any given time, the position of the shaft is known.
- Holding torque requires power.

Servos


- Servos are motors with electronic circuitry that controls the angular position of the shaft based on a control signal. If the angle is incorrect the motor is turned on until the correct position is reached.
- Angular position controlled by a 0 – 2.0 ms pulse width.

Schematic Drawing Convention

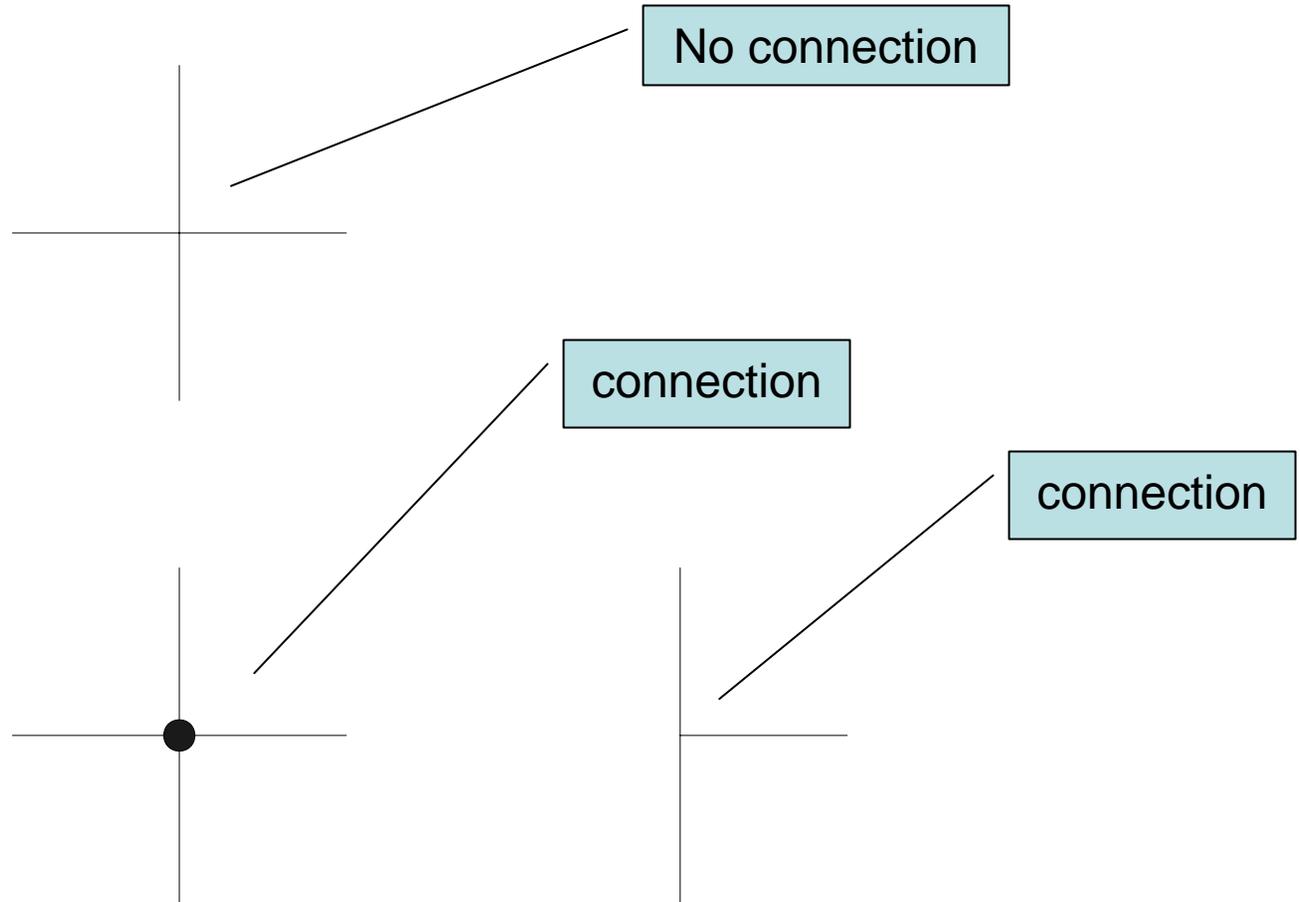


Lab Exercise - Review

Ramp Generator

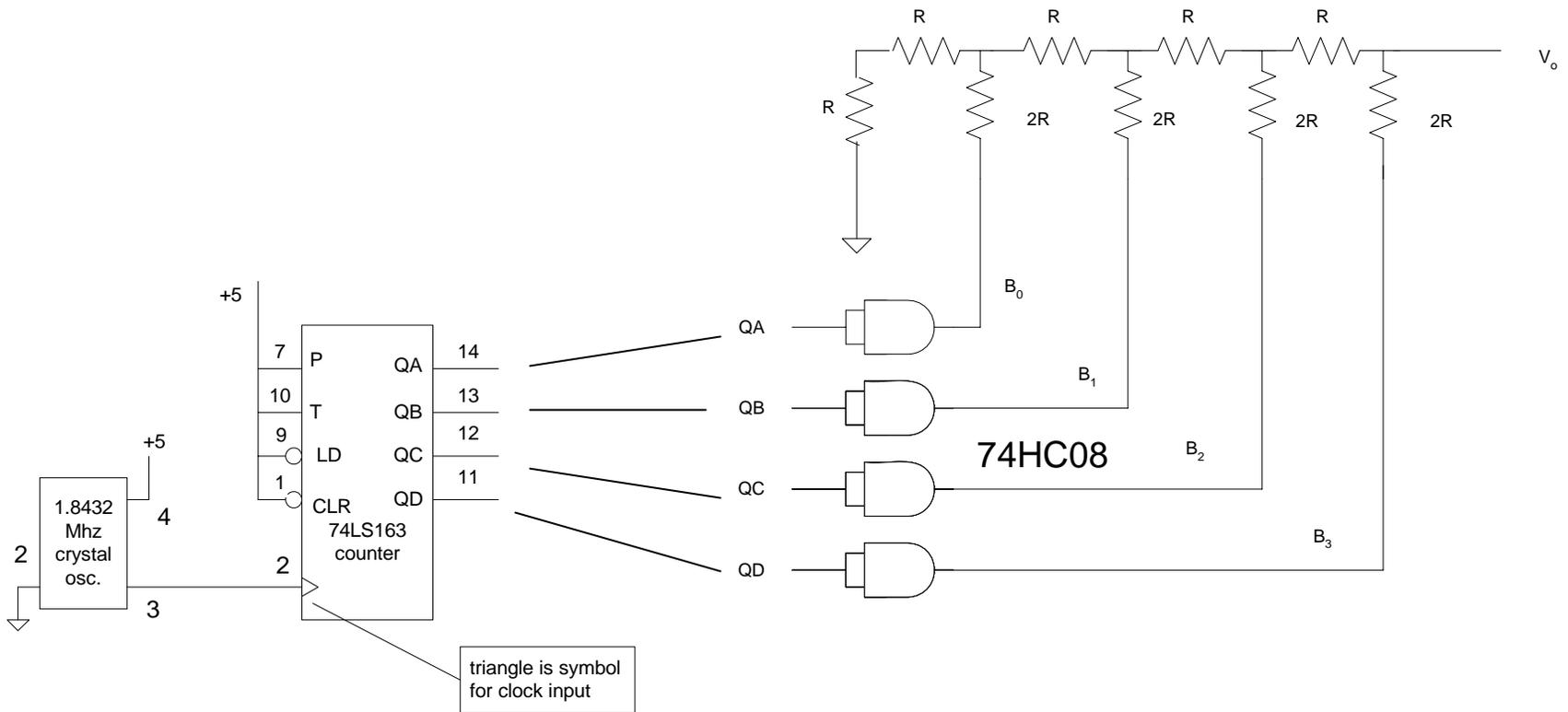

RAMP Generator Output

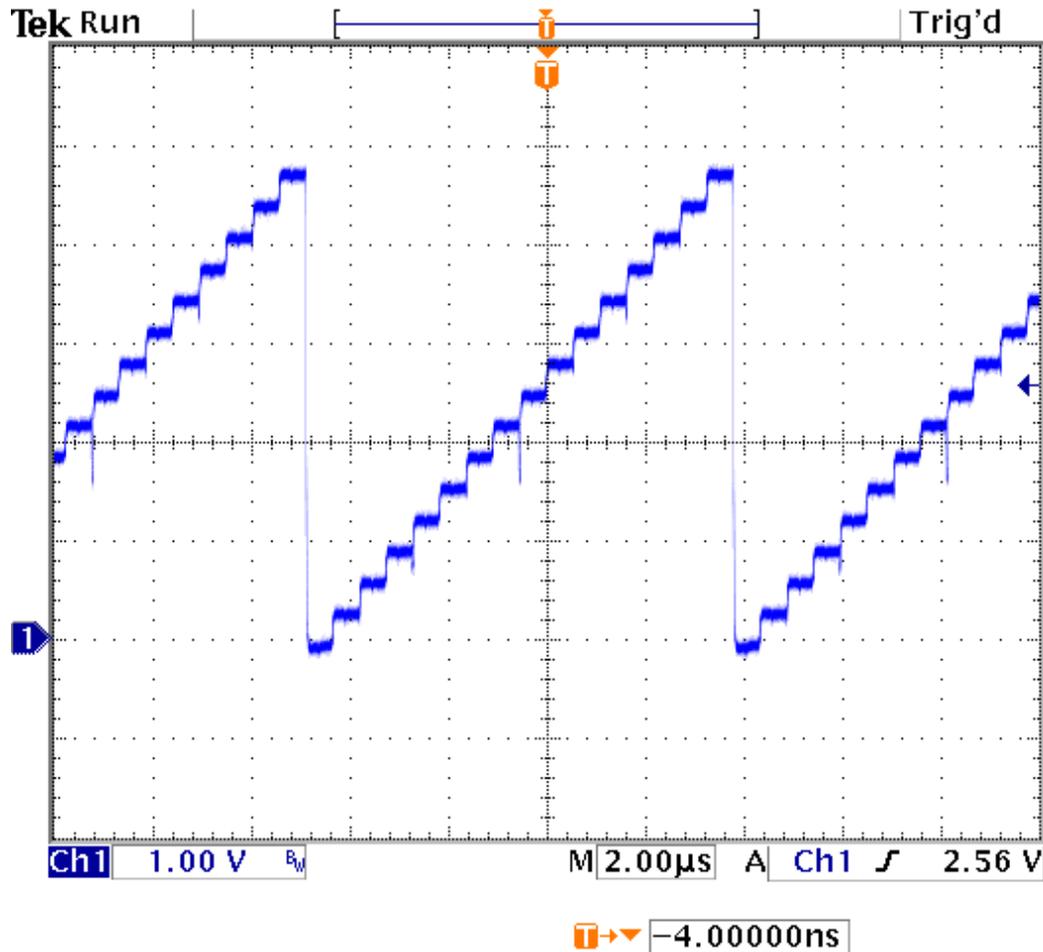

24 Jan 2007
16:09:07


DA Summary

- Output from digital to analog conversion are discrete levels.
- More bits means better resolution.
- An example of DA conversion
 - Current audio CD's have 16 bit resolution or 65,536 possible output levels
 - New DVD audio samples at 192 khz with 24 bit resolution or $2^{24} = 16,777,216$

Analog to Digital Conversion (ADC)

- Successive approximate conversion steps
 - Scale the input to 0-3 volts (example)
 - Sample and hold the input
 - Internally generate and start ramp and compare
- Flash Compare
 - Compare voltage to one of 2^n possible voltage levels.
8 bit ADC would have 255 comparators.
- Note that by definition, ADC have quantizing errors (number of bits resolution)


Successive Approximation AD

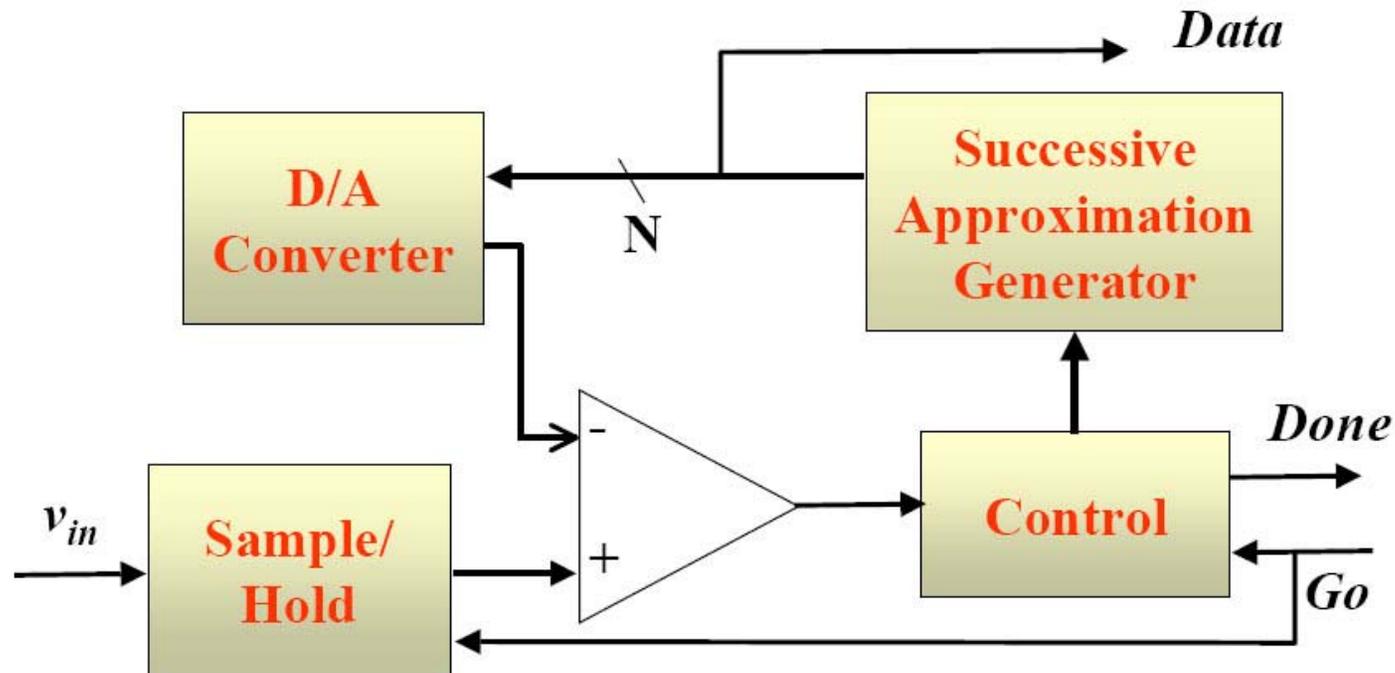

Serial conversion takes a time equal to $N(t_{D/A} + t_{comp})$

Binary Adder – m^{th} bit

C_{in}	A	B	Sum	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


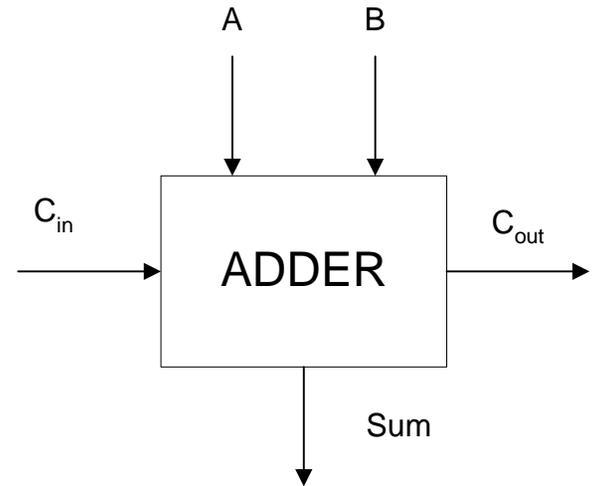


Sum =



C_{out} =

Switch Bounce

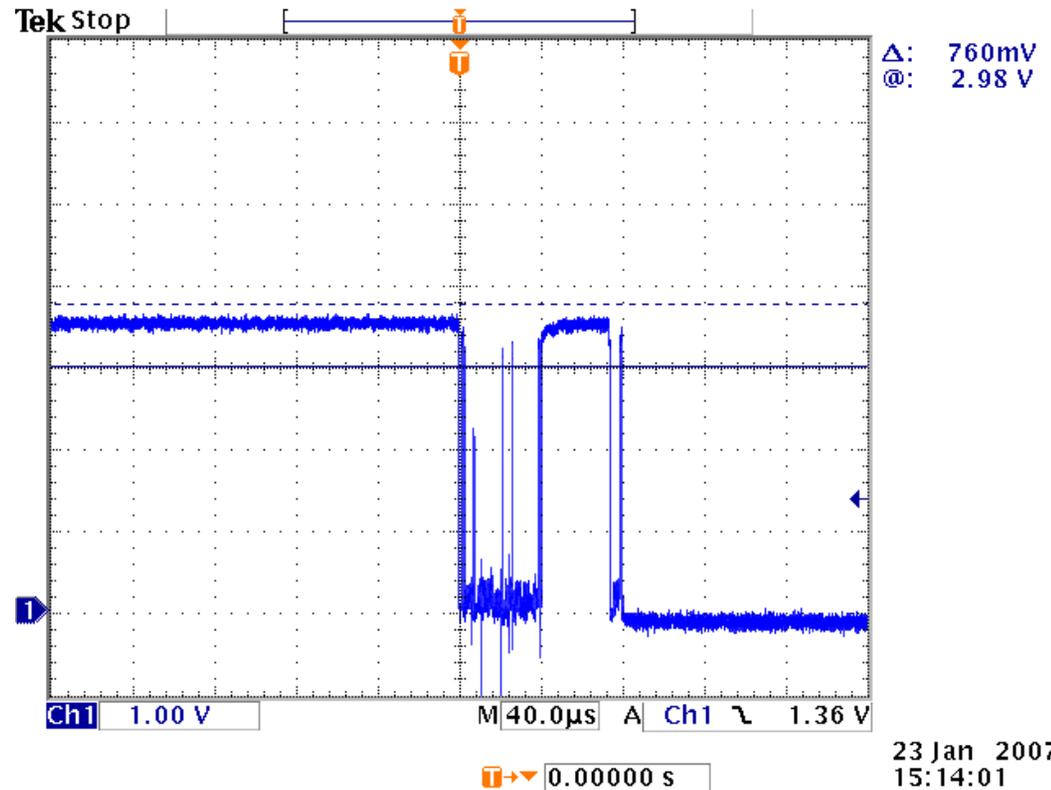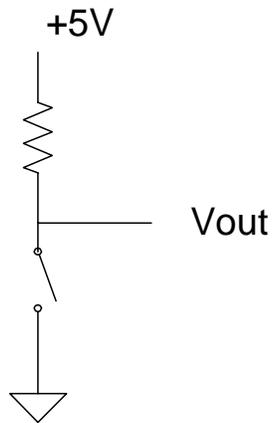- All mechanical switches have “switch bounce”



Debounce Circuit

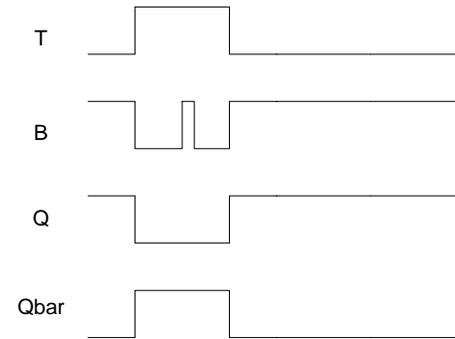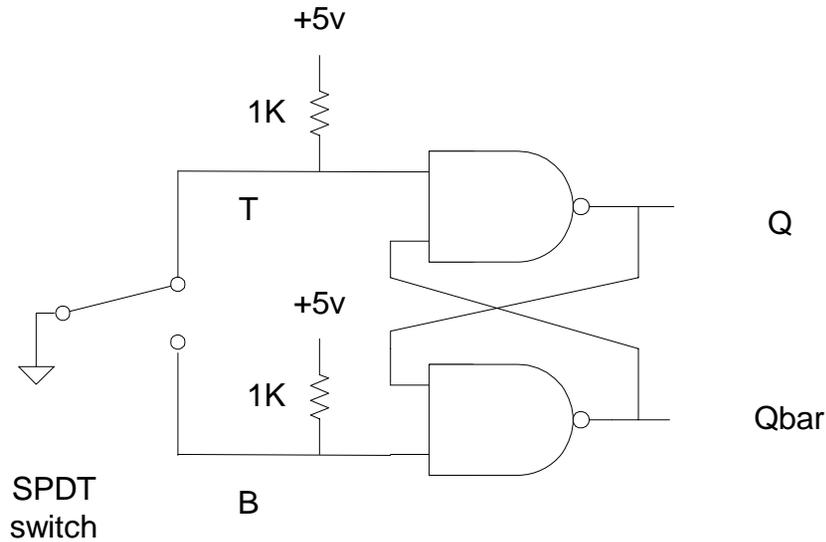

Requires SPDT switch

T	Qbar	Q
0	0	1
0	1	1
1	0	1
1	1	0


T	0		
B	1		
Q			
Qbar			

Lab 5



- Design, build and keep the electronics for a digital lock.
- Unlock key based on sequence of 0, 1.




Digital Lock

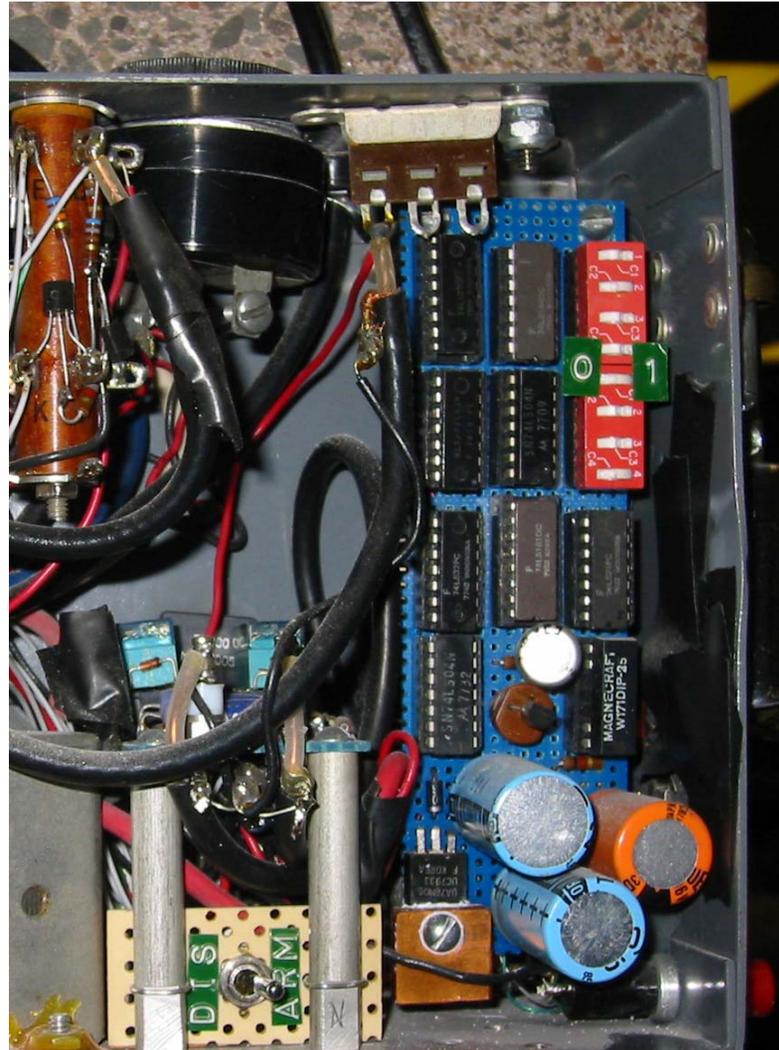

Pushbutton Clocking

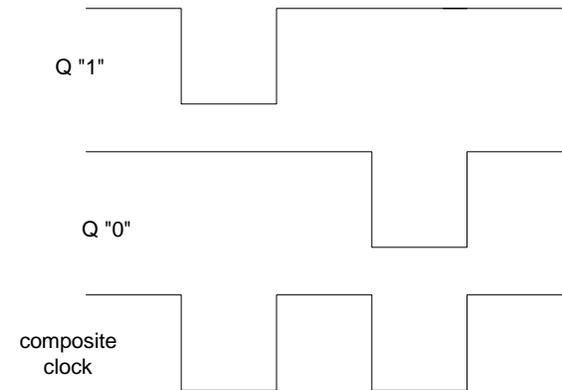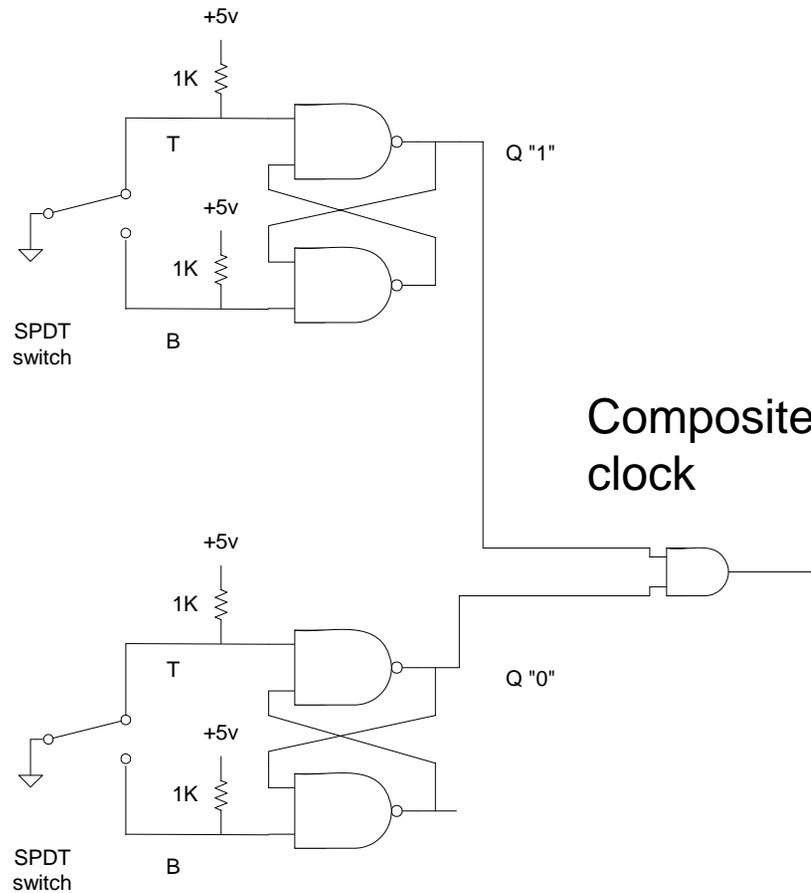

Digital Lock

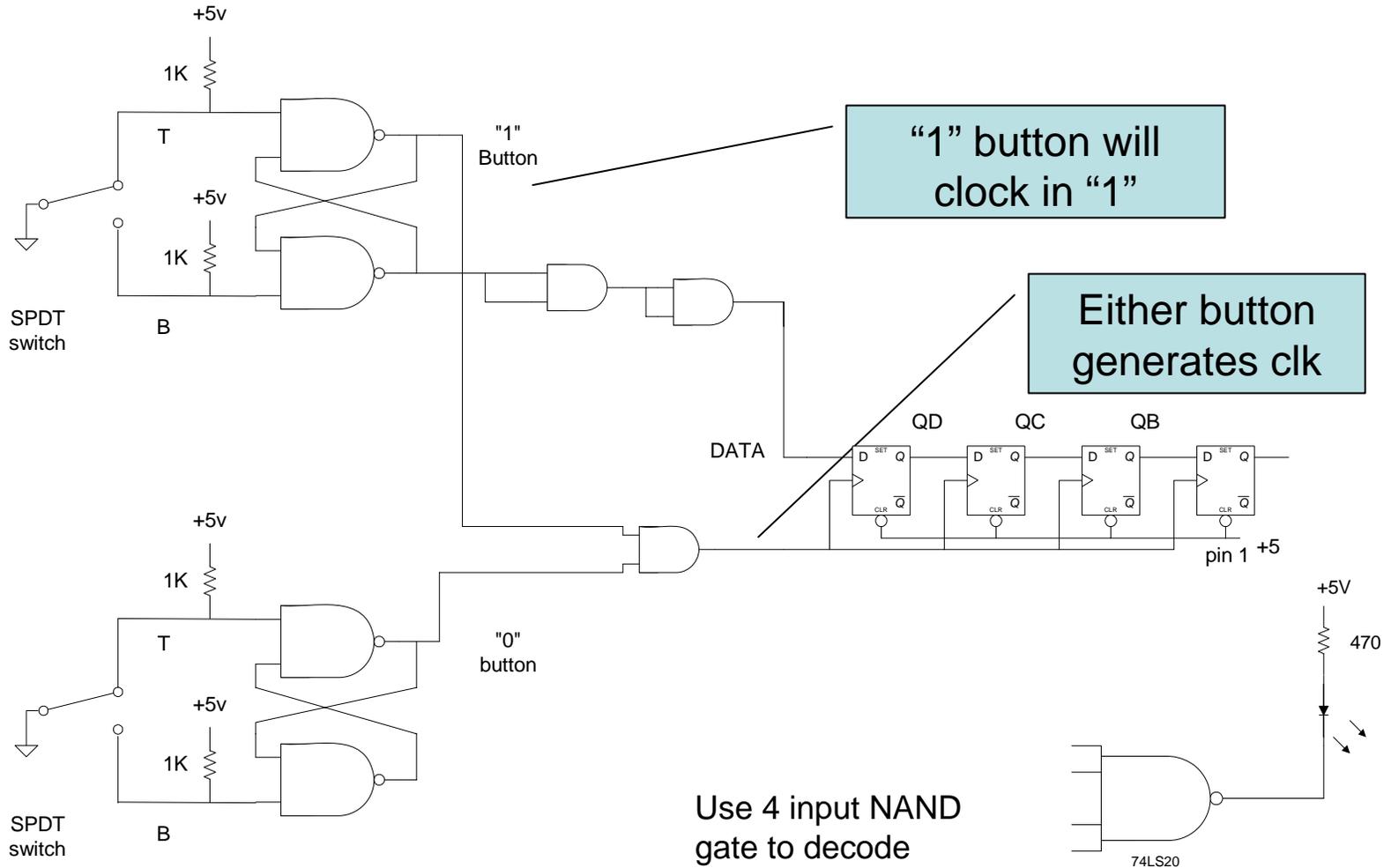

Design guidelines


- Apply power and ground to each chip
- Add 10 uf or greater to power bus
- Select and wire up desired code
- For control inputs on all IC's or inputs that matter, tie to a "1" or a "0". Floating inputs are in an indeterminate state.

Construction Techniques

- Consider placement of IC's
- Wire up power and ground to all IC's
 - Use all four power rails
- Build and debug in stages
 - Debounce circuits
 - Composite clock
 - Shift registers
 - Neat wiring helps!

Enhancements

- Increase lock code to 8 bits
- Add power up reset

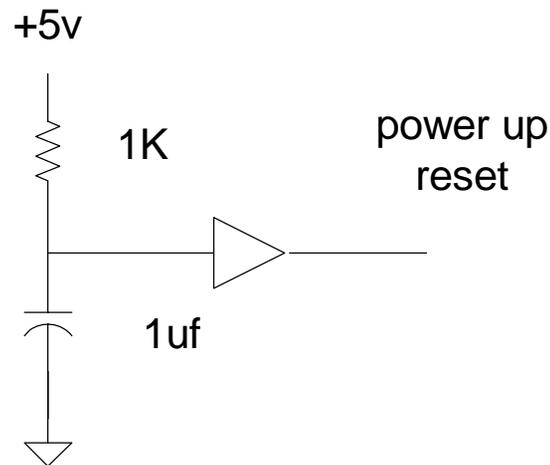

Lab 5

- Use last three aisle on the left at the end of the 6.111 lab
- Pick up IC's and tools from LA's.
- You may keep the completed circuit you build (pushbuttons, IC's, everything!)
- Return tools.

Odds and Ends

- FPGA: Field Programmable Gate Array
 - Use high level hardware description language (HDL) to describe behavior
 - Can be re-programmed thousands of times.
 - very inexpensive kits
 - free software tools on web
- Please complete your evaluation of this course