


6.301 Solid-State Circuits

Recitation 19: More on Translinear Circuits

Prof. Joel L. Dawson

We're going to continue today with more on "Pythagorators," and then talk about an industry design: The LH0091 True RMS to DC converter. It's a very interesting application of some of these translinear ideas. In the middle of the class, though, we'll try our hand at a small translinear design problem.

Five-Transistor Pythagorator

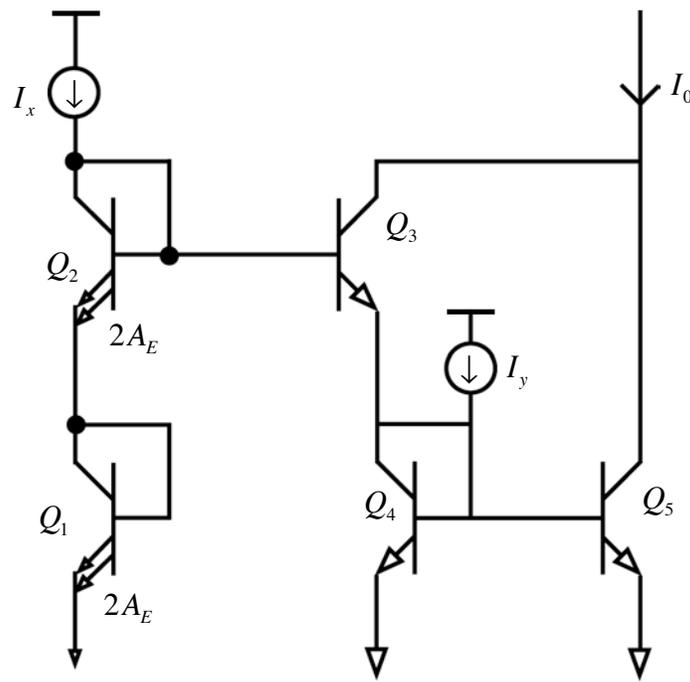

What is I_0 in terms of I_x and I_y ? Well, we see a Gilbert loop right away in $Q_1 - Q_4$. Must use the more general form:

$$\frac{I_x}{2A_E} \cdot \frac{I_x}{2A_E} = \frac{I_3}{A_E} \frac{(I_3 + I_y)}{A_E}$$

$$\frac{1}{4} I_x^2 = I_3 (I_3 + I_y)$$

6.301 Solid-State Circuits

Recitation 19: More on Translinear Circuits

Prof. Joel L. Dawson

Need the relationship between I_3 and other variables of interest. We can write

$$I_0 = I_3 + I_5$$

Q_4 and Q_5 form a current mirror (which, incidentally, is the simplest possible Gilbert loop):

$$I_5 = I_4 = I_3 + I_y$$

$$I_0 = 2I_3 + I_y \Rightarrow I_3 = \frac{I_0 - I_y}{2}$$

Substituting back into our first expression:

$$\begin{aligned} \frac{1}{4} I_x^2 &= \left(\frac{I_0 - I_y}{2} \right) \left(\frac{I_0 - I_y}{2} + I_y \right) \\ &= \frac{1}{4} (I_0^2 - 2I_y I_0 + I_y^2) + \frac{1}{2} I_y I_0 - \frac{1}{2} I_y^2 \end{aligned}$$

$$\frac{I_x^2}{4} = \frac{I_0^2}{4} - \frac{I_y^2}{4} = \frac{1}{4} (I_0^2 - I_y^2)$$

$$I_0^2 = I_x^2 + I_y^2 \Rightarrow I_0 = \sqrt{I_x^2 + I_y^2}$$

Question of the day: How did someone come up with that? Now let's try some on our own.

6.301 Solid-State Circuits

Recitation 19: More on Translinear Circuits

Prof. Joel L. Dawson

CLASS EXERCISE 1 (to be worked on individually):

Design a translinear circuit that performs the function

$$i_0 = 4 \cdot i_i$$

(Workspace)

CLASS EXERCISE 2 (to be worked on in pairs):

Design a translinear circuit that gives the following input-output relation:

$$i_0 = ki^3$$

6.301 Solid-State Circuits


Recitation 19: More on Translinear Circuits

Prof. Joel L. Dawson

Now let's turn our attention to National's LH0091 True RMS to DC converter. It is called this because its output is

$$v_0 = \sqrt{\frac{1}{RC} \int |v_I|^2 dt}$$

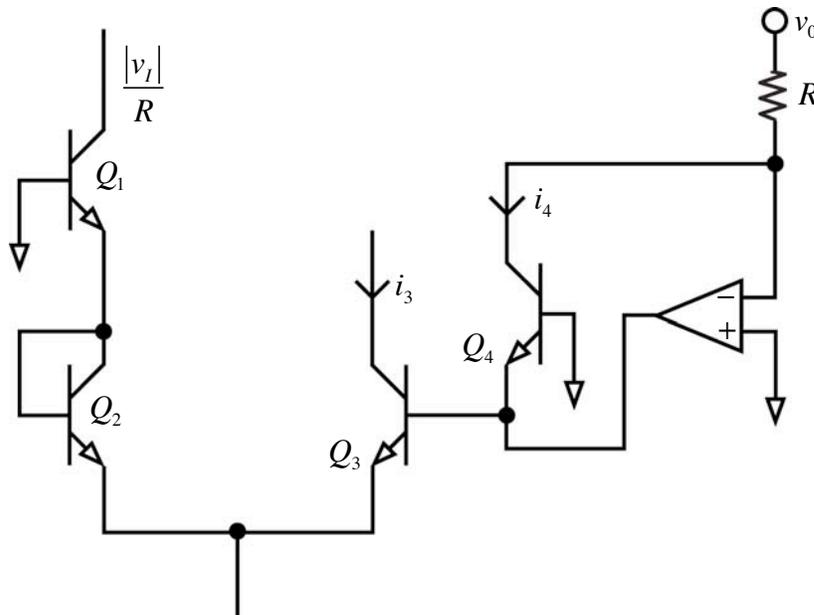
To see how this happens, turn your attention to $Q_1 - Q_4$ indicated on the schematic:



See the Gilbert loop? $I_1 I_2 = I_3 I_4$

But $I_1 = I_2 = \frac{|v_I|}{R}$, and $I_4 = \frac{v_0}{R}$. This gives $\frac{|v_I|^2}{R^2} = i_3 \left(\frac{v_0}{R} \right)$.

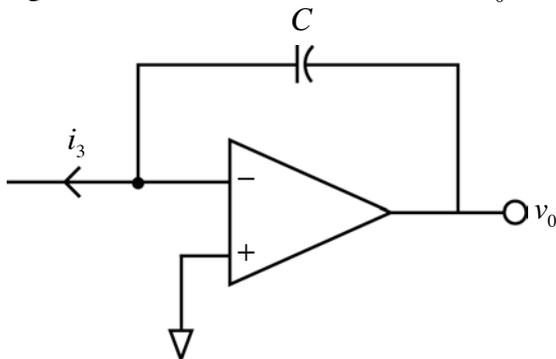Looking back at the schematic, we can tie v_0 and i_3 together:



$$C \frac{dv_0}{dt} = i_3$$

$$v_0 = \frac{1}{C} \int i_3 dt$$

6.301 Solid-State Circuits

Recitation 19: More on Translinear Circuits

Prof. Joel L. Dawson

So now we can fully analyze the circuit:

$$\frac{|v_I|^2}{R} = i_3 \frac{v_0}{R}$$

Integrate both sides

$$\frac{1}{R^2} \int |v_I|^2 dt = \frac{1}{R} \int i_3 v_0 dt$$

Now assume v_0 changes slowly compared to v_I , so that we can write

$$\frac{1}{R^2} \int |v_I|^2 dt = \frac{v_0}{R} \int i_3 dt$$

$$\frac{1}{R^2} \int |v_I|^2 dt = \frac{v_0}{R} C v_0$$

$$v_0 = \sqrt{\frac{1}{RC} \int |v_I|^2 dt}$$

MIT OpenCourseWare
<http://ocw.mit.edu>

6.301 Solid-State Circuits
Fall 2010

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.