

6.301 Solid-State Circuits

Recitation 21: Current-Feedback, or Transimpedance, Amplifiers
Prof. Joel L. Dawson


By now, you've practically grown up hearing about a "constant gain-bandwidth product." Where does that come from? And is it really a physical law?

The answer to the second question is that it is not a physical law. While it is true that you will often find it easier to get high gain for low bandwidths, this is more a consequence of the topology choices that we make than an expression of nature's laws. For instance, there is something called a "distributed amplifier," for which gain trades off with delay rather than bandwidth.

So what about the first question?


CLASS EXERCISE:

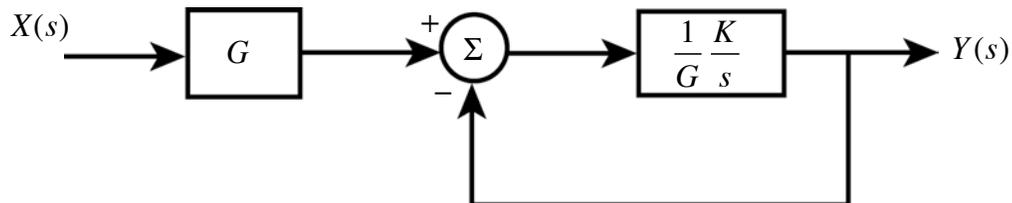A simple inverting amplifier using an op-amp can be approximately modeled as follows:



Here, G is the ideal gain, and the dynamics of the op-amps are captured by $\frac{k}{s}$. Show that as the gain G is varied, this system exhibits a constant gain-bandwidth product.

(Workspace)

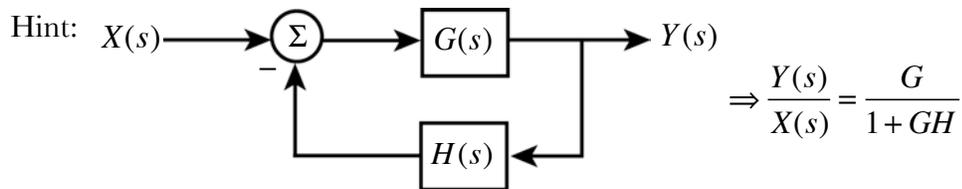

6.301 Solid-State Circuits

Recitation 21: Current-Feedback, or Transimpedance, Amplifiers


Prof. Joel L. Dawson

Op-amps are often “compensated” such that their dynamics are dominated by one low-frequency pole. Op-amps are almost everywhere...hence the common belief in a fundamental gain-bandwidth product.

The current-feedback amplifier happens to be an amplifier that does not follow the constant gain-bandwidth “rule”...

Current-Feedback Amplifiers

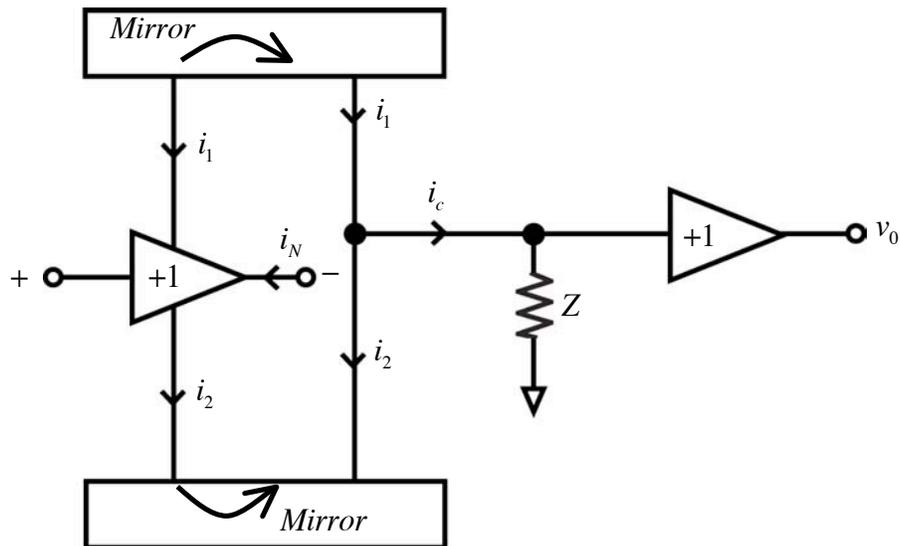Let’s look at the implementation of a typical transimpedance amplifier.



6.301 Solid-State Circuits

Recitation 21: Current-Feedback, or Transimpedance, Amplifiers

Prof. Joel L. Dawson

The underlying assumption is that i , i_2 , and i_N together satisfy KCL. Thus,


$$(1) \quad i_1 + i_N = i_2$$

$$(2) \quad i_1 = i_2 + i_C$$

$$(1) \rightarrow (2) \quad \cancel{i_1} = \cancel{i_1} + i_N + i_C$$

$$i_C = -i_N \Rightarrow \boxed{v_0 = i_C z = -Z i_N}$$

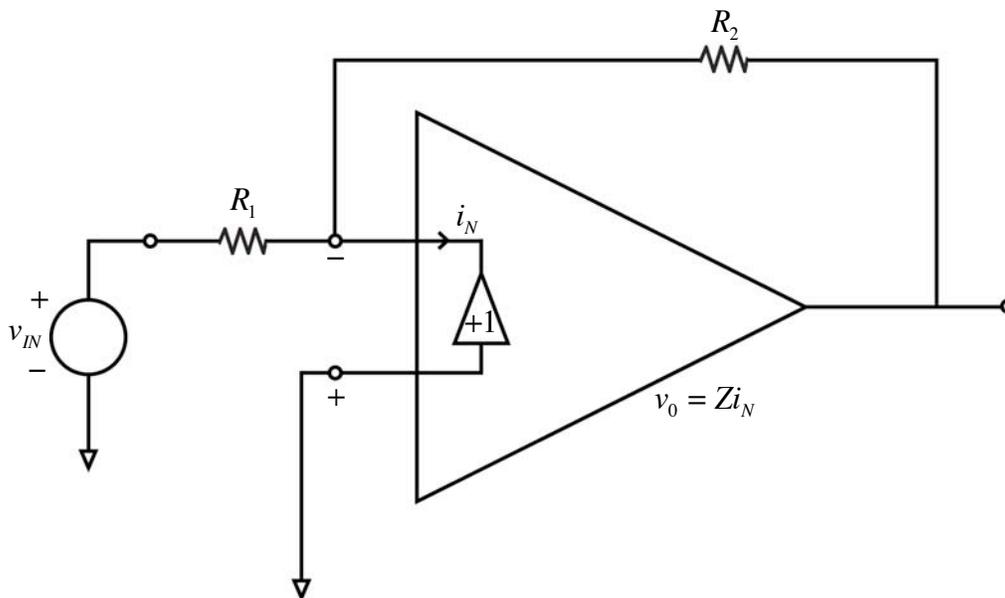Pretty simple. It turns out that we can use this circuit in many instances just like a voltage op-amp. Let's see how.



A start to the analysis is to observe that, as in the case of the voltage op-amp, $V_+ = V_- (= 0)$. The reasons are different, of course. For the voltage op-amp, it was negative feedback, combined with infinite gain, that forced $V_+ = V_-$. Here, $V_+ = V_-$ by construction, because we have placed a voltage buffer between them.

6.301 Solid-State Circuits

Recitation 21: Current-Feedback, or Transimpedance, Amplifiers

Prof. Joel L. Dawson

Very well. We write KCL at the inverting input:

$$\frac{v_{IN}}{R_1} + \frac{v_0}{R_2} = i_N$$

Recall that $v_0 = -Zi_N \Rightarrow i_N = -\frac{v_0}{Z}$

$$\frac{v_{IN}}{R_1} + \frac{v_0}{R_2} = -\frac{v_0}{Z}$$

$$\frac{v_{IN}}{R_1} + \frac{v_0}{R_2} + \frac{v_0}{Z} = 0$$

$$v_0 \left(\frac{1}{Z} + \frac{1}{R_2} \right) = -\frac{v_{IN}}{R_1}$$

$$v_0 \left(\frac{R_2 + Z}{ZR_2} \right) = -\frac{v_{IN}}{R_1}$$

$$v_0 = -\frac{ZR_2}{R_2 + Z} \frac{1}{R_1} v_{IN}$$

Now the idea behind a transimpedance amp is that Z , the transimpedance, is far and away the biggest impedance around.

$$Z \gg R_2$$

$$v_0 = -\left(\frac{ZR_2}{R_2 + Z} \right) \frac{1}{R_1} v_{IN}$$

$$v_0 \approx -\frac{R_2}{R_1} v_{IN}$$


Just like a voltage
op-amp!

6.301 Solid-State Circuits


Recitation 21: Current-Feedback, or Transimpedance, Amplifiers

Prof. Joel L. Dawson

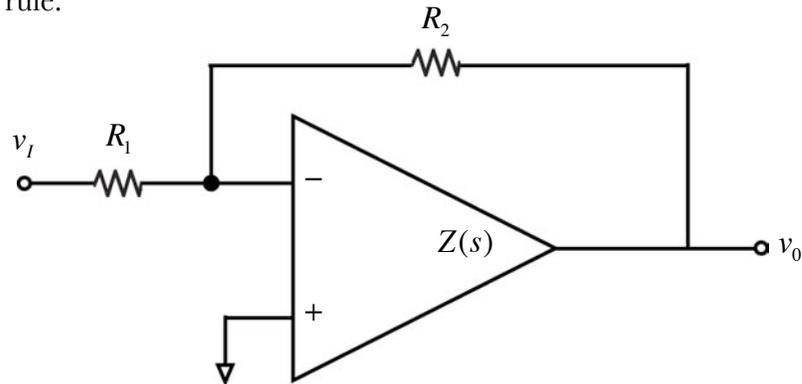
It turns out that with the transimpedance amplifier we are not subject to the constant gain-bandwidth product rule.



Block diagram:

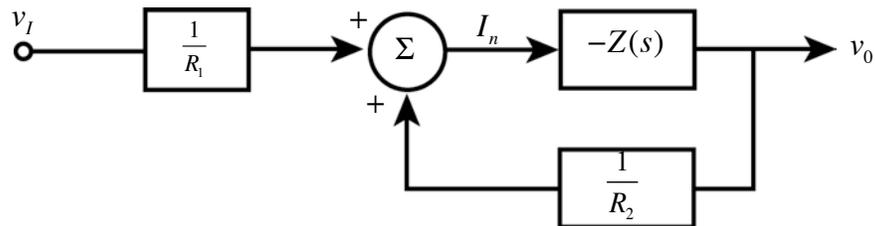

Rearranging:

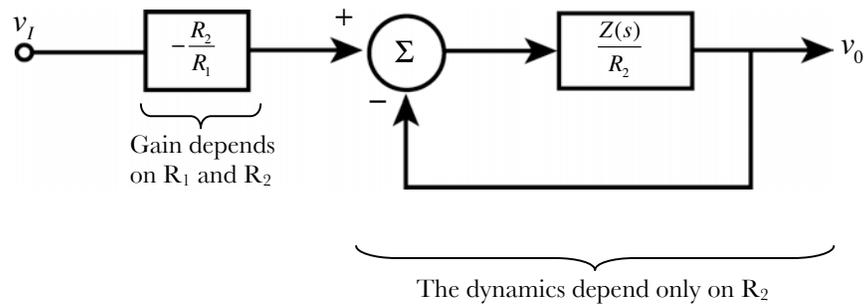


So you can fix your bandwidth by choosing R_2 , and set your gain by choosing R_1 in relation to R_2 .

We'll close by looking at a common input buffer structure.

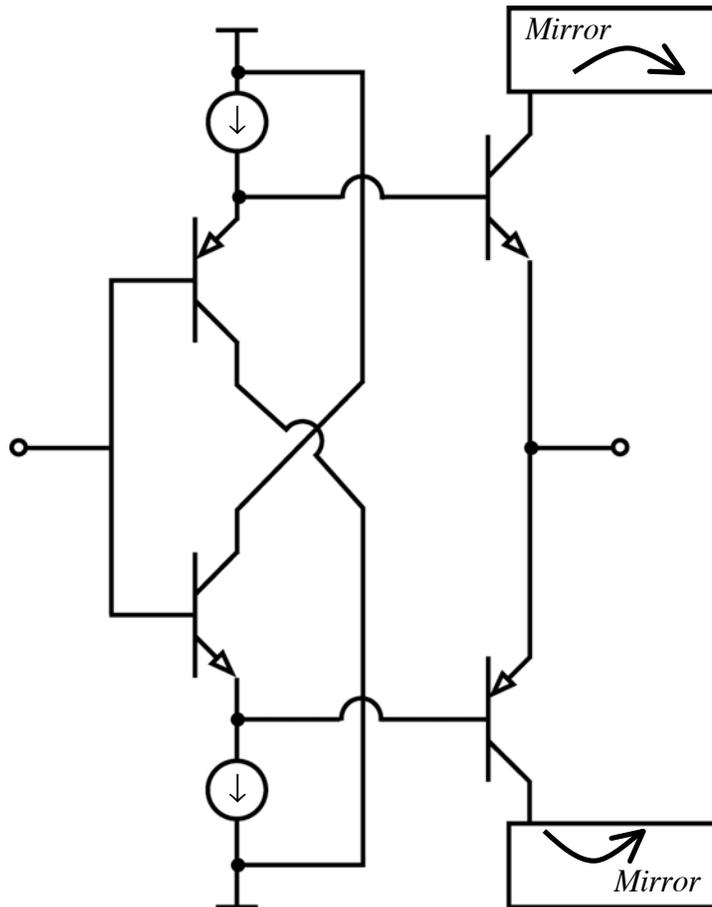6.301 Solid-State Circuits

Recitation 21: Current-Feedback, or Transimpedance, Amplifiers
Prof. Joel L. Dawson

Buffer circuit topology: (sometimes called a “diamond circuit”)



For design project, read course notes about slew rate for transimpedance amplifiers.

MIT OpenCourseWare
<http://ocw.mit.edu>

6.301 Solid-State Circuits
Fall 2010

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.