

## 6.301 Solid-State Circuits

Recitation 23: Zener Diode References (continued)


Prof. Joel L. Dawson

---

We've talked about this before, but it bears repeating: True DC performance is every bit as difficult to achieve as high-frequency performance. By "DC" performance, we're talking low DC offsets, in the case of amplifiers, and low drift performance. Usually with drift, temperature changes are the enemy.

With Zener references, we've already talked about using self-biasing to set the current through the diode. Why go to such pains? It turns out that with regards to temperature stability, Zener diodes tend to have a "sweet spot": run them at a particular current, and their temperature stability is especially good.

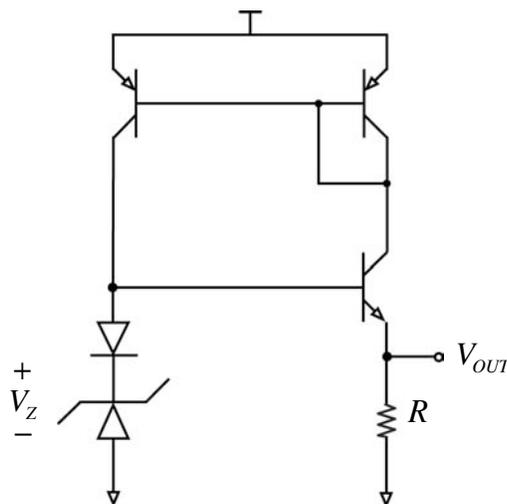In the last class we looked at a particular self-biased cell. Let's look at it again.




CLASS EXERCISE: Argue that the output impedance of this circuit must be negative.

## 6.301 Solid-State Circuits

Recitation 23: Zener Diode References (continued)


Prof. Joel L. Dawson

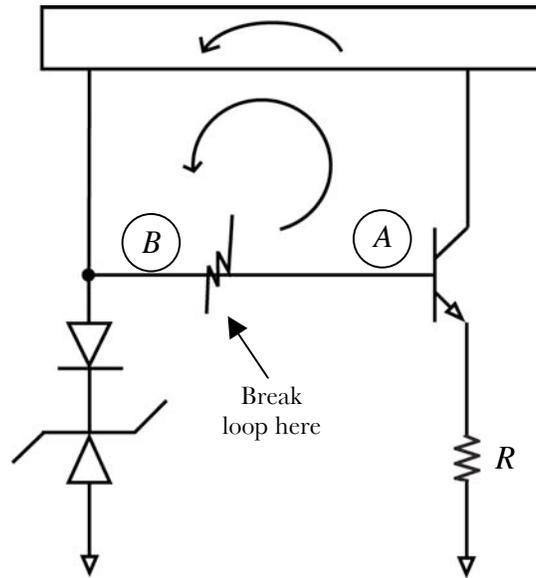Another interesting tidbit about this circuit is that it is actually an example of positive feedback:



After loop is broken, raising node (A) causes (B) to rise! We don't get into trouble because the gain around the loop is small ( $<1$ ).

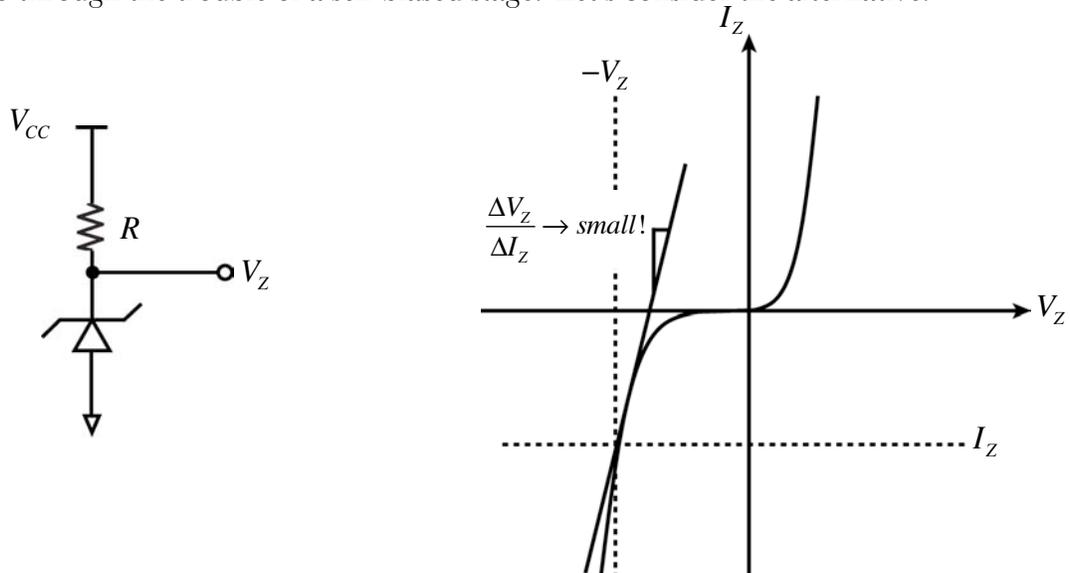Again, why go through the trouble of a self-biased stage? Let's consider the alternative.



A good Zener diode will have a small incremental resistance,  $r_z$ . If we write out the response of the output voltage to changes in the supply, we get:

## 6.301 Solid-State Circuits

Recitation 23: Zener Diode References (continued)

Prof. Joel L. Dawson

---

$$\frac{\Delta V_z}{\Delta V_{CL}} = \frac{r_z}{r_z + R}$$

Time for some numbers. Let  $V_{CC} = 15V$ ,  $r_z = 10\Omega$ ,  $V_Z = 6.2V$ . Further, suppose that the “sweet spot” for  $I_Z$  is  $7.5mA$ , at which point the temperature coefficient is a mere  $5ppm/^\circ C$ . The value of  $R$  is determined by the sweet spot:

$$R = \frac{V_{CC} - V_Z}{I_Z} = \frac{15V - 6.2V}{7.5mA} = 1.17k\Omega$$

Now, what happens when there is a 1% change in  $V_{CC}$ ?

$$\Delta V_z = \left( \frac{R_z}{r_z + R} \right) \Delta V_{CC} = \left( \frac{10r}{1.18k\Omega} \right) 150mV = 1.25mV$$

This, in the rarefied air of good voltage references, is huge. We can appreciate that by considering what temperature swing would correspond to this kind of change.

$$\frac{\Delta V_z}{V_z} = \frac{1.25mV}{6.2V} = 200ppm = (40^\circ C)(5ppm / ^\circ C)$$

For those of us who work in Fahrenheit, it would take a temperature swing of  $72^\circ F$  to cause this much change! The point is that the care you took to temperature stabilize the Zener will be undermined by fluctuations or drift in the power supply.


## 6.301 Solid-State Circuits

Recitation 23: Zener Diode References (continued)

Prof. Joel L. Dawson

---

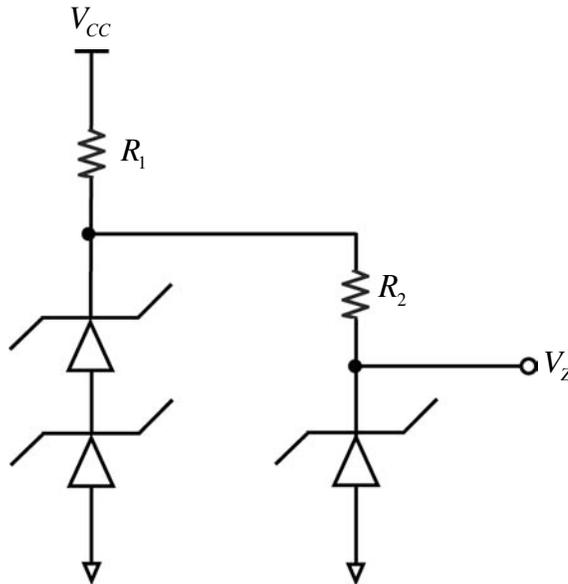One way to improve things is to use pre-regulation:




Otherwise, we go to any number of self-biasing techniques. The class exercise is a good example.

---
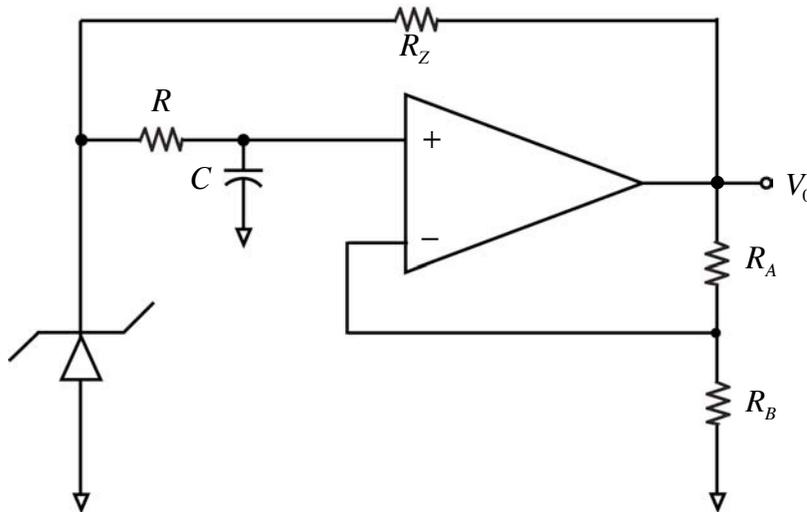
### Another Self-Biasing Technique

As usual, our old friend the op-amp comes in handy here.



Notice that the op-amp is just connected as a non-inverting amplifier of gain  $k$ . For purposes of the DC bias calculation, notice that  $R$  and  $C$  have no impact.


## 6.301 Solid-State Circuits

Recitation 23: Zener Diode References (continued)

Prof. Joel L. Dawson

---

Simplifying, we can draw this as

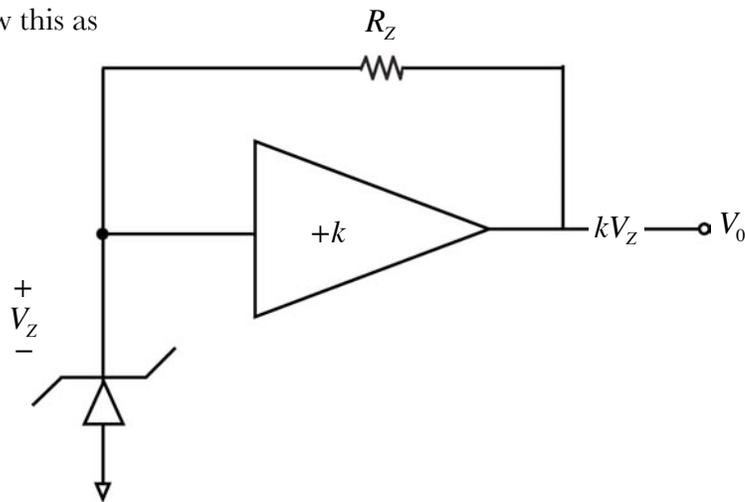

And now  $I_z$  is straightforward to calculate:

$$I_z = \frac{kV_z - V_z}{R_z} = \left( \frac{k-1}{R_z} \right) V_z$$

The nice thing about this circuit is that it let's us get stable voltage references at values other than  $V_z$ . For example, suppose that we need an output voltage of 10V, and our Zener diode has a  $V_z$  of 6.2V with a "sweet spot" current of 7.5mA. We select  $k$  according to

$$kV_z = 10V \Rightarrow k = \frac{10V}{6.2V} = 1.61$$

Then, we choose  $R_z$  to get the  $I_z$  that we want.

$$7.5mA = \left( \frac{1.61-1}{R_z} \right) (6.2V)$$

$$R_z = \left( \frac{0.61}{7.5mA} \right) (6.2V) = 504\Omega$$


## 6.301 Solid-State Circuits

Recitation 23: Zener Diode References (continued)

Prof. Joel L. Dawson

---

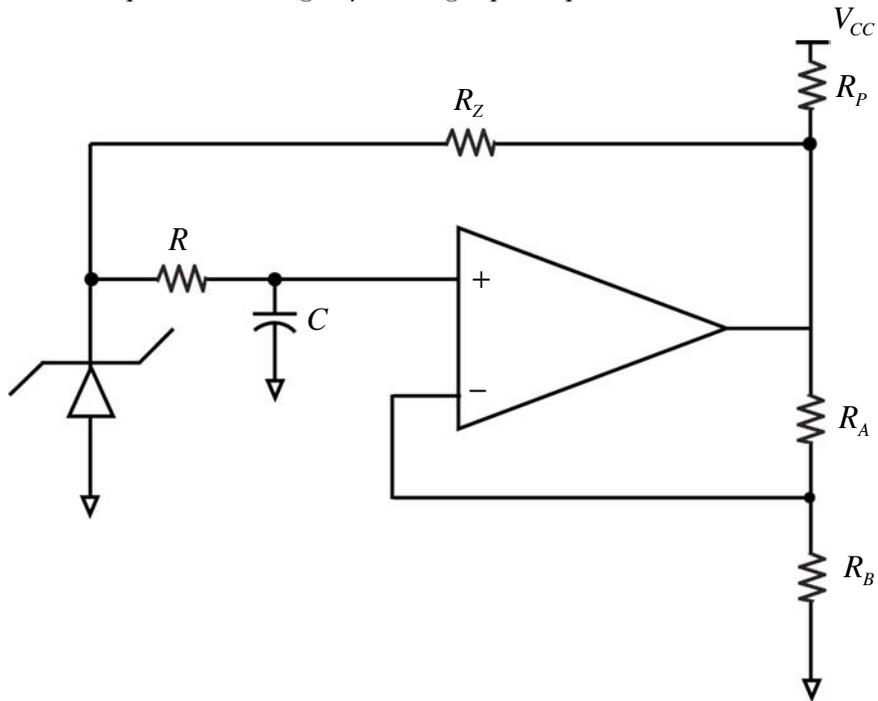This circuit has the drawback of demanding a relatively large amount of current from the output of the op-amp. We can improve on things by adding a pull-up resistor as follows:



$R_P$  can be chosen to provide much of the Zener current. In addition, it helps with startup for this circuit.

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.301 Solid-State Circuits  
Fall 2010

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.