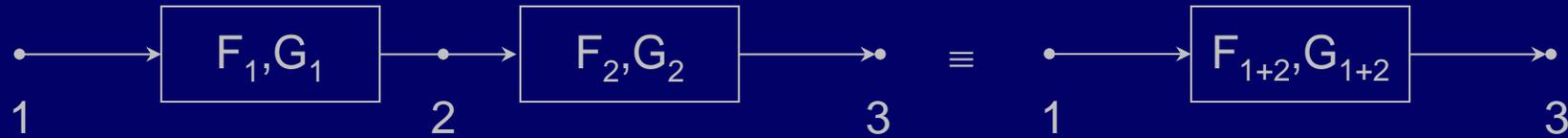


Noise in Cascaded Amplifiers



$$F_{1+2} \triangleq \frac{S_1/N_1}{S_3/N_3} \text{ where } S_3 = G_1 G_2 S_1$$

$$N_2 = kT_0 F_1 G_1 \left(\text{Recall } F_1 = \frac{S_1/N_1}{S_2/N_2} \right)$$

$$N_3 = \underbrace{G_2 kT_0 F_1 G_1}_{\text{amplified from "2"}} + \underbrace{G_2 (F_2 - 1) kT_0}_{\text{excess from "2"}}$$

$$\therefore S_3/N_3 = G_1 G_2 S_1 / (G_1 G_2 F_1 + G_2 (F_2 - 1)) (kT_0)$$

$$= (S_1/kT_0) / \left(F_1 + \frac{F_2 - 1}{G_1} \right)$$

$$\therefore F_{1+2} = \frac{S_1/N_1}{S_3/N_3} = F_1 + \frac{F_2 - 1}{G_1}$$

Noise in multiple cascade amplifiers

By extension: $F_{1,2,3} = F_{1+2} + \frac{F_3 - 1}{G_1 G_2}$ $F_{1+2} = F_1 + \frac{F_2 - 1}{G_1}$

In general,

$$F_{1,2,\dots} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \dots \text{cascade noise formula}$$


Note:



The better choice is not obvious.

$F_{1,2}$ also depends on interstage impedance mismatches and gain of the first amplifier, not just on F_1

Noise in superheterodyne receivers

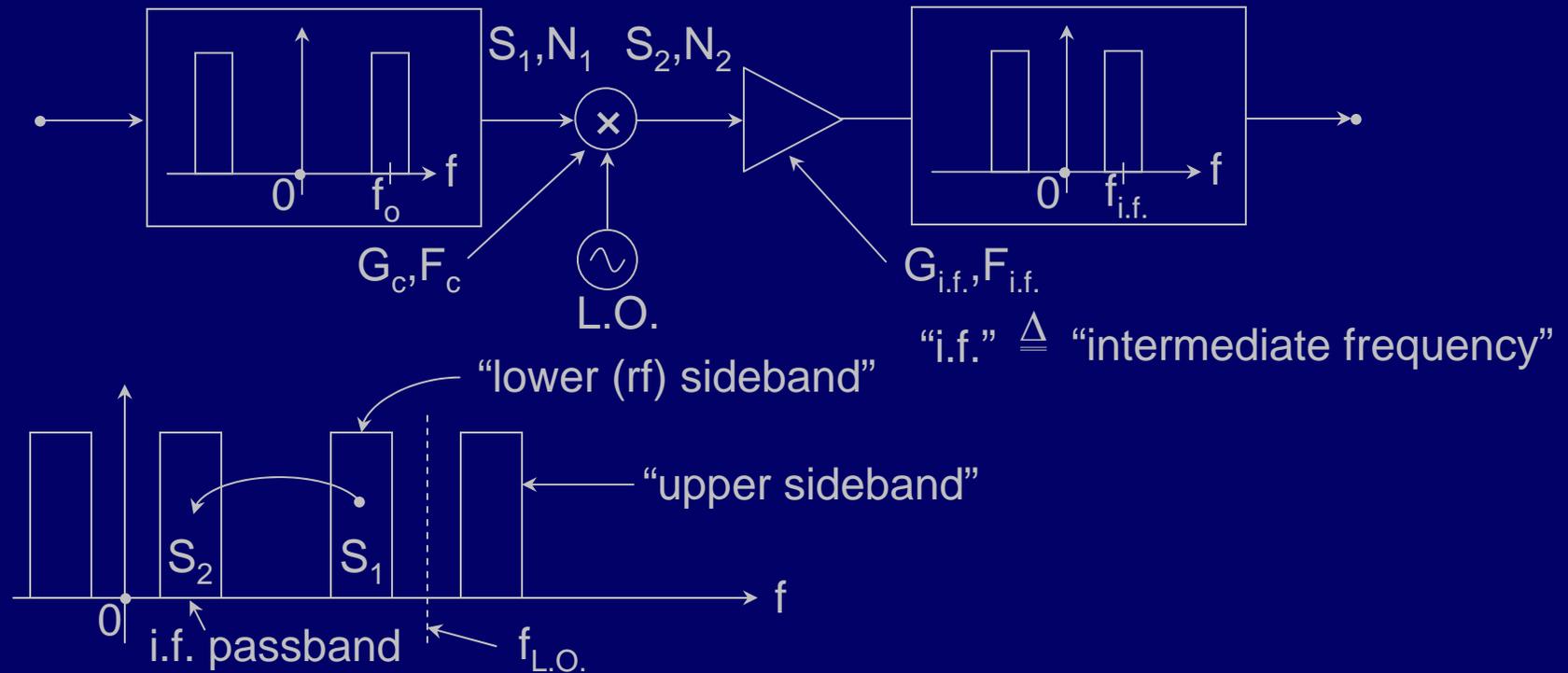

- 1) “Conversion loss of mixer” $\triangleq L_c \triangleq \frac{1}{G_c} = \frac{S_2(\text{i.f.})}{S_1(\text{r.f., SSB})}$
- 2) “Noise temperature ratio of mixer” $\triangleq t_r = N_2(\text{i.f.})/kT_0$
- 3) $F_{\text{mixer}} \triangleq \frac{S_1/N_1}{S_2/N_2} = \frac{S_1/kT_0}{(S_1/L_c)/t_r kT_0} = L_c t_r$

Noise in superheterodyne receivers


$$3) F_{\text{mixer}} \triangleq \frac{S_1/N_1}{S_2/N_2} = \frac{S_1/kT_o}{(S_1/L_c)/t_r kT_o} = L_c t_r$$

$$4) F_{\text{mixer+i.f. amp.}} = F_{\text{mixer}} + \frac{F_{\text{i.f.}} - 1}{G_{\text{mixer}}}$$
$$= L_c t_r + L_c (F_{\text{i.f.}} - 1) = L_c (F_{\text{i.f.}} + t_r - 1)$$


e.g. $F_{\text{mixer+i.f. amp.}} \cong 2 - 8 (\sim 3 - 9 \text{ dB})$

Basic receiver types-Amplification


1) Simple detector

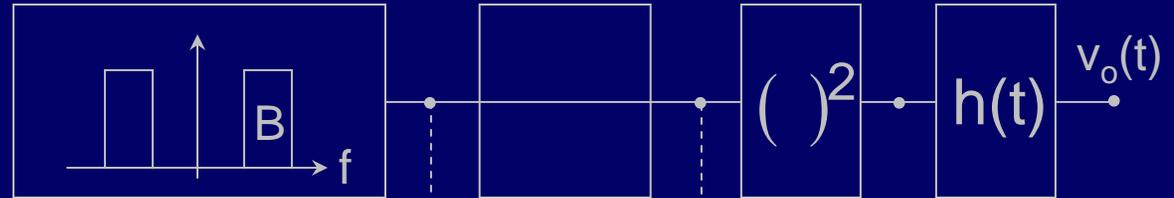

2) RF Amplifier

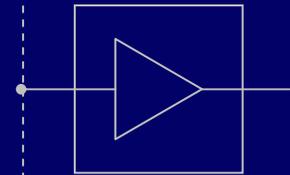





3) Superhetrodyne

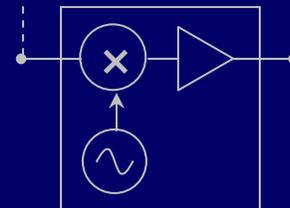

OR


OR

Basic receiver types-Combinors

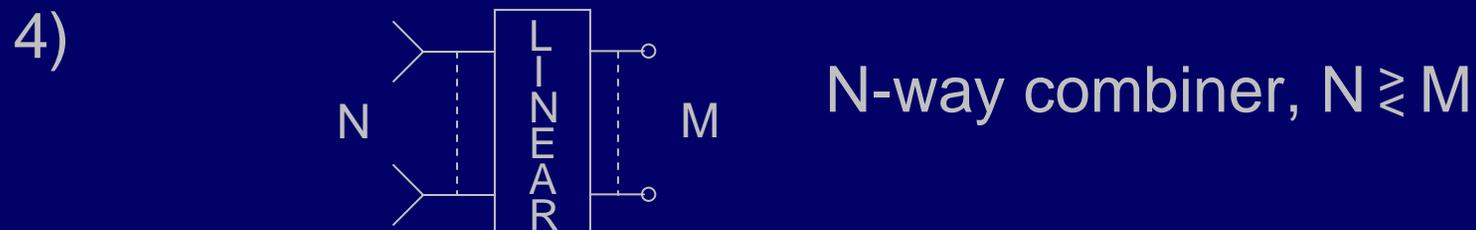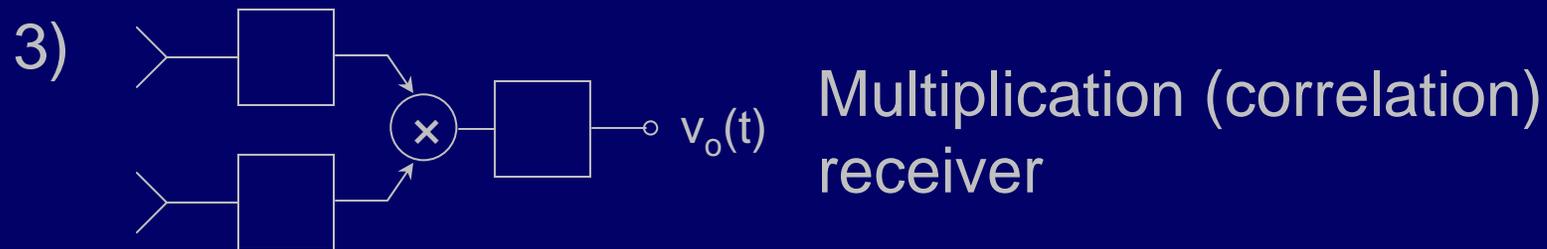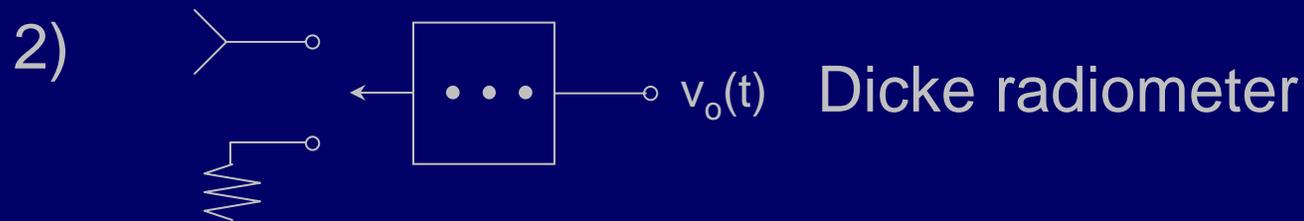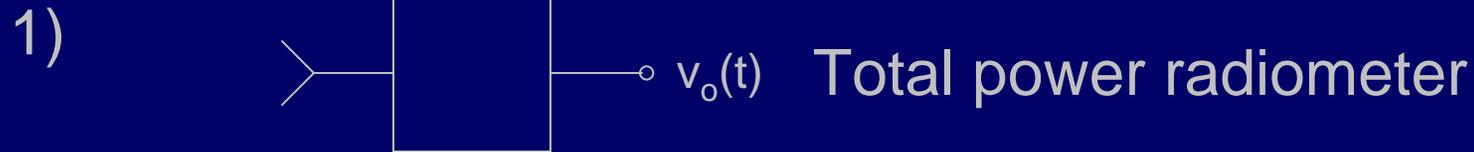


Passive Multiport Networks


1)

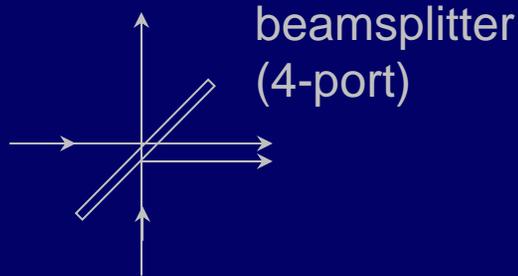


2)

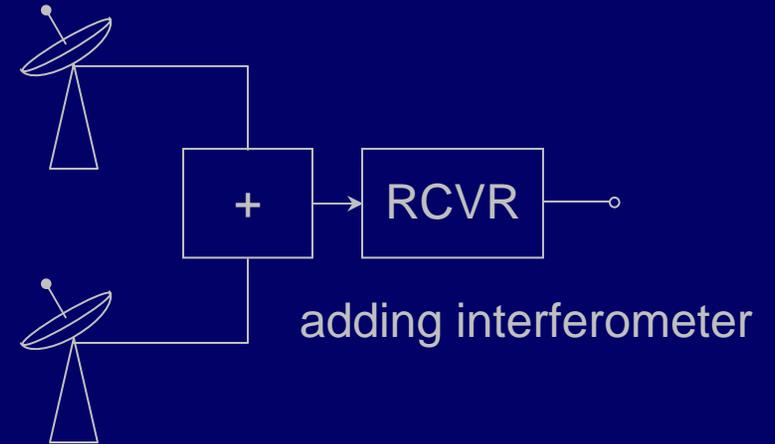

3)

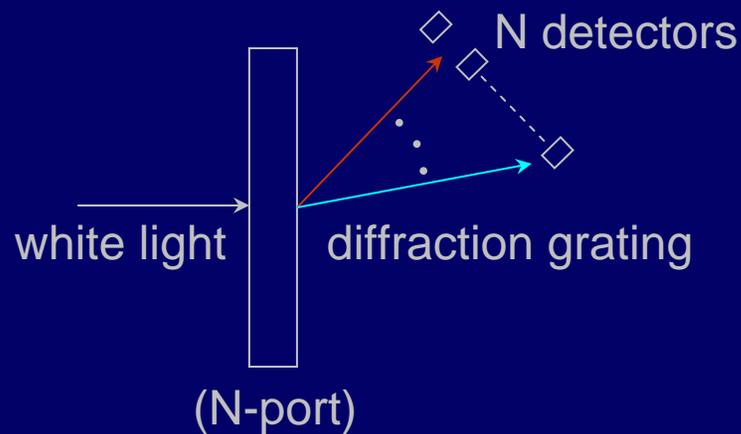


4)

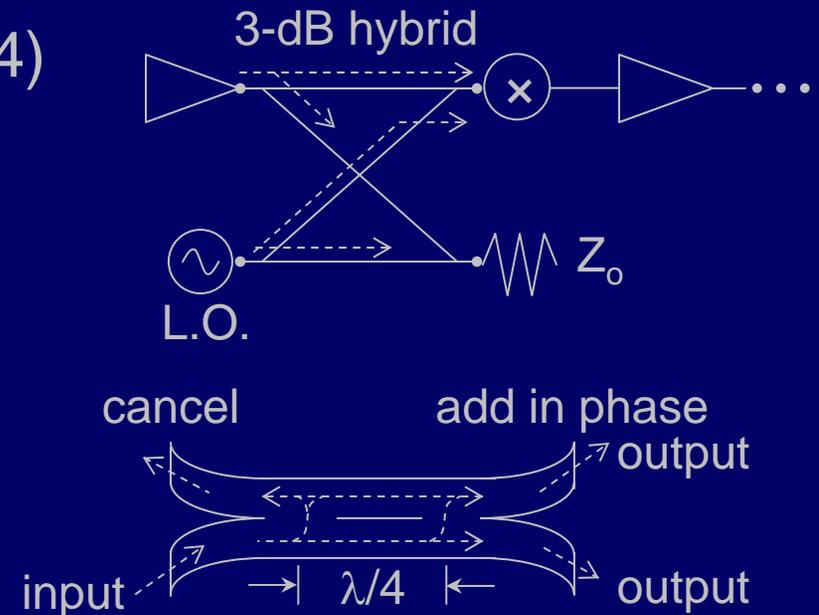



Passive Multiport Networks

5) "Magic tee"

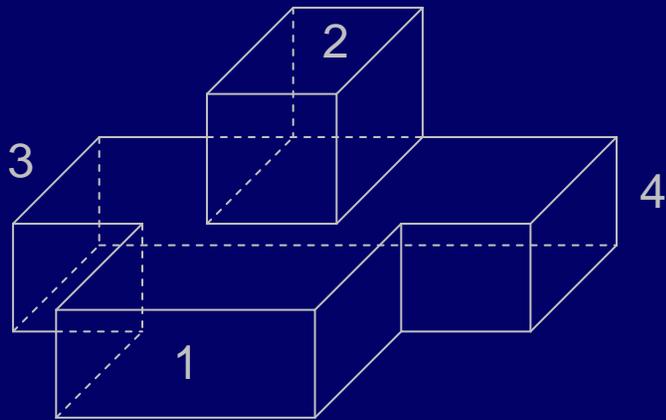


Port 1 orthogonal to Port 2
Port 3 orthogonal to Port 4
All 4 ports can be matched

6) Frequency converter

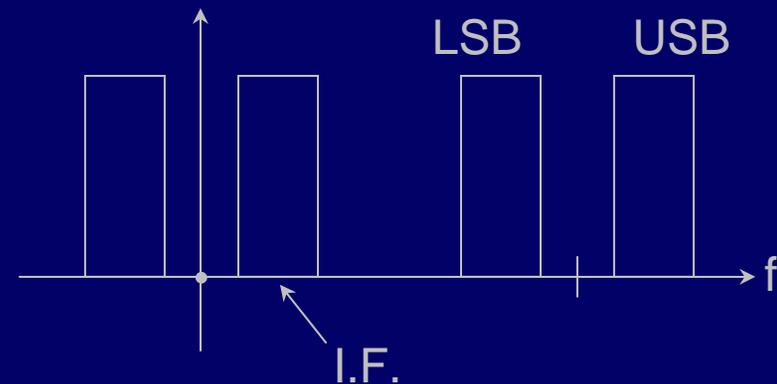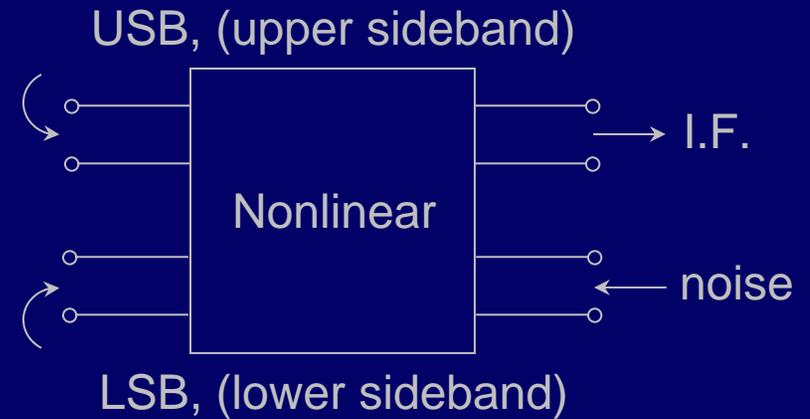

Linear Passive N-port Networks

Define exchangeable power = $\left\{ \begin{array}{l} |a_i|^2 \text{ toward port } i \\ |b_i|^2 \text{ from port } i \text{ (W or } \text{WHz}^{-1}) \end{array} \right\}$

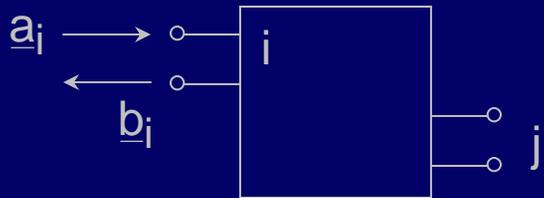

$$\text{Net power entering port "i"} = |a_i|^2 - |b_i|^2$$

$$\text{Scattering matrix equation: } \underline{\bar{b}} = \underline{\bar{S}} \underline{\bar{a}}$$

Note:

- 1) The scattering matrix $\underline{\bar{S}}$ is defined only when the n-port is imbedded in a network
- 2) The phases of a_i and b_i can be defined as some linear combinations of those for voltage and current

e.g. $\underline{a}_i = \underline{V}_+ \sqrt{Y_o/2} = (\underline{V} + Z_o I) / \sqrt{8Z_o}$, $\underline{b}_i = (\underline{V} - Z_o I) / \sqrt{8Z_o}$

Gain definition for N-port networks

“Transducer gain”

$$G_{TKj} \triangleq \frac{|b_k|^2}{|a_j|^2} = |\underline{S}_{kj}|^2 = P_{Dk}/P_{Aj}$$

“Exchangeable gain” (~“available gain”)

$$G_{E_{kj}} \triangleq \frac{P_{E_k}}{P_{E_j}} = \frac{?}{|a_j|^2} \quad \text{Note: available power out} \geq |b_k|^2 \text{ due to possible port-k mismatch}$$

$$\text{i.e. fractional power absorbed (FPA)} = \frac{|a_k|^2 - |b_k|^2}{|a_k|^2} = 1 - |\underline{S}_{kk}|^2$$

But FPA = fractional power emitted, if reciprocity applies.

$$\text{Therefore available power from port K} = \frac{|b_k|^2}{(1 - |\underline{S}_{kk}|^2)}$$

$$\text{Therefore } G_{E_{kj}} = \frac{|b_k|^2}{(1 - |\underline{S}_{kk}|^2)} \Big/ |a_j|^2 = \frac{|\underline{S}_{kj}|^2}{1 - |\underline{S}_{kk}|^2} = G_{E_{kj}}$$


Constraints on N-port networks

Lossless passive networks $\Rightarrow \sum_{i=1}^N |\underline{a}_i|^2 = \sum_{i=1}^N |\underline{b}_i|^2$

Reciprocity $\Rightarrow \bar{\underline{S}} = \bar{\underline{S}}^t$

Example of constrained N-port networks

Does an ideal power combiner exist?

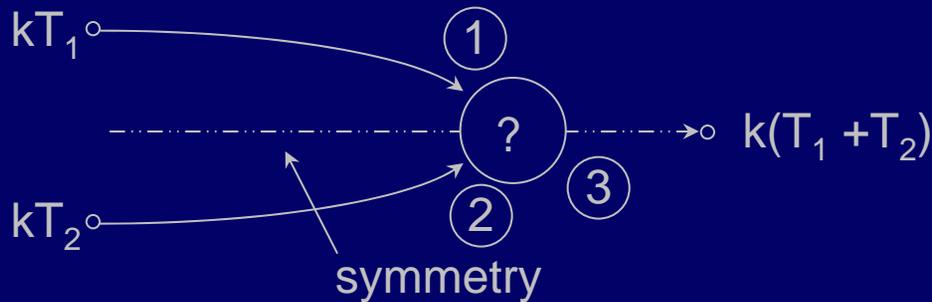

We want $\underline{\underline{S}} = \begin{bmatrix} 0 & 0 & \underline{\alpha} \\ 0 & 0 & \underline{\alpha} \\ \underline{\alpha} & \underline{\alpha} & \underline{\beta} \end{bmatrix}$

Losslessness $\Rightarrow \underline{\underline{a}}^{t*} \bullet \underline{\underline{a}} = \underline{\underline{b}}^{t*} \bullet \underline{\underline{b}}$

$$\underline{\underline{b}}^{t*} \bullet \underline{\underline{b}} = (\underline{\underline{S}}\underline{\underline{a}})^{t*} \bullet (\underline{\underline{S}} \bullet \underline{\underline{a}}) = \underline{\underline{a}}^{t*} \underline{\underline{S}}^{t*} \underline{\underline{S}}\underline{\underline{a}}$$

Therefore $\underline{\underline{S}}^{t*} \underline{\underline{S}} = \underline{\underline{I}} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$; if the combiner is lossless

Example of constrained N-port networks

Therefore $\underline{\underline{S}}^{t*} \underline{\underline{S}} = \underline{\underline{I}} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$; if the container is lossless

$$\text{Test: } \underline{\underline{S}}^{t*} \underline{\underline{S}} = \begin{bmatrix} |\underline{\alpha}|^2 & |\underline{\alpha}|^2 & \underline{\alpha}^* \underline{\beta} \\ |\underline{\alpha}|^2 & |\underline{\alpha}|^2 & \underline{\alpha}^* \underline{\beta} \\ \underline{\alpha} \underline{\beta}^* & \underline{\alpha} \underline{\beta}^* & 2|\underline{\alpha}|^2 + |\underline{\beta}|^2 \end{bmatrix} \quad \underline{\underline{S}} = \begin{bmatrix} 0 & 0 & \underline{\alpha} \\ 0 & 0 & \underline{\alpha} \\ \underline{\alpha} & \underline{\alpha} & \underline{\beta} \end{bmatrix}$$


If $|\underline{\alpha}|^2 = 1$, then $2|\underline{\alpha}|^2 + |\underline{\beta}|^2 \neq 1$

Therefore constraints (8-14) and (8-15) cannot be satisfied simultaneously for this system

Ideal matched 2-input-port combiners are impossible

Another N-port network example

Can we match all 3 ports simultaneously?

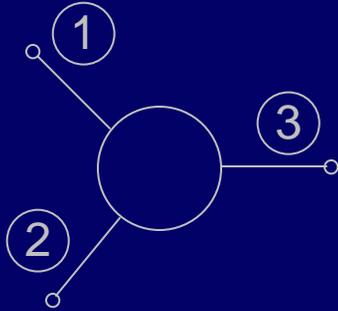

(Note: $\underline{\underline{S}}$ is defined only when imbedded in network)

For 3 matched ports:

$$\underline{\underline{S}} = \begin{bmatrix} 0 & \underline{\alpha} & \underline{\beta} \\ \underline{\alpha} & 0 & \underline{\gamma} \\ \underline{\beta} & \underline{\gamma} & 0 \end{bmatrix}$$

Does $\underline{\underline{S}}^t \underline{\underline{S}} = \underline{\underline{I}}$? (lossless passive constraint)

Matched 3-port example

For 3 matched ports:

$$\underline{\underline{S}} = \begin{bmatrix} 0 & \underline{\alpha} & \underline{\beta} \\ \underline{\alpha} & 0 & \underline{\gamma} \\ \underline{\beta} & \underline{\gamma} & 0 \end{bmatrix}$$

Does $\underline{\underline{S}}^{t*} \underline{\underline{S}} = \underline{\underline{I}}$? (lossless passive constraint)


$$\underline{\underline{S}}^{t*} \underline{\underline{S}} = \begin{bmatrix} |\underline{\alpha}|^2 + |\underline{\beta}|^2 & \underline{\beta}^* \underline{\gamma} & \underline{\alpha}^* \underline{\gamma} \\ \underline{\beta} \underline{\gamma}^* & |\underline{\alpha}|^2 + |\underline{\gamma}|^2 & \underline{\alpha}^* \underline{\beta} \\ \underline{\alpha} \underline{\gamma}^* & \underline{\alpha} \underline{\beta}^* & |\underline{\beta}|^2 + |\underline{\gamma}|^2 \end{bmatrix} \stackrel{?}{=} \underline{\underline{I}}$$

If $\underline{\beta}^* \underline{\gamma} = \underline{\alpha}^* \underline{\gamma} = \underline{\alpha}^* \underline{\beta} = 0$, then 2 of (α, β, γ) and at least one diagonal element of $\underline{\underline{S}}^{t*} \underline{\underline{S}} = 0$

Therefore not possible to match all 3 ports simultaneously


Lossless passive reciprocal symmetric 4-port network

Ports 1, 2 are isolated; also 3, 4

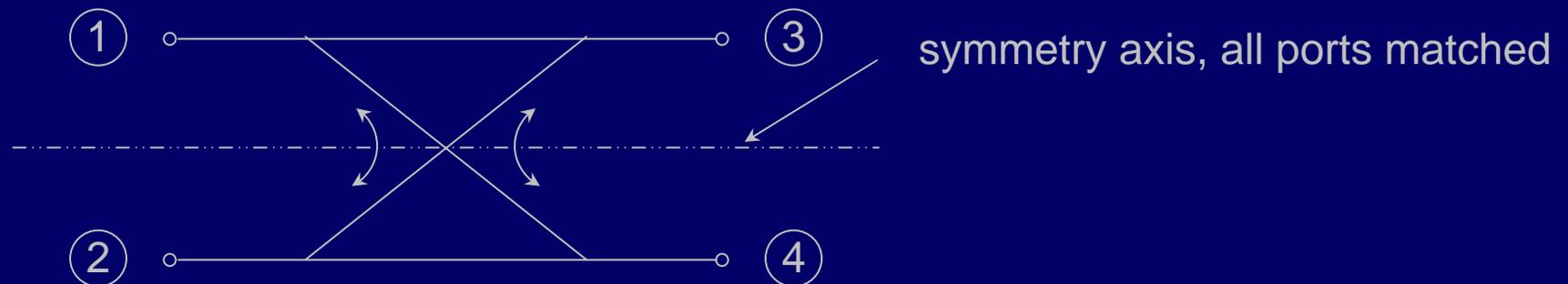

We can show $\Delta\phi$ for $\textcircled{1} \rightarrow \textcircled{3}$ versus $\textcircled{1} \rightarrow \textcircled{4}$ paths is unique using losslessness, reciprocity, and symmetry

Mixer

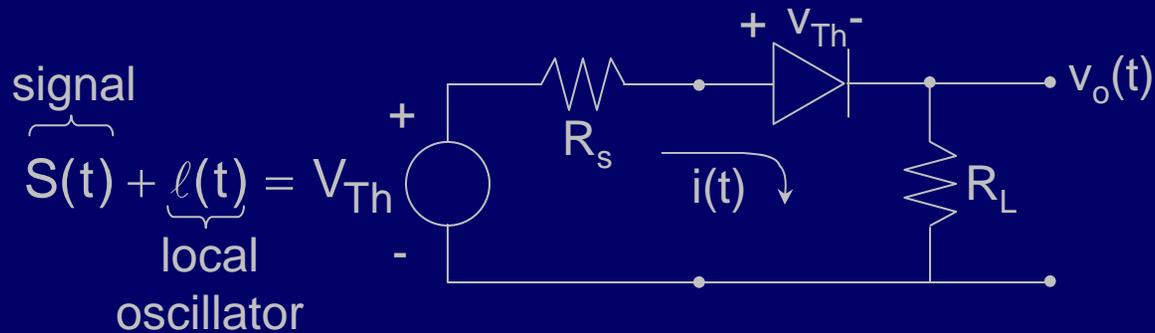


$$v_d(t) \cong v_l \sin \omega_0 t + v_s \sin \omega_s t$$

+ small high - order terms

$$v_o(t) = i R_L \left(\propto v_{Th}^2 R_L \right)$$

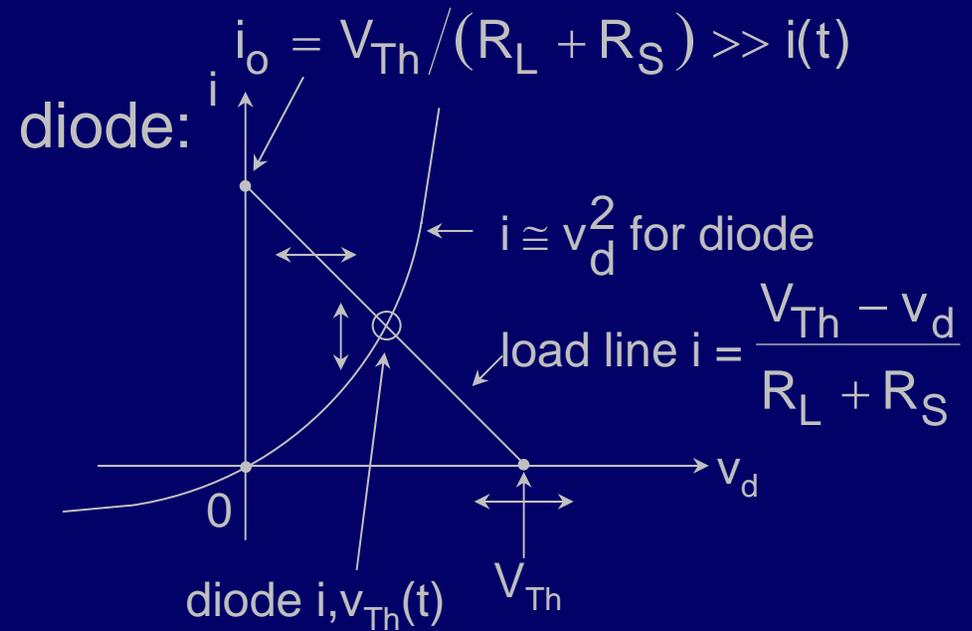
$$= k_0 + k_1 v_{Th} + \underbrace{k_2 v_{Th}^2}_{\text{dominant}} + k_3 v_{Th}^3 + \dots$$



Mixer

$$v_o(t) = iR_L = k_0 + k_1 v_{Th} + \underbrace{k_2 v_{Th}^2}_{\text{dominant}} + k_3 v_{Th}^3 + \dots \quad \left(\propto v_d^2 R_L \right)$$


Spectral content of detector output:

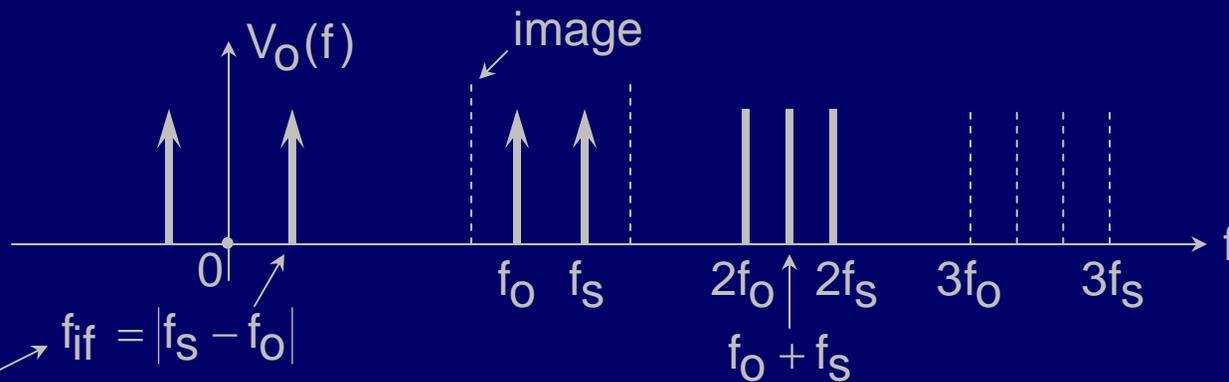

Pure product (frequency component for pure $s(t) \cdot l(t)$)

(Note: $v_d^4 \Rightarrow 2f_{i.f.}$, can be in i.f. passband)

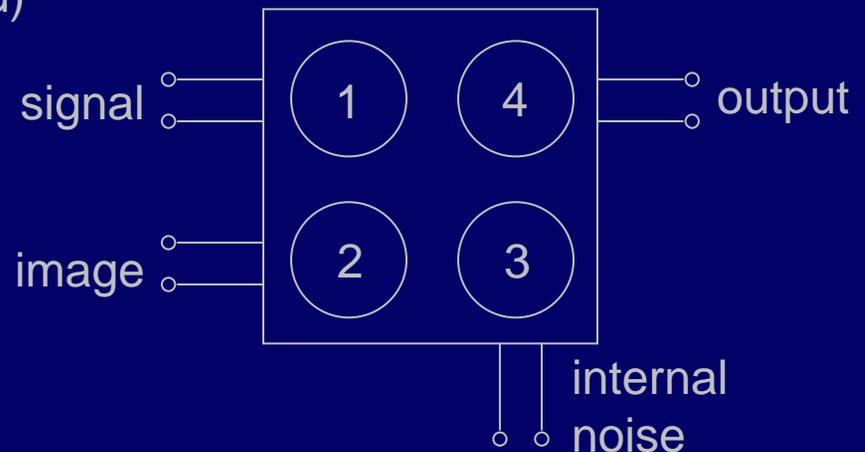
Normally:
a 4-port model suffices
to find F, T_{SSB}, T_R :



Mixer Noise Figure Using 4-port Model

$$T_R = T_{SSB} = (F - 1)T_o = T_o(L_{ct_r} - 1)$$

for single sideband (SSB) operation

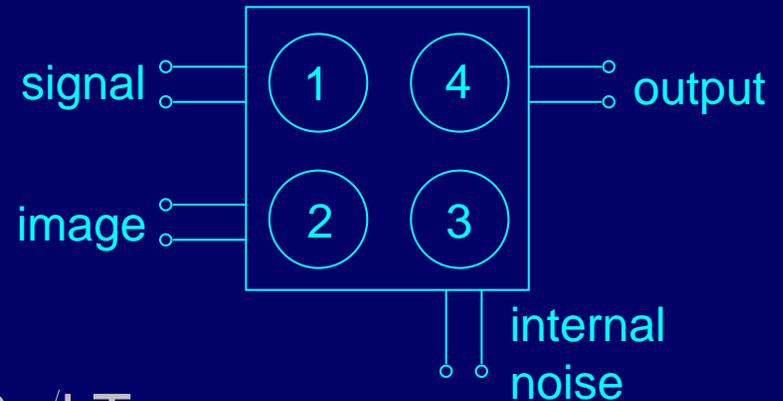

$$F_{SSB} = \frac{S_1/N_1}{S_4/N_4} = \frac{S_1/kT_o}{\left[\frac{S_1|S_{41}|^2}{1-|S_{44}|^2} \right] / \left[\frac{kT_o|S_{41}|^2 + kT_2|S_{42}|^2 + kT_3|S_{43}|^2}{1-|S_{44}|^2} \right]}$$


[Note: "S", signifies signal in port 1, S_{kj} is a scattering matrix element]

$$\text{Simplifying, } F_{SSB} = 1 + \frac{T_2 |S_{42}|^2}{T_o |S_{41}|^2} + \frac{T_3 |S_{43}|^2}{T_o |S_{41}|^2} = 1 + \frac{T_{SSB}}{T_o}$$

$$\text{Therefore } T_{SSB} = T_2 \frac{|S_{42}|^2}{|S_{41}|^2} + T_3 \frac{|S_{43}|^2}{|S_{41}|^2}$$

Double-sideband Receiver

Therefore $T_{SSB} = T_2 \frac{|S_{42}|^2}{|S_{41}|^2} + T_3 \frac{|S_{43}|^2}{|S_{41}|^2}$

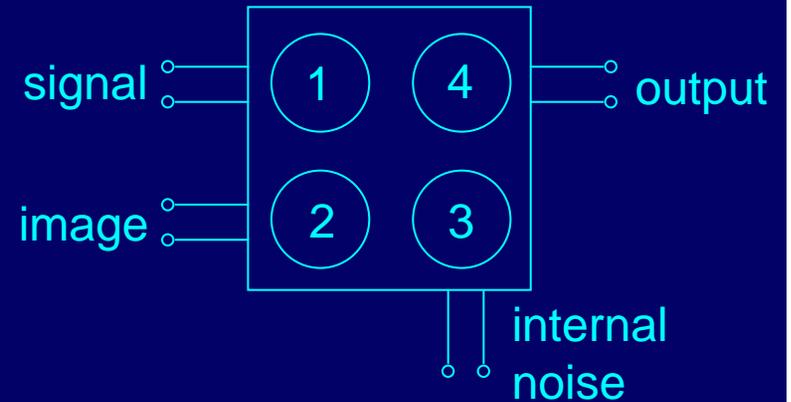

Both ports 1 and 2 are signal, so

$$S_4 = kT_o \left(|S_{41}|^2 + |S_{42}|^2 \right) / \left(1 - |S_{44}|^2 \right)$$


It follows that

$$T_{DSB} = T_3 |S_{43}|^2 / \left[|S_{41}|^2 + |S_{42}|^2 \right]$$

Often suggested: $F_{SSB} \cong 2F_{DSB}$

Double-sideband Receiver

Therefore $T_{SSB} = T_2 \frac{|S_{42}|^2}{|S_{41}|^2} + T_3 \frac{|S_{43}|^2}{|S_{41}|^2}$

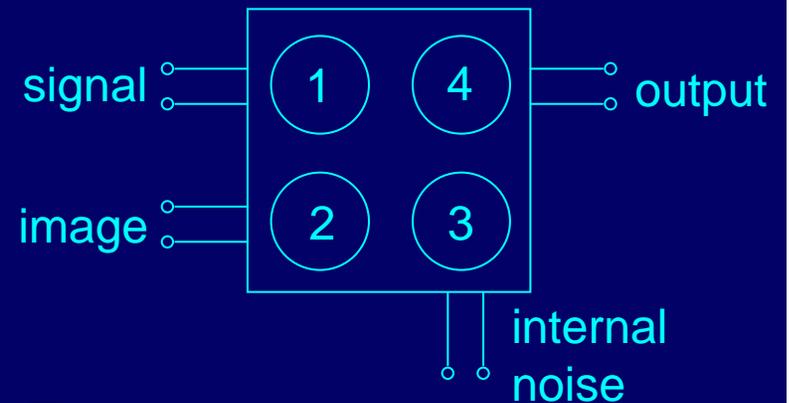

Often suggested: $F_{SSB} \cong 2F_{DSB}$

Let $|S_{41}|^2 = |S_{42}|^2$ and $T_0 = T_1 = T_2$; then

$$F_{DSB} = 1 + \frac{T_{DSB}}{T_0} = 1 + \frac{1}{2} \frac{T_3 |S_{43}|^2}{T_0 |S_{41}|^2}$$

$$F_{SSB} = 1 + \frac{T_{SSB}}{T_0} = 2 + \frac{T_3 |S_{43}|^2}{T_0 |S_{41}|^2} = 2F_{DSB}$$