

MIT OpenCourseWare  
<http://ocw.mit.edu>

2.004 Dynamics and Control II  
Spring 2008

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.

## Lecture 5<sup>1</sup>


### Reading:

- Class Handout: *Modeling Part 1: Energy and Power Flow in Linear Systems*  
Sec. 1 (Introduction)  
Sec. 4 (Electrical System Elements)
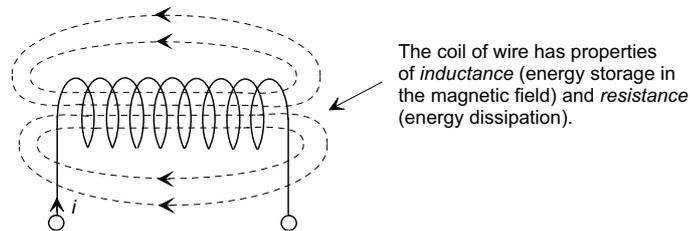
## 1 Modeling of Physical Systems

We will develop a unified modeling method that will allow the generation of a transfer function in several energy domains. The method is based on an extension of *impedance* concepts used in electrical systems. For that reason we will start with electrical systems.

*Lumped parameter modeling* involves approximating physical elements (where the parameters may be distributed in space) with discrete elements that are assumed to be concentrated at points (or “lumped”) in space. For example, a real electrical inductor is made from a coil of wire.



The coil has the primary property of electrical *inductance*, BUT it also has property of *resistance* associated with the wire - this resistance is distributed throughout the coil. In lumped parameter modeling we approximate the coil as having two elements - an inductance  $L$  and a lumped resistance  $R$ .

## 2 Modeling Electrical Systems

**Step 1: Identify the variables to be used.** We will concentrate on the use of *power variables*, that is a pair of variables whose product is power. In electrical systems:

$$P = vi$$


where  $P$  is power,  $v$  is the voltage drop (volts) across an element, and  $i$  is the current (amps) through an element. We therefore use  $v$  and  $i$  as our modeling variables.

---

<sup>1</sup>copyright © D.Rowell 2008

**Step 2: Identify the "primitive" lumped modeling elements.** In each energy domain we will identify 3 elements, two elements that store energy, and an element that dissipates energy. In the electrical domain the energy storage elements are the *capacitor* and the *inductor*, and the dissipative element is the *resistor*.

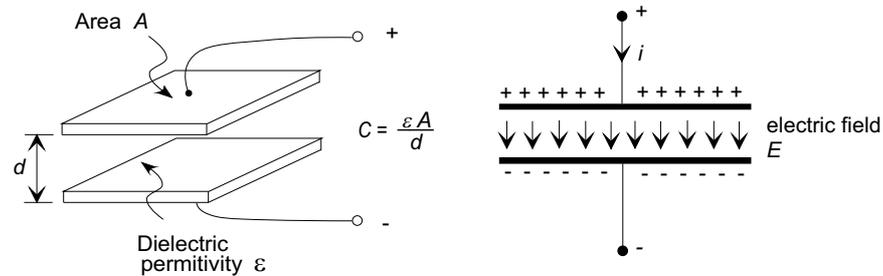**The Capacitor:** The capacitor stores energy in the electrostatic field between its "plates".



For a capacitor the current and voltage drop are related by

$$i = C \frac{dv}{dt}$$

where  $C$  is defined as the capacitance (Farad), or alternatively

$$v = \frac{1}{C} \int_0^t i dt + v(0)$$

Also, if we define charge as  $q = \int_0^t i dt$  then

$$v = \frac{1}{C} q$$

For a parallel plate capacitor, where the plates have area  $A$ , and are separated by a distance  $d$

$$C \propto \frac{A}{d} \implies C = \epsilon \frac{A}{d}$$

where  $\epsilon$  is defined to be the permittivity of the (non-conducting) dielectric material between the plates.

Note that power can flow in and out of a capacitor, since

$$P = vi = Cv \frac{dv}{dt}$$

and  $v$  and  $dv/dt$  may have same or opposite signs. The capacitor is therefore an energy storage element. The energy stored in a capacitor is

$$E_C(t) = \int_0^t P dt + E(0) = \frac{1}{2} C v^2.$$


Notes:

1) The Farad is a very large unit. Most practical capacitors are measured in units of


- microfarads ( $\mu F$ ) =  $10^{-6}F$ ,
- nanofarads (nF) =  $10^{-9}F$ , or
- picofarads (pF) =  $10^{-12}F$

2) A capacitor will not pass a dc current. Current only flows when the applied voltage is changing.

**The Inductor:**

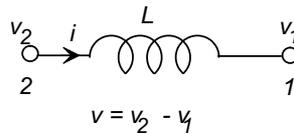

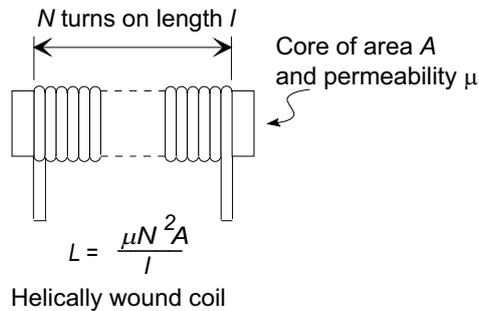Inductance is a property that represents energy stored in the electromagnetic field in a current carrying conductor. A practical inductor consists of a coil of wire



Lenz' Law relates the voltage across an inductor to the current flowing through it:

$$v = L \frac{di}{dt}$$

or

$$i = \frac{1}{L} \int_0^t v dt + i(0)$$

where  $L$  is the inductance, with units of the Henry. Power can flow in and out of an inductor since


$$P = vi = Li \frac{di}{dt},$$

and  $i$  and  $di/dt$  may have the same or opposite signs. The stored energy is

$$E = \int_0^t P dt + E(0) = \frac{1}{2} Li^2$$


Notes:

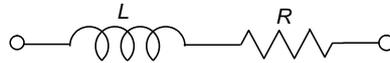- 1) The Henry is a very large unit. Practical inductors have values in
  - millihenrys (mH) -  $10^{-3}\text{H}$
  - microhenrys ( $\mu\text{H}$ ) -  $10^{-6}\text{H}$
- 2) Notice that a pure inductance will have  $v = 0$  if  $\frac{di}{dt} = 0$  (a dc current)
- 3) Practical inductors are wound with (copper) wire and will have a finite resistance  $R$ . The lumped model including both phenomena is



The relative importance of the resistance is dependent on the operating conditions.

**The Resistor:**

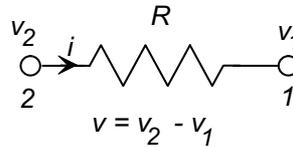

The current and voltage in a resistor are governed by Ohm's law:


$$V = iR \quad \text{or} \quad i = \frac{1}{R}v$$

Resistance is a dissipative property since  $v$  and  $i$  always have the same sign, and the power is always positive

$$P = i^2R = v^2/R > 0$$

Energy always flows into a resistor, and cannot be recovered.

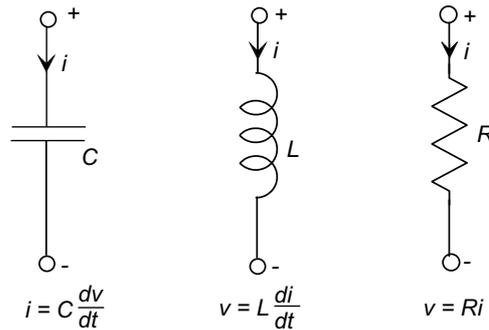
**Summary:** In modeling electrical systems we use three passive modeling elements:




The capacitor and inductor are energy storage elements in that power can flow into the element, and recovered. The resistor is a dissipative element because the voltage and current are algebraically related and power always flows *into* the element.

**Sources:** In addition to the three passive elements we will use two ideal electrical power sources:


## The Voltage Source:

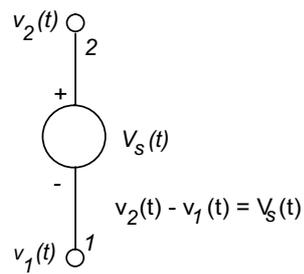

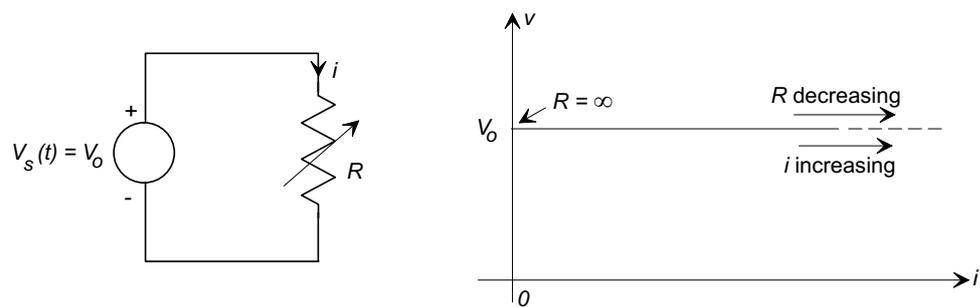A voltage source will *maintain the voltage at its terminals* regardless of the current it must supply to the connected load.



## The Current Source:

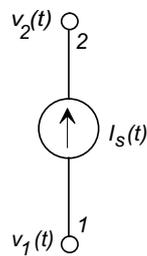

A current source will *maintain the current supplied to the attached circuit* regardless of the voltage at it must generate to do so.

