

MIT OpenCourseWare  
<http://ocw.mit.edu>

2.004 Dynamics and Control II  
Spring 2008

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.

## Lecture 6<sup>1</sup>

### Reading:

- Nise: Sec. 2.4 (pages 45–55)
- Class Handout: *Modeling Part 1: Energy and Power Flow in Linear Systems*  
Sec. 1 (Introduction)  
Sec. 4 (Electrical System Elements)


## 1 Modeling Electrical Systems (continued)

In Lecture 5 we examined the primitive electrical elements (capacitors inductors and resistors), and sources (voltage source and current source). We now look at how these elements behave when connected together in a circuit.

### Interconnection Laws:

(a) **Kirchoff's Current Law (KCL):** The sum of currents flowing *into*(or out of) a junction is zero. In the figure below, at the circled junction we sum the currents into the junction to find

$$i_1 - i_2 - i_3 = 0$$

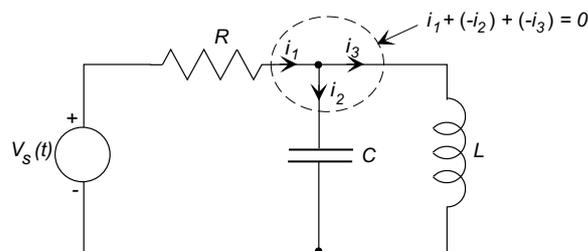


We will define a junction as a *node*, and if there are  $n$  circuit branches attached to a node

$$\sum_{i=1}^n i_n = 0$$

where we define the convention that positive current flow is into the node.

---

<sup>1</sup>copyright © D.Rowell 2008

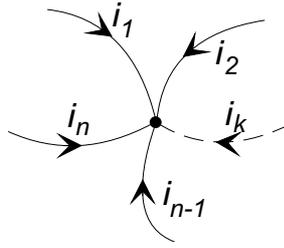


**Kirchoff's Voltage Law (KVL):** The sum of voltage *drops* around any closed loop in a circuit is zero. The assumed sign convention for the voltage drop on each element must be defined. Two clockwise loops are shown in the figure below. For loop (1)

$$v_R + v_C - V_s(t),$$

while for loop (2)

$$v_L - v_C(t) = 0.$$

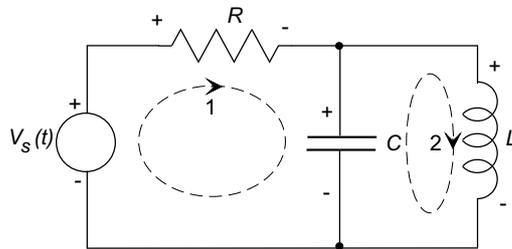


Loop 1:  $v_R + v_C - V_s = 0$

Loop 2:  $v_L - v_C = 0$

Note: The + and - on the diagram shows the direction of the assumed voltage drop.

**Electrical Impedance:**

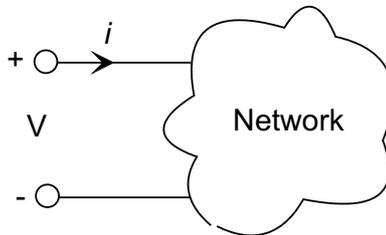

Define the *impedance* of an element or passive circuit as a *transfer function* relating current  $I(s)$  to voltage  $V(s)$  at its terminals:


$$Z(s) = \frac{V(s)}{I(s)}$$

In addition we can define the *admittance*  $Y(s)$  as the reciprocal of the impedance:

$$Y(s) = \frac{1}{Z(s)} = \frac{I(s)}{V(s)}$$

**The Impedance of Passive Electrical Elements**

(a) **The Capacitor:**

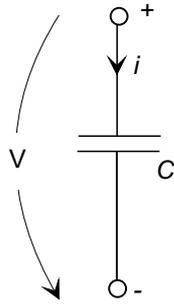

For the capacitor

$$i = C \frac{dv}{dt}.$$


Taking the Laplace Transform:

$$I(s) = CsV(s)$$

$$Z_C(s) = \frac{V(s)}{I(s)} = \frac{1}{sC}$$

or the admittance  $Y_C(s) = sC$ .

(b) **The Inductor:**

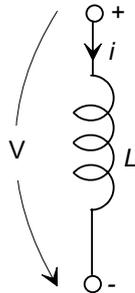

For the inductor

$$v = L \frac{di}{dt}.$$

Taking the Laplace Transform:

$$V(s) = LsI(s)$$

$$Z_L(s) = \frac{V(s)}{I(s)} = sL$$

or the admittance  $Y_L(s) = 1/sL$ .

(c) **The Resistor:**



For the resistor

$$v = Ri.$$


Taking the Laplace transform

$$V(s) = RI(s)$$

$$Z_R(s) = \frac{V(s)}{I(s)} = R$$

or the admittance  $Y_R = 1/R$ .

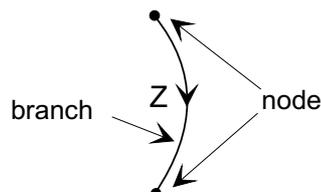
**Impedance Nomenclature:** We now introduce a graphical representation that will be used to denote systems in many energy domains.



The impedance is drawn as a graph *branch* between two *nodes*. Nodes represent junctions between the elements in the circuit. The arrow on the branch indicates both the assumed direction of voltage drop across the element, and the assumed current direction.
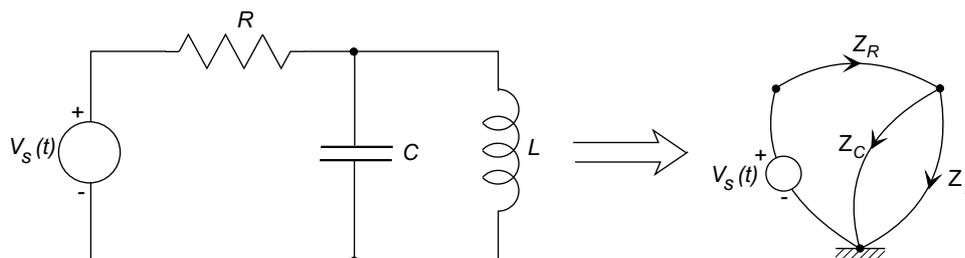
### ■ Example 1


The electrical circuit, consisting of a capacitor  $C$ , an inductor  $L$ , and a resistor  $R$  is shown below:



The impedance graph is shown on the right. The nodes on the graph represent *points of distinct voltage* in the circuit.

### Impedance Connection Rules

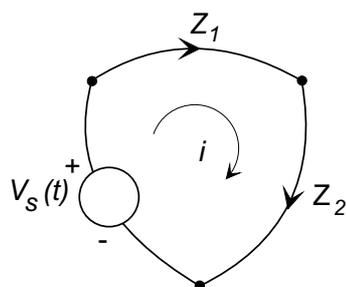- (a) **Series connection:** Two or more elements are defined to be connected in series *if they share a common current*. For the two elements  $Z_1$  and  $Z_2$  in series below:  
Using KCL at the junction between  $Z_1$  and  $Z_2$ :



$$i_{Z_1} = i_{Z_2} = i$$

Using KVL around the loop:  $v_{Z_1} + v_{Z_2} - V_s = 0$

$$V_s = iZ_1 + iZ_2$$


$$Z_{eq} = \frac{V(s)}{I(s)} = Z_1 + Z_2$$

In general with  $n$  impedances  $Z_i$  ( $i = 1, \dots, n$ ) in series:

$$Z_{eq} = \sum_{i=1}^n Z_i$$

## ■ Example 2

For the tree elements in series below:

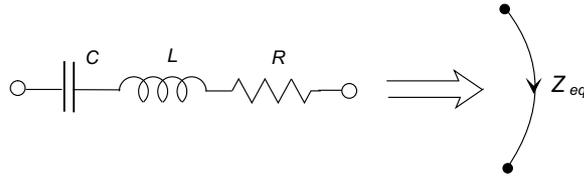

$$Z_{eq} = Z_C + Z_L + Z_R = \frac{1}{sC} + sL + R$$


or expressing the impedance as a transfer function (a ratio of polynomials):

$$Z_{eq} = \frac{V(s)}{I(s)} = \frac{LCs^2 + RCs + 1}{Cs}$$

**(b) Parallel connection:** Two or more elements are defined to be connected in parallel if they *share a common voltage*. For the two elements  $Z_1$  and  $Z_2$  in parallel below:

Using KVL:

$$v_{Z_1} = v_{Z_2} = V_s$$

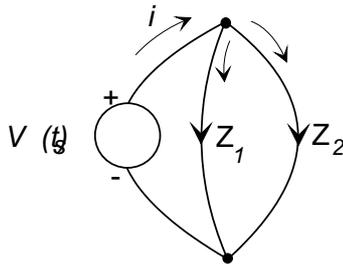

Using KCL at the node:

$$i_s = i_{Z_1} + i_{Z_2}$$

$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{i_{Z_1} + i_{Z_2}}{V}$$

$$\boxed{\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}}$$

In general for  $n$  impedances  $Z_i$  ( $i = 1, \dots, n$ ) in parallel, the equivalent impedance is:

$$\boxed{\frac{1}{Z_{eq}} = \sum_{i=1}^n \frac{1}{Z_i}}$$

Alternatively, using admittances  $Y = 1/Z$

$$y_{eq} = \frac{1}{Z_{eq}} = \sum_{i=1}^n Y_i.$$

**Note:** For  $N = 2$  we can write


$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{Z_1 + Z_2}{Z_1 Z_2}$$

which leads to the very common representation

$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$
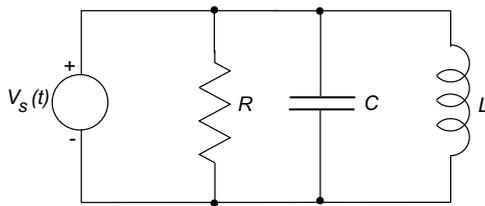
### ■ Example 3

Find the impedance of a capacitor  $C$ , and inductor  $L$  and a resistor  $R$  connected in parallel:




$$\begin{aligned} \frac{1}{Z} &= \frac{1}{1/sC} + \frac{1}{sL} + \frac{1}{R} \\ &= sC + \frac{1}{sL} + \frac{1}{R} \\ &= \frac{LCRs^2 + Ls + R}{RLs} \end{aligned}$$

$$Z = \frac{V(s)}{I(s)} = \frac{RLs}{LCRs^2 + Ls + R}$$
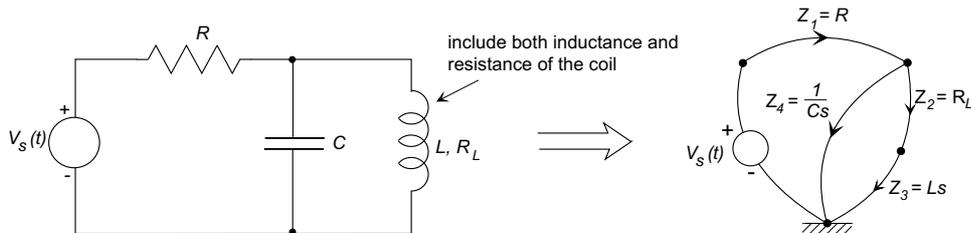
### ■ Example 4


Find the impedance of the following circuit, assuming we should include resistance and inductance of the coil:



$$\begin{aligned} Z &= Z_1 + Z_4 \parallel (Z_2 + Z_3) \\ &= Z_1 + \frac{Z_4(Z_2 + Z_3)}{Z_4 + Z_2 + Z_3} \\ &= R + \frac{(1/sC)(R_L + Ls)}{1/sC + R_L + Ls} \\ &= R + \frac{R_L + Ls}{LCs^2 + R_LCs + 1} \end{aligned}$$

$$Z = \frac{V(s)}{I(s)} = \frac{RLCs^2 + (RR_L C + L)s + (R + R_L)}{LCs^2 + R_L Cs + 1}$$

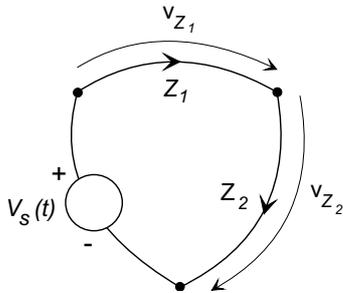**The Voltage Divider:** Consider two impedances in series with voltage  $V$  across them:



and

$$I(s) = \frac{V(s)}{(Z_1 + Z_2)}$$

$$V_{Z_2}(s) = I(s)Z_2 = V_{Z_2}(s) = \frac{Z_2}{Z_1 + Z_2}V(s).$$


Similarly

$$V_{Z_1}(s) = \frac{Z_1}{Z_1 + Z_2}V(s).$$

The voltage divider relationship may be used to find the transfer function of many simple systems.
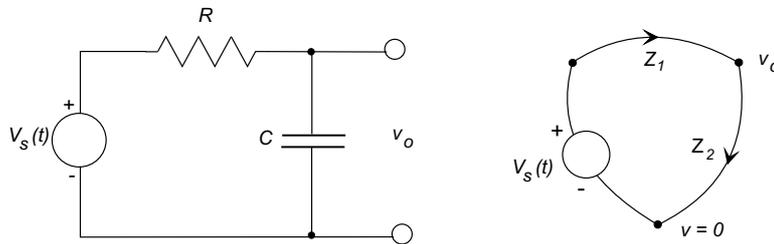
### ■ Example 5

Find the transfer function relating  $V_0$  to  $V_s$  in the following circuit




Use the voltage divider relationship

$$V_0 = \frac{Z_2}{Z_1 + Z_2}V_s = \frac{1/sC}{R + 1/sC}V_s$$


$$H(s) = \frac{V_0(s)}{V(s)} = \frac{1}{RCs + 1}$$
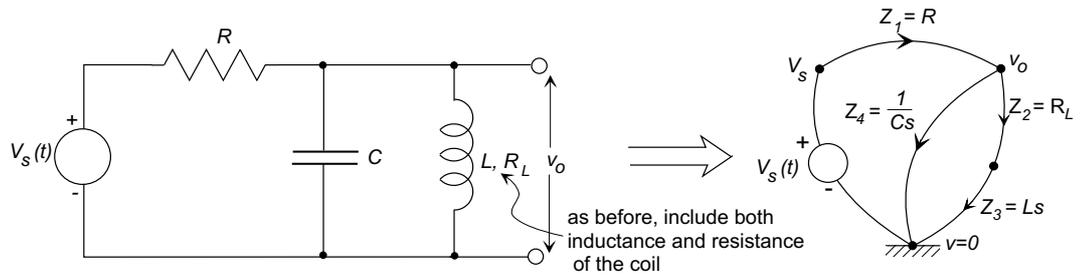
### ■ Example 6

Find the transfer function relating  $V_0$  to  $V_s$  in the following circuit:



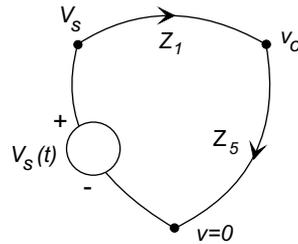Reduce the impedance graph to a series connection of two elements



$$V_0 = \frac{Z_5}{Z_1 + Z_5} V_s$$

where


$$\begin{aligned} Z_5 &= Z_4 \parallel (Z_2 + Z_3) = \frac{Z_4(Z_2 + Z_3)}{Z_4 + Z_2 + Z_3} \\ &= \frac{(1/sC)(R_L + Ls)}{1/sC + R_L + Ls} \end{aligned}$$

Using the voltage divider relationship, the transfer function is

$$H(s) = \frac{V_0(s)}{V_s(s)} = \frac{Z_5}{Z_1 + Z_5} = \frac{\frac{R_L + Ls}{LCs^2 + R_LCs + 1}}{R_1 + \frac{R_L + Ls}{LCs^2 + R_LCs + 1}}$$

$$H(s) = \frac{R_L + Ls}{R_1LCs^2 + (R_1R_LC + L)s + (R_1 + R_L)}$$

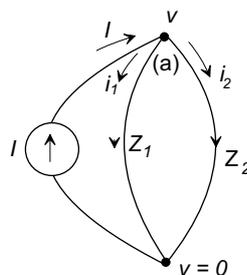**The Current Divider:** Consider two impedances in parallel:



Using KCL at the top node (a),

$$I - i_1 - i_2 = 0 \quad \text{or} \quad i_1 + i_2 = I$$

But  $i_1 = V/Z_1$ , and  $i_2 = V/Z_2$  so that

$$\frac{V}{Z_1} + \frac{V}{Z_2} = I \quad \text{or} \quad V = \frac{1}{1/Z_1 + 1/Z_2} I$$

$$i_1 = \frac{V}{Z_1} = \frac{1/Z_1}{(1/Z_1 + 1/Z_2)} I = \frac{Y_1}{Y_1 + Y_2} I$$

Similarly

$$i_2 = \frac{Y_2}{Y_1 + Y_2} I.$$


The current divider may be used to find transfer functions for some simple circuits.

### ■ Example 7


Find the transfer function

$$H(s) = \frac{V_o(s)}{I(s)}$$

in the following circuit:

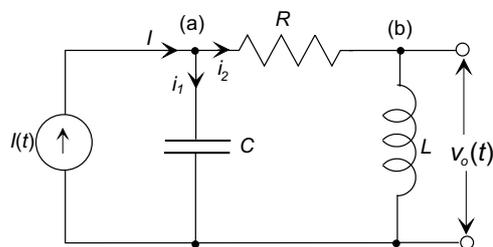

Draw the system as an impedance graph:

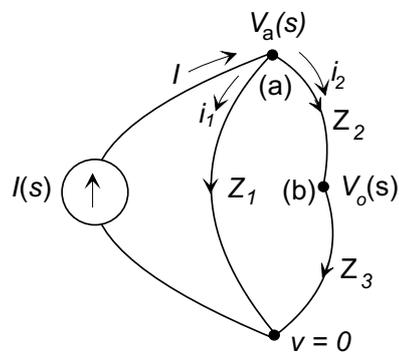

Let  $Z_1 = 1/sC$ ,  $Z_2 = R$ , and  $Z_3 = sL$ . We will use  $V_o(s) = I_2(s)Z_3$  (at node (b)), and find  $I_2(s)$  from the current division at node (a):

$$\begin{aligned} I_2(s) &= \frac{\frac{1}{Z_2+Z_3}}{\frac{1}{Z_1} + \frac{1}{Z_2+Z_3}} I(s) = \frac{1}{(1/Z_1)(Z_2 + Z_3) + 1} I(s) \\ &= \frac{1}{Cs(R + Ls) + 1} I(s) = \frac{1}{LCs^2 + RCs + 1} I(s) \end{aligned}$$

$$V_o(s) = I_2(s)Ls = \frac{Ls}{LCs^2 + RCs + 1} I(s)$$

or

$$\boxed{H(s) = \frac{V_o(s)}{I(s)} = \frac{Ls}{LCs^2 + RCs + 1}}$$

---