

MIT OpenCourseWare  
<http://ocw.mit.edu>


2.004 Dynamics and Control II  
Spring 2008

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.


Lecture 8<sup>1</sup>

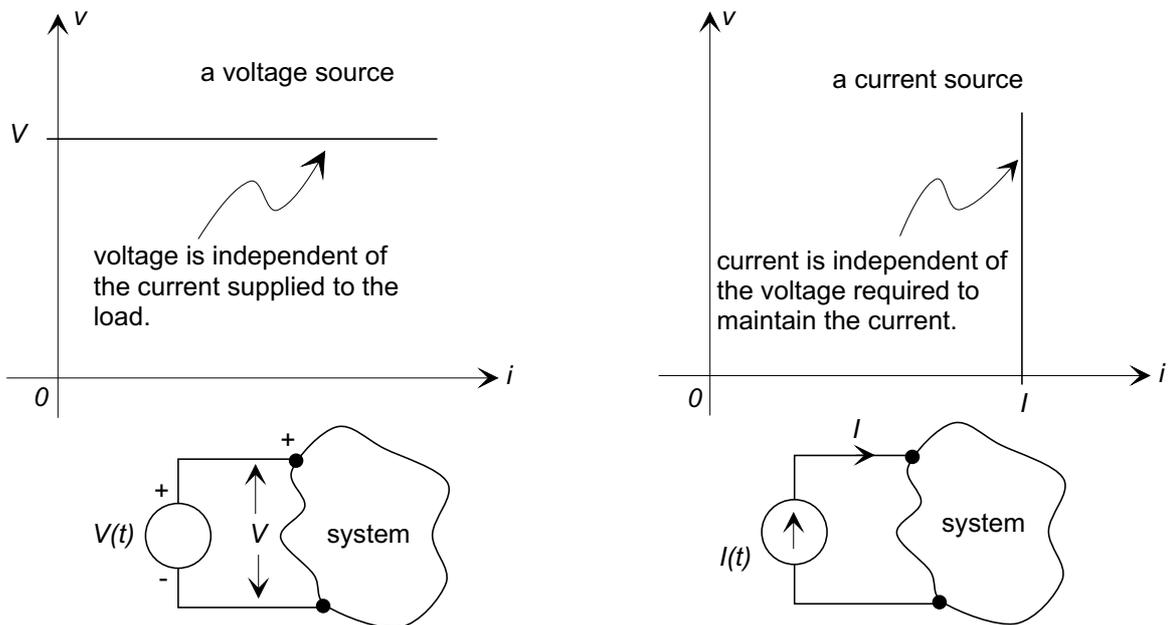**1 Electrical System Modeling (continued)**

**Modeling Real Sources:** Up to this point we have considered only *ideal* voltage and current sources:




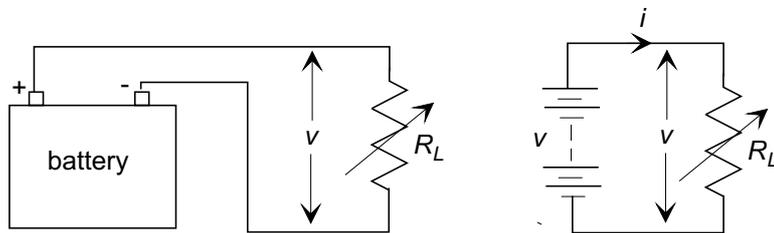However, practical (real) sources do not have an ideal characteristic – they are power limited. For example we may think of a battery as an ideal voltage source - say with a 9 volt output, but if we were to measure the terminal voltage under increasing load currents



we would find that at high currents the voltage decreases in a nonlinear manner:

<sup>1</sup>copyright © D.Rowell 2008

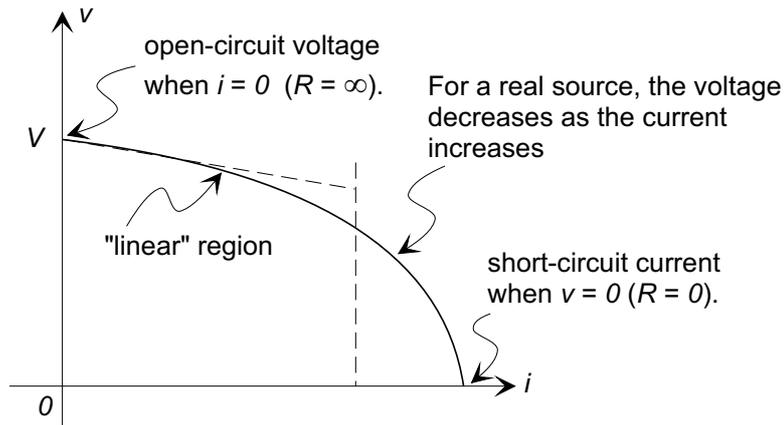


The voltage–current relationship is determined by the electrochemical reaction within the battery. It may be possible to define a region of operation at low currents in which there is an approximately linear relationship between voltage and current

$$v(i) \approx v_{oc} - R_s i$$


where  $v_{oc}$  is the open-circuit voltage (when  $i = 0$ ), and  $R_o$  is a resistance.

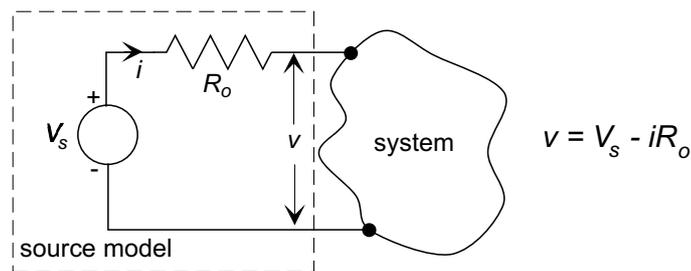How can we model this linear part of the characteristic?



One way to do this is to model the real source(the battery) as an ideal voltage source  $V_s$  in series with a resistor  $R_o$  (the value of which is found experimentally). The voltage drop  $v_{R_o} = iR_o$  across the resistor accounts for the “droop” in the source characteristic.

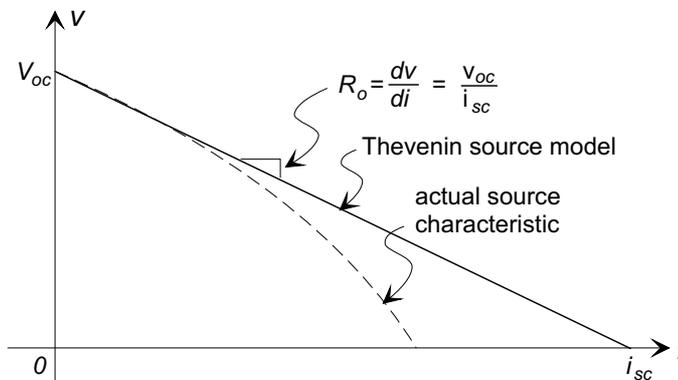This is known as the *Thévenin equivalent source model*.




Note that

- (1) The open-circuit ( $i = 0$ ) voltage is  $V_s$ .
- (2) The short-circuit ( $v = 0$ ) current is  $i_{sc} = V_s/R$ .
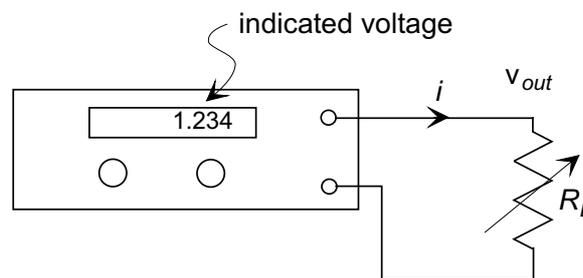
### ■ Example 1


Electronic instruments are often designed to have a specific output impedance (resistance)  $R_o$ . For example when the Tektronix function generator in the 2.004 laboratory is connected to an arbitrary load resistance  $R_L$  the measured output voltage  $v_{out}$  will not necessarily be equal to the value set on the front panel:



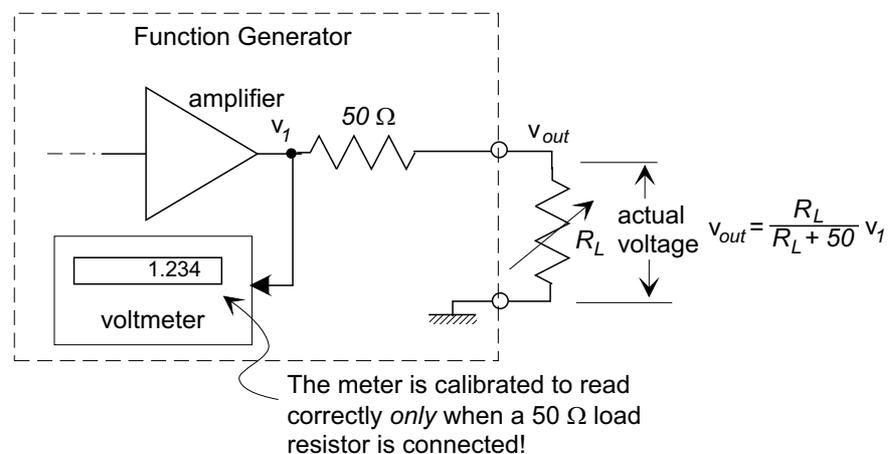- (a) If  $R_L = \infty$  (no load connected) the true voltage at the terminals is twice the indicated value.
- (b) If  $R_L = 0$  (short circuit) the actual voltage is zero but the indicated voltage is unchanged.
- (c) If  $R_L = 50 \Omega$  the indicated and measured output voltages are the same.

Why?


**Answer:** The function generator is specified as having an output impedance of  $50\Omega$ . In fact, if you look at the circuit schematic, you will find that there is a  $50\Omega$  resistor in series with the output terminal:




In the lab we have  $50\Omega$  terminator resistors connected across the output terminals so that the voltage reads correctly.

---

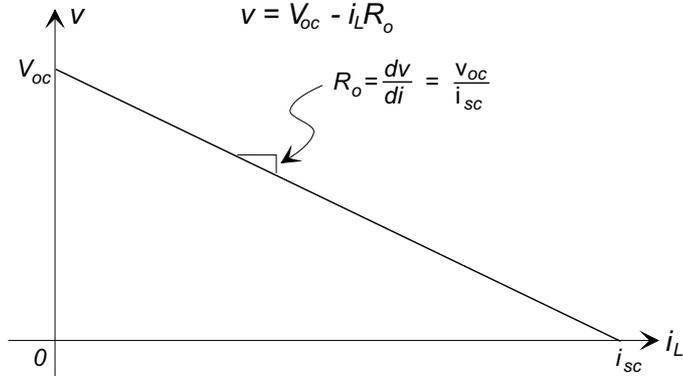A second approach to modeling the real source characteristic



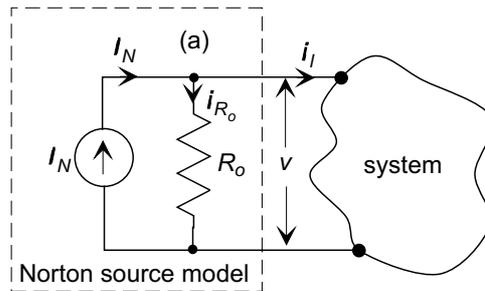is to use a current source  $I_N$  in parallel with the resistor  $R_o$



This is known as the *Norton equivalent source model*.

If no load resistor is connected (open-circuit)

$$v_{os} = I_N R_o.$$

The short-circuit current is

$$i_{sc} = I_N.$$

If the load is a resistor  $R_L$

$$v = \frac{R_L R_o}{R_L + R_o} = \frac{R_L}{R_L + R_o} v_{oc} = \frac{v/i}{v_1 + R_o}$$


and rearranging

$$v = v_{oc} - i R_L.$$


The Norton and Thévenin source models are equivalent and cannot be distinguished by measurements at the terminals.
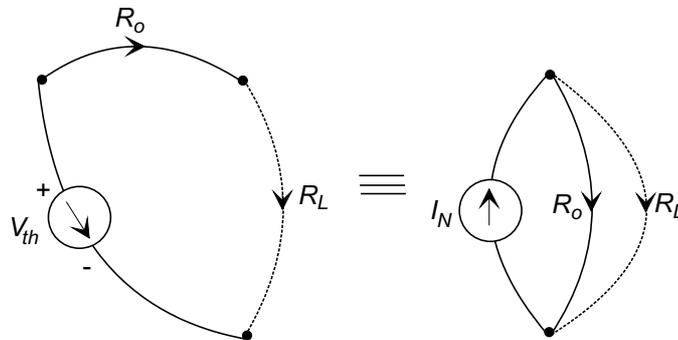
## ■ Example 2

Measurements on an industrial dc power supply showed it to have an open-circuit voltage of 200 v, but when 10 Ω resistor is connected, the voltage drops to 133v. Find Thévenin and Norton equivalent source models.



**Thévenin Model:**

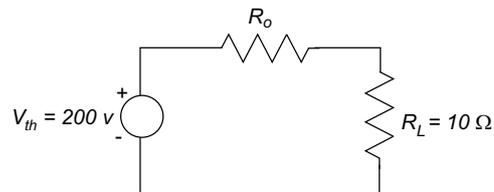

$$V_{th} = v_{oc} = 200 \text{ v.}$$


Using the voltage divider relationship

$$v_o = v_{R_L} = \frac{10}{10 + R_o} = 133 \text{ volts}$$

which gives

$$R_o = 5 \Omega.$$

The Thévenin model is:

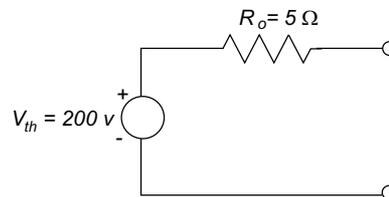

**Norton Model:** From above, the short-circuit current is

$$i_{sc} = \frac{V_{th}}{R_o} = \frac{200}{5} = 40 \text{ amps}$$

and the Norton model is:

