

8.022 Lecture Notes Class 37 - 11/22/2006

Complex impedance instead of diff eq!

Use fact that everything in RLC circuit has same frequency as driving frequency(?).

$$V(t) = \hat{V}e^{i\omega t} \quad I(t) = \hat{I}e^{i\omega t}$$

Inductor

$$V = L \frac{dI}{dt}$$

$$\frac{dI}{dt} = i\omega I$$

$$\frac{V}{I} = i\omega L = \chi_L \quad (\text{complex impedance of inductor})$$

Capacitor


$$\frac{dV}{dt} = \frac{dQ}{dtC} = \frac{I}{C}$$

$$i\omega V = \frac{I}{C}$$

complex impedance of capacitor

$$\frac{V}{I} = \frac{1}{i\omega C} = \chi_c$$

Resistor

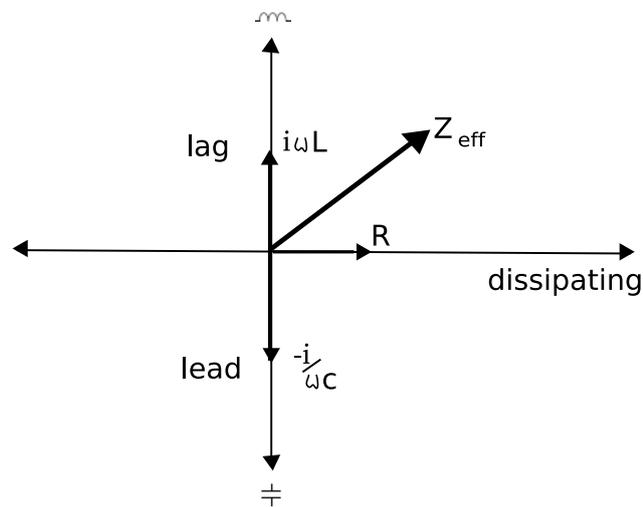

$$\frac{V}{I} = R$$


$$V = I \cdot z$$

$$\chi_L = i\omega L$$

$$\chi_C = \frac{1}{i\omega C}$$

$$\chi_R = R$$

RLC Circuit

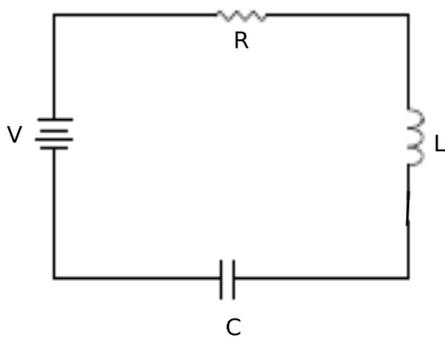

No derivatives any more! Can sum just like resistors in series.


$$\chi_{total} = \chi_R + \chi_C + \chi_L = R + i\omega L + \frac{1}{i\omega C}$$

$$\begin{aligned} I &= \frac{V}{\chi_{total}} \\ &= \frac{V}{R + i(\omega L - \frac{1}{\omega C})} \cdot \frac{R - i(\omega L - \frac{1}{\omega C})}{R - i(\omega L - \frac{1}{\omega C})} \\ &= \frac{V(R - i[\omega L - \frac{1}{\omega C}])}{R^2 + (\omega L - \frac{1}{\omega C})^2} \end{aligned}$$

$$\hat{I} = \frac{V}{[R^2 + (\omega L - \frac{1}{\omega C})^2]^{1/2}}$$

$$\tan \phi = \frac{\omega L - \frac{1}{\omega C}}{R}$$

Parallel RLC Circuit

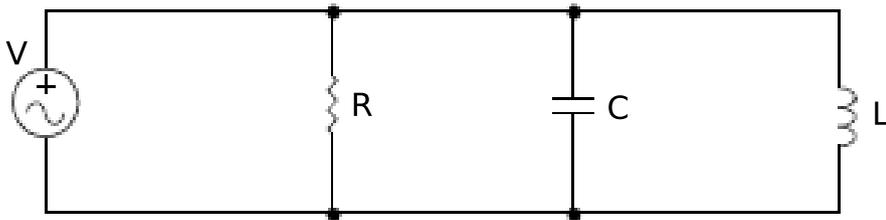

Let $Y = \frac{1}{Z}$, $I = V \cdot Y$

admittance current

$$Y_L = \frac{1}{i\omega L}$$

$$Y_C = i\omega C$$

$$Y_R = \frac{1}{R}$$

$$I = V\left(\frac{1}{R} + i\left(\omega C - \frac{1}{\omega L}\right)\right)$$



$$\hat{I} = V\left(\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2\right)^{1/2}$$

$$\tan \phi = \frac{R\omega C - \frac{R}{\omega L}}{R}$$

Large ω : $\frac{1}{L}$, $V\omega C$ is important.

Small ω : no C , $\frac{V}{\omega L}$ important.

Can we do equivalent of Thevenin's?

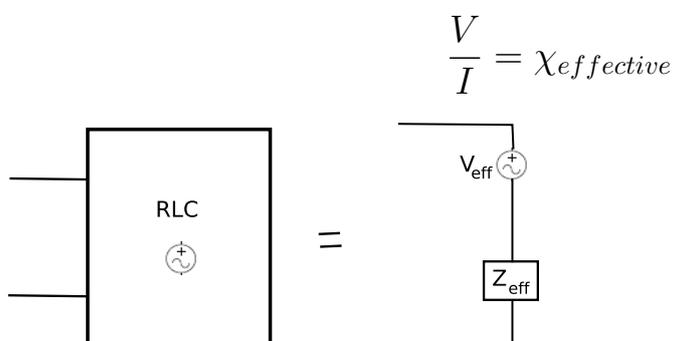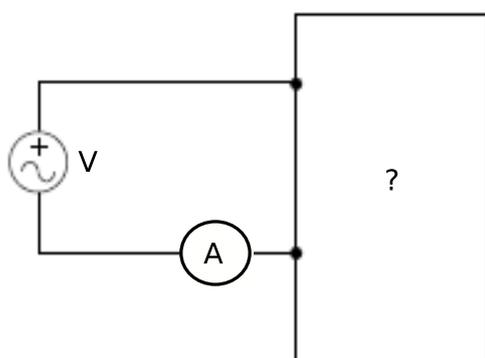

$$\frac{V}{I} = \chi_{effective}$$

$$z_{eff} = R_{eff} + i\chi_{eff}$$

First term decays, second term oscillates.

Power Dissipation

R does this! (LC circuit just oscillates, even w/o driver no loss of power).

$$\frac{dV}{dt} = RI^2 \quad (= VI)$$

$$z = R = i\chi$$


$$z = i\chi$$

$$V = i\chi I$$

$$\hat{V}e^{i\omega t} = \chi \hat{I}e^{i\omega t + \frac{\pi}{2}}$$

$$\begin{aligned} \langle P \rangle_{avg} &= \frac{1}{T} \int_0^T V \cdot I dt \\ &= \int_0^T \hat{I}^2 R \cos^2(\omega t) dt - \frac{1}{T} \int_0^T \chi \hat{I}^2 \cdot \cos \omega t \sin \omega t dt \\ &= \frac{\hat{I}^2 R}{2} \end{aligned}$$

Ladder Impedance

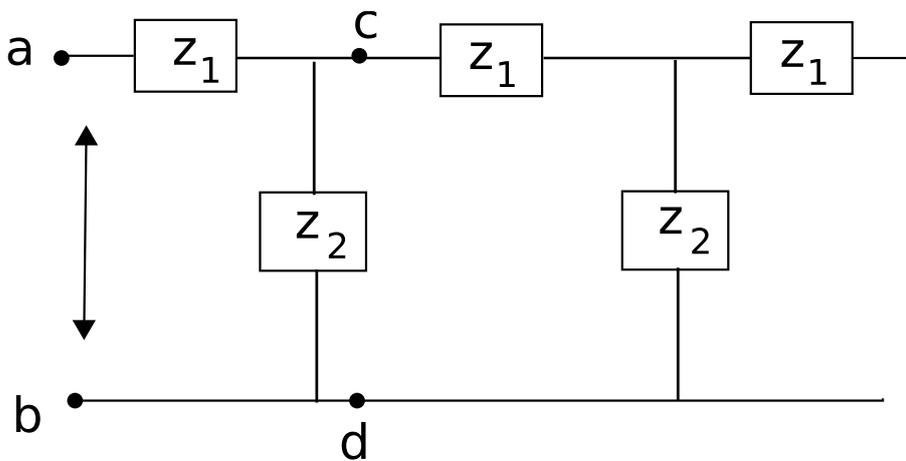

$$z = z_1 + \frac{z_2 z}{z_2 + z}$$


Solve:

$$z = \frac{z_1}{z} + \sqrt{\frac{z_1^2}{4} + z_1 z_2}$$

Let:

$$z_1 = i\omega L$$

$$z_2 = \frac{1}{i\omega C}$$

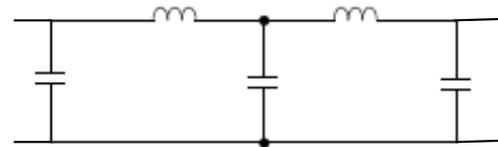

•

$$z = \frac{i\omega L}{2} + \sqrt{\frac{-\omega^2 L^2}{4} + \frac{L}{C}}$$

•

$$v < 0 \quad \text{for} \quad \frac{\omega^2 L^2}{4} > \frac{L}{C}$$

$$\omega^2 > \frac{4}{LC}$$

- for $\omega^2 < \frac{4}{LC}$, there's a real part = resistance! But from only $L = C$? It's because its infinite! Energy keeps traveling out for certain ω !

Critical Frequency - if you are under, energy will just keep going out. Otherwise, will go out and come back.