

Electricity and Magnetism

- Today
 - Ohm's Law
 - Electric Power
 - Electromotive Force
 - Circuits
 - Kirchoff's Rules

Electric Current

- We left Electrostatics
 - Now: Charges can move in steady state
- Electric Current I :
 - $I = dQ/dt$
 - Net amount of charge moving through conductor per unit time
- Units:
 - $[I] = C/s = A$ (Ampere)


Electric Current

- Current $I = dQ/dt$ has a direction
 - Convention: Direction of flow of positive charges
 - In our circuits, I carried by electrons
- To get a current:
 - Need mobile charges
 - Need $|E| > 0$ (Potential difference)

Resistivity

- Suppose we have
 - mobile charge carriers
 - a Potential difference
- What determines magnitude of I ?
 - limited by friction
- Charge carriers lose energy in collisions with e.g. metal lattice

Resistivity

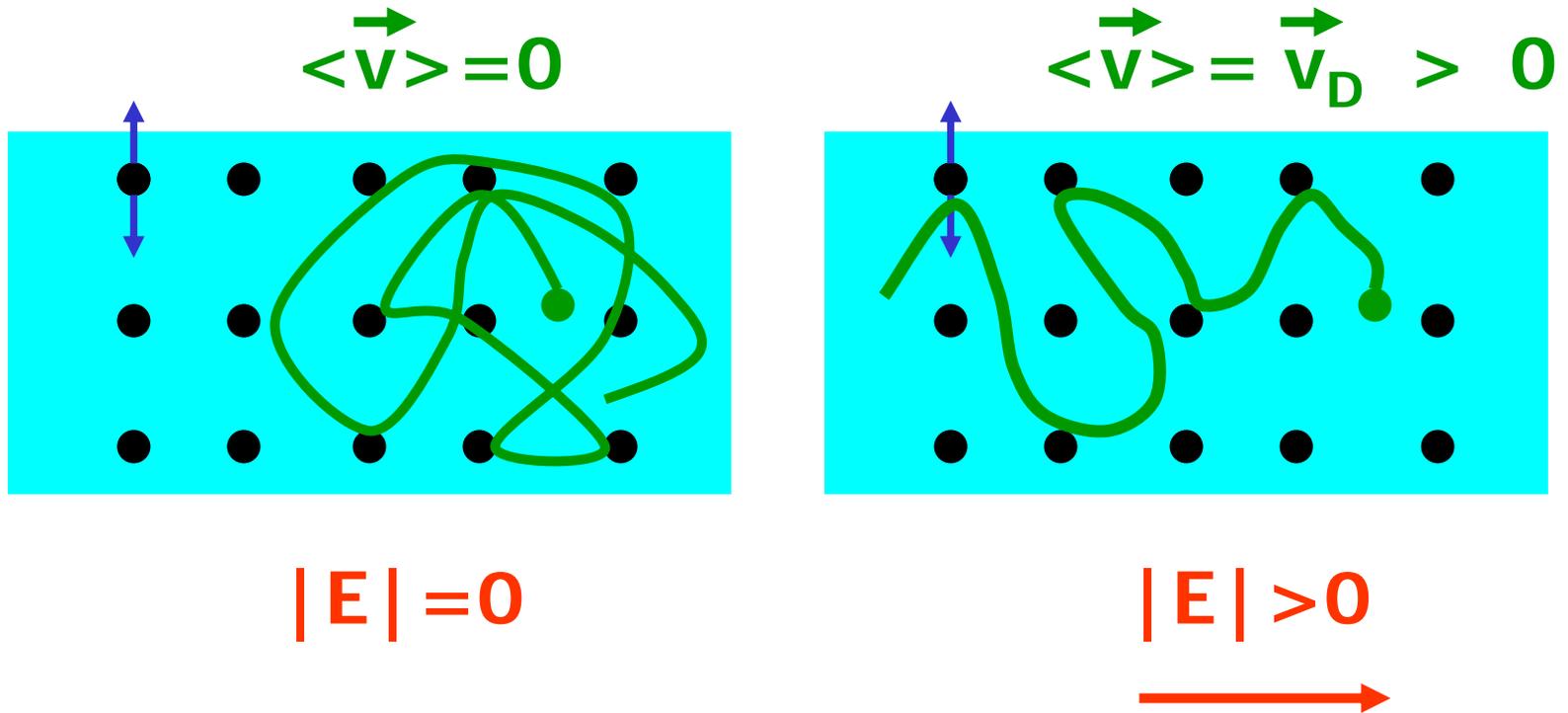

If $|E| > 0$: Electron accelerated between scatterings

On average: Electron moves in $-E$ direction

Resistivity


- Interplay of scattering and acceleration gives an average velocity v_D
- v_D is called 'Drift velocity'
- How fast do the electrons move?
 - Thermal speed is big: $v_{th} \sim 10^6$ m/s
 - Drift velocity is small: $v_D \sim 10^{-3}$ m/s
- All electrons in conductor start to move, as soon as $E > 0$

Resistivity

Ohm

$\rho = f / (q^2 n_q)$: Resistivity

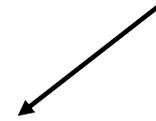Units: $[\rho] = \text{V/m m}^2/\text{A} = \text{m V/A} = \text{m } \Omega$



Material	ρ [m Ω]
Glass	$> 10^{10}$
Pure Water	$2 * 10^5$
Carbon	$3.5 * 10^5$
Silicon	2300
Sea Water	0.2
Gold	$2.4 * 10^{-8}$
Copper	$1.7 * 10^{-8}$

} Insulator

} Semiconductor

} Conductor

Resistance


- Define $R = V/I$: Resistance
- $R = \rho L / A = f / (n_q q^2) L / A$
 - for constant cross section A
- R is measured in Ohm $[W] = [V/A]$
- **Resistivity** ρ is property of material (e.g. glass)
- **Resistance** R is property of specific conductor, depending on material (ρ) and geometry

Resistance


- $R = \rho L / A = f / (n_q q^2) L / A$
 - assuming constant cross-section A
- What if $A = A(x)$?
- Slice into pieces dx with constant A

$$dR = \rho \, dx / A(x)$$

- Integrate

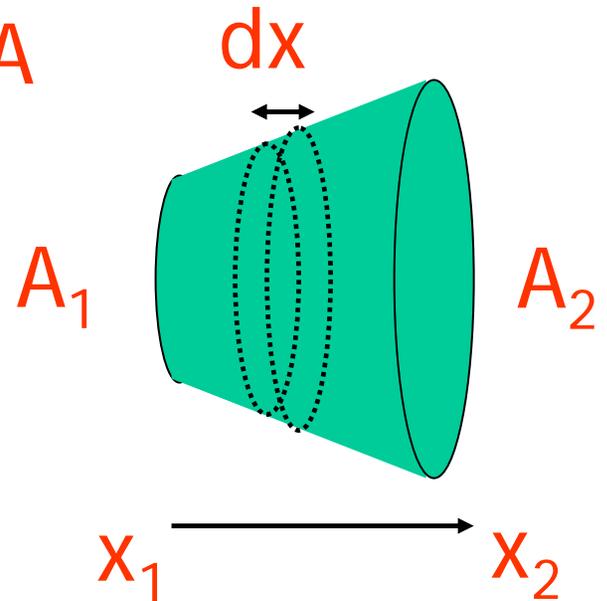


In-Class Demo

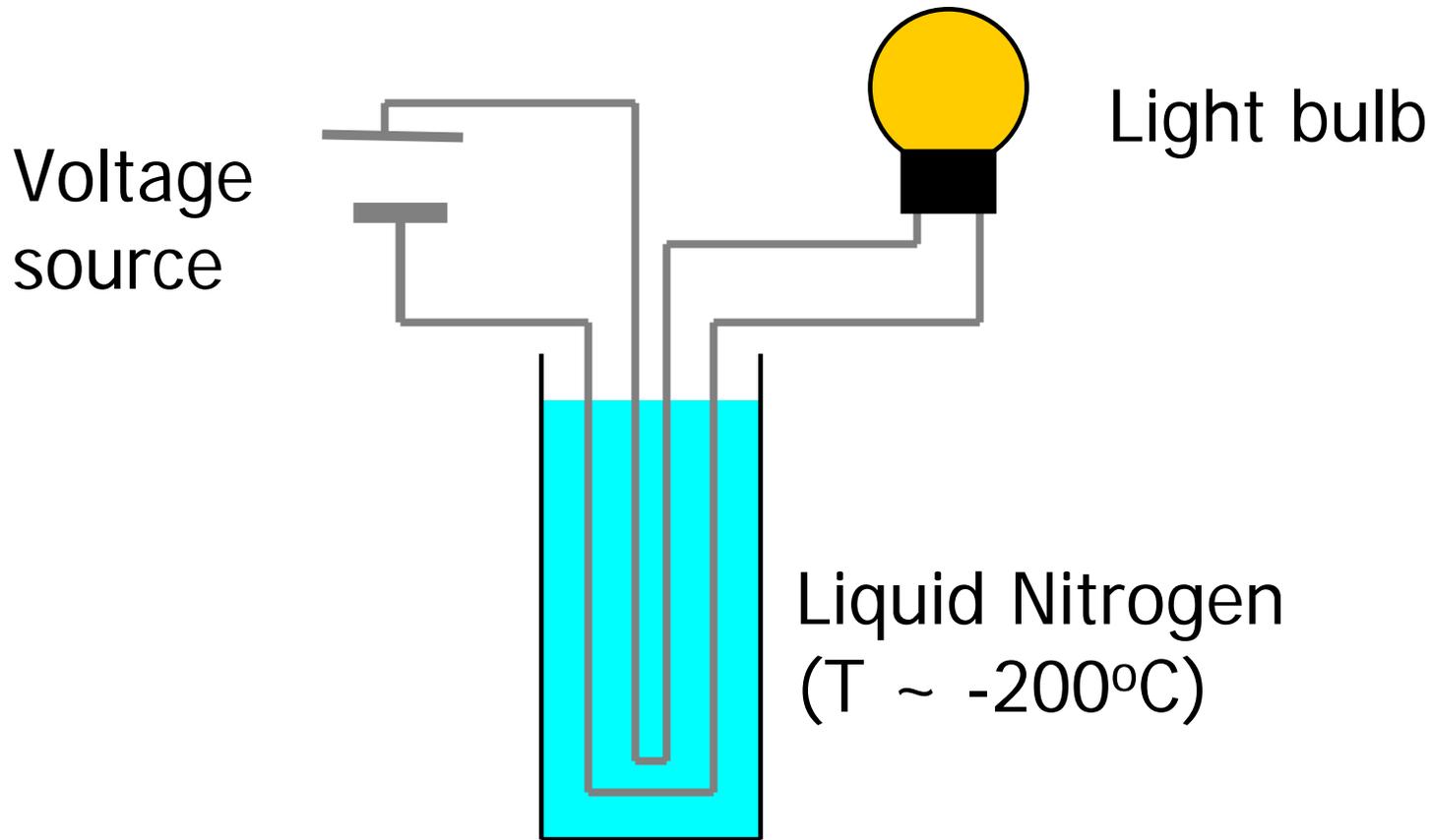

Resistivity depends on Temperature

Resistivity vs Temperature

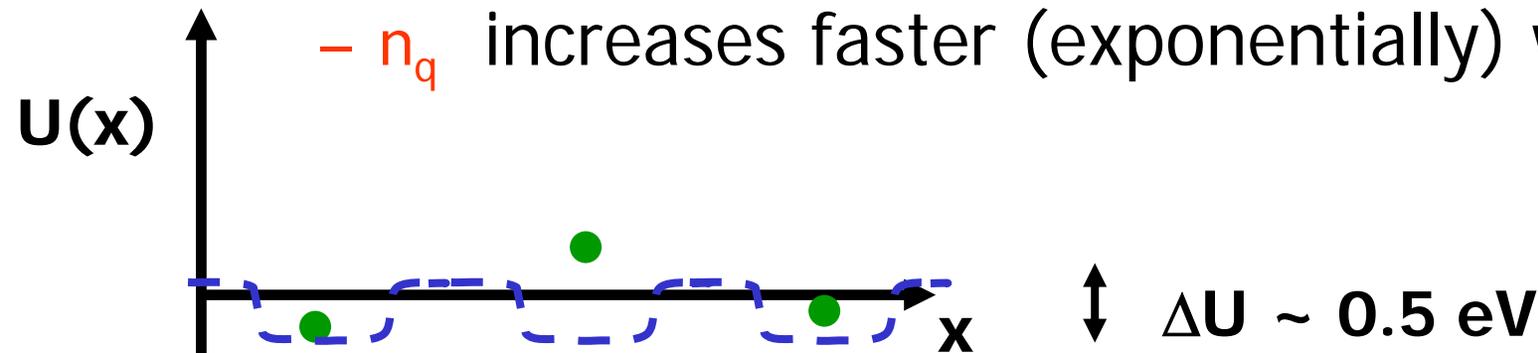- Resistivity $\rho = f / (q^2 n_q)$
- For Conductors: f increases with T
 - more scattering from vibrating lattice
- For Semiconductors: Different behaviour
 - f increases with T
 - n_q increases faster (exponentially) with T



Ohm's law

$$V = R I$$

- Isn't that just the definition of R ?
- Not quite
 - Def. $R = V/I$ for any conductor
 - Ohm's Law says that for some conductors, current and voltage are linear
 - For real conductors, that's an approximation (e.g. $R = R(T)$ and $T = T(I)$)


Electric Power

- Fundamental application of Electricity
 - Deliver Electric Power
 - Converted to
 - Mechanical power
 - Heat
 - Light


$$\begin{aligned} \text{Power} &= \text{Energy/time} = \\ dW/dt &= (dq V)/dt = \\ dq/dt V &= \underline{I V} = I^2 R = V^2/R \end{aligned}$$


Electric Circuits

Resistor

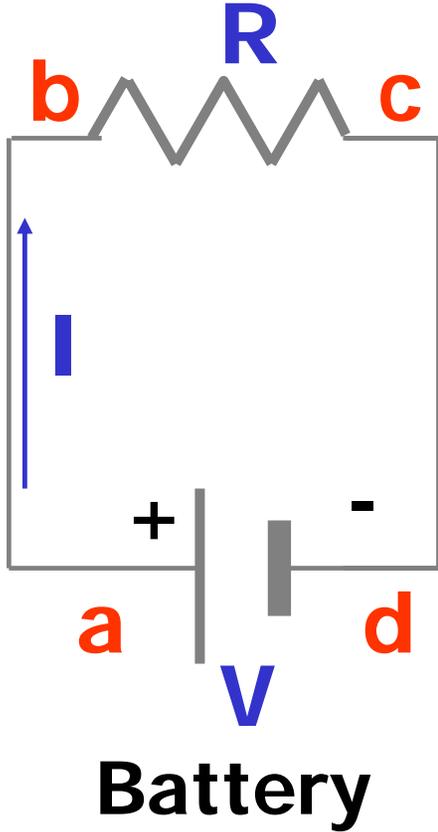

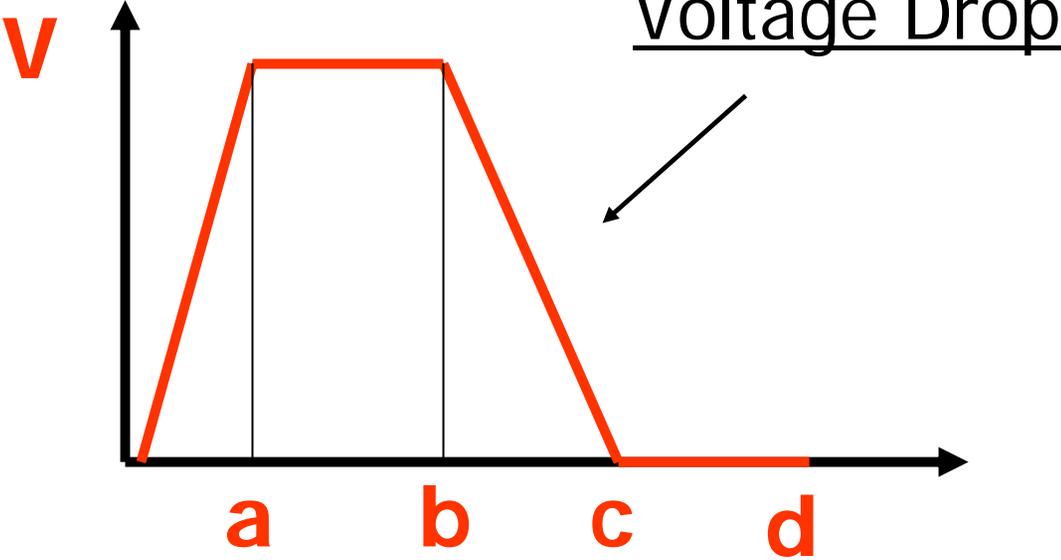
$$\left. \begin{aligned} V_{ad} &= V \\ V_{ab} &= 0 \\ V_{cd} &= 0 \end{aligned} \right\} \rightarrow V_{bc} = V_{ad} = \underline{IR}$$




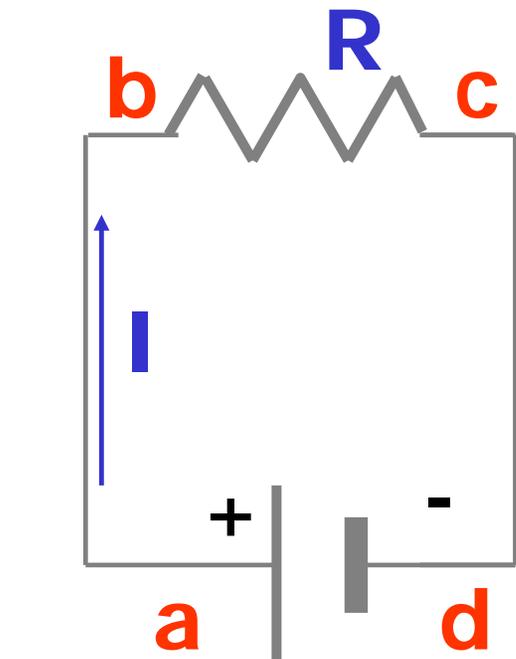

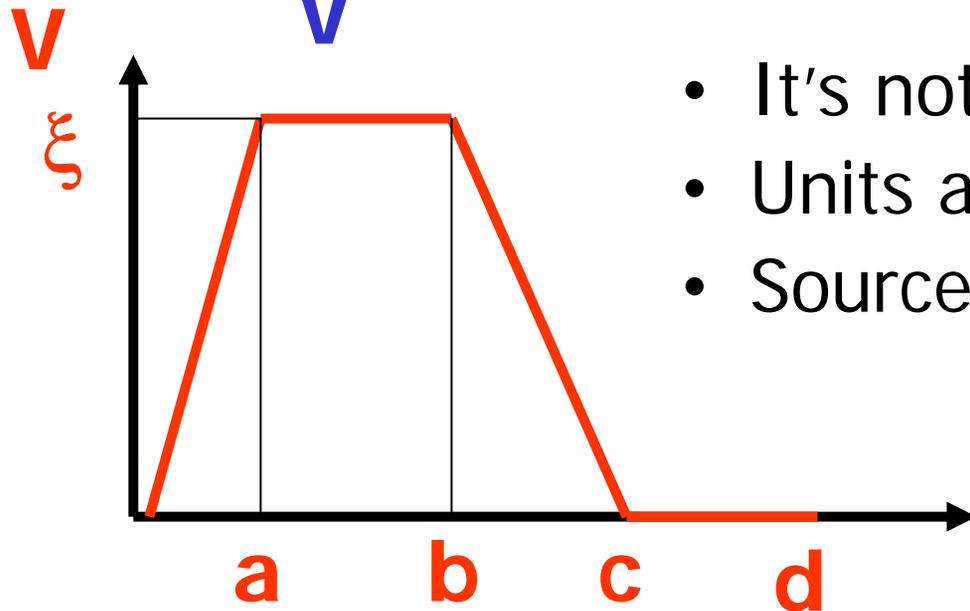- To keep charge moving
 - work $W = q V$ to get from **d** to **a**
- Def: $\xi = \text{Work/unit charge}$
- ξ is 'Electromotive Force' (EMF)
- It's not a Force!
- Units are **[V]**
- Sources of EMF: Battery, LVPS




In-Class Demo

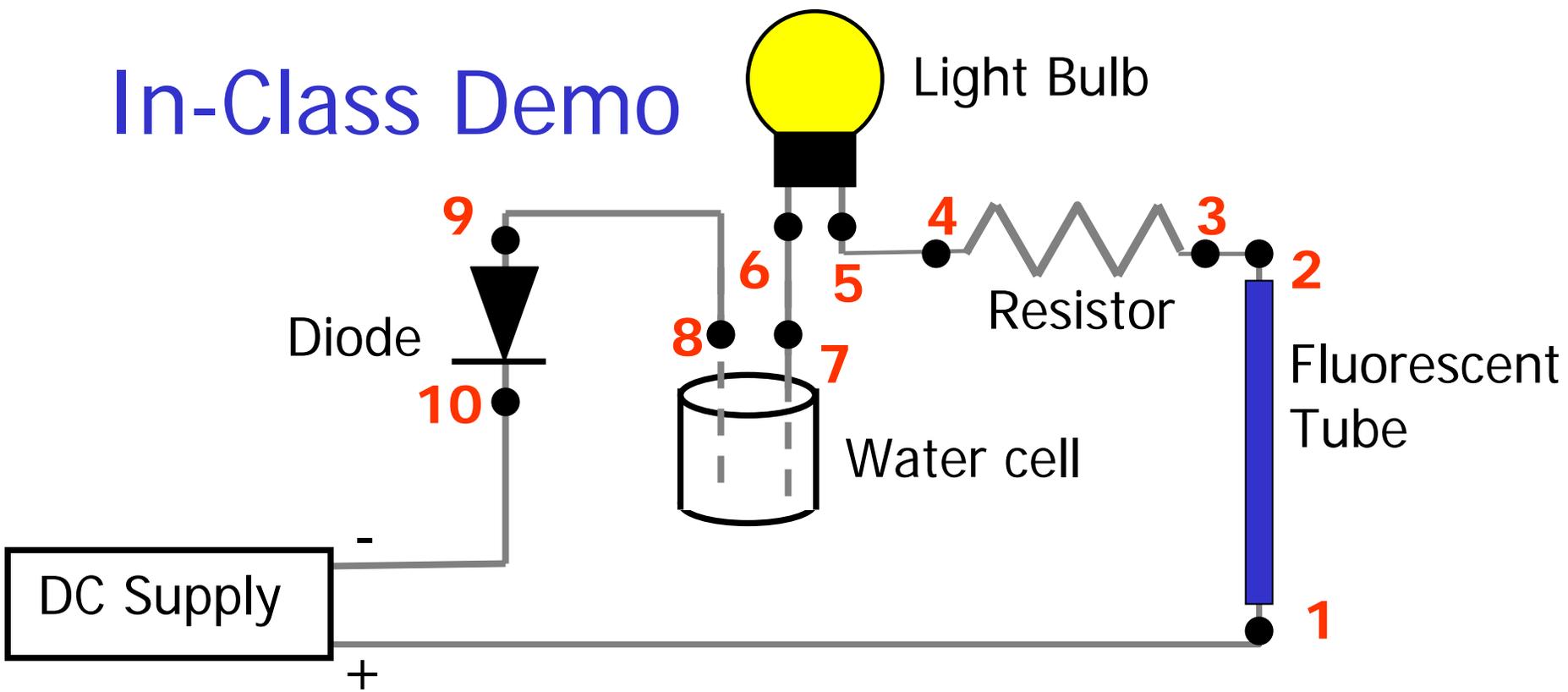

?

$$\text{EMF } \xi = V_{12} + V_{34} + V_{56} + V_{78} + V_{910}$$

Electromotive Force

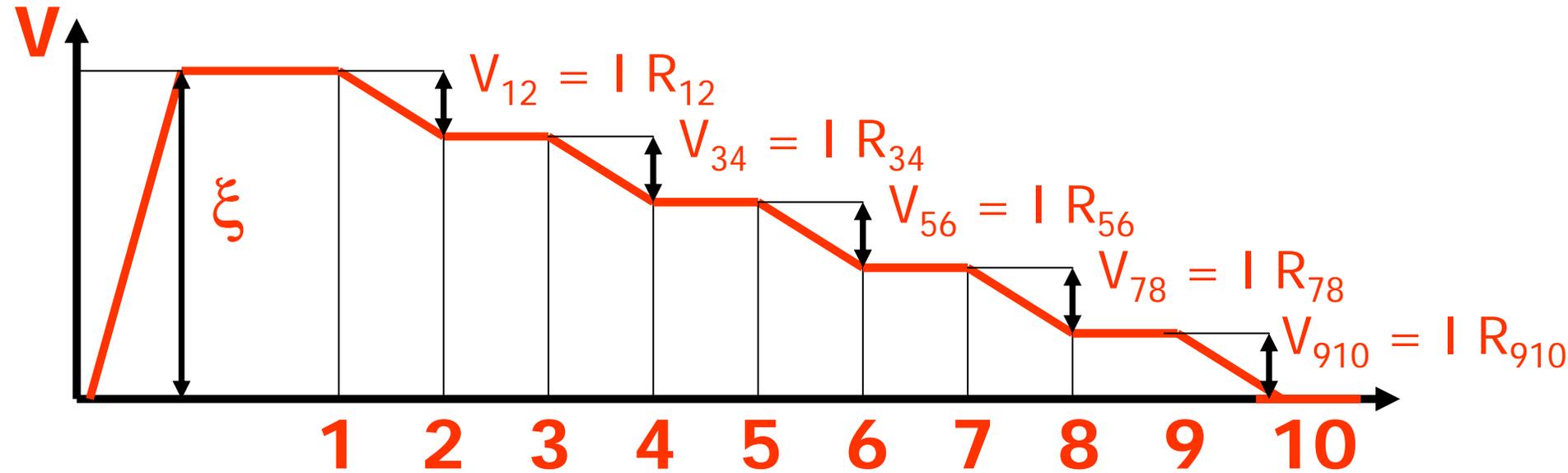


In general, $\sum \xi_i = \sum V_j$ Loop Rule

Electromotive Force

- Ideal source of EMF: $\xi = V = \text{constant}$
 - independent of I
- Problem: Power $P = IV = V^2/R$
 - for $R \rightarrow 0$, power gets infinite
- Real source of EMF: $V = \xi - I r$
 - r is internal resistance

Electromotive Force

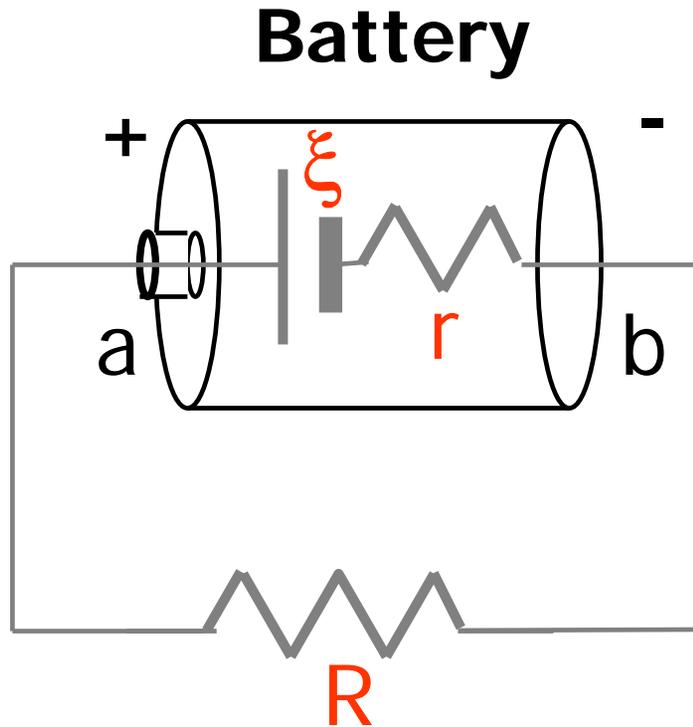

$$V_{ab} = \xi - I r$$

$$V_{ab} = I R$$


$$\rightarrow \xi - I r = I R$$

$$\rightarrow I = \xi / (r + R)$$

Old batteries: r gets larger

DC Circuits

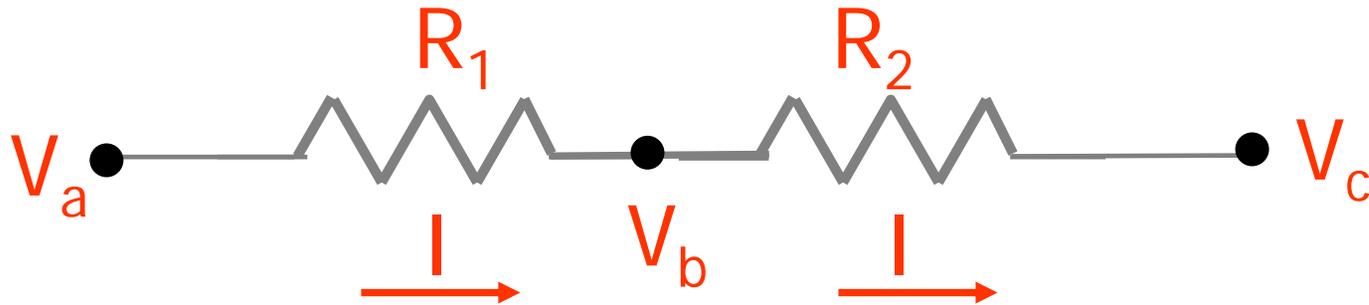
- DC: Direction of current doesn't change
- Example: Resistors in series



$$\begin{aligned} V_{ac} &= V_{ab} + V_{bc} = I R_1 + I R_2 = I (R_1 + R_2) \\ &= I R_{eq} \text{ for } R_{eq} = (R_1 + R_2) \end{aligned}$$

DC Circuits

- Next example: Resistors in parallel

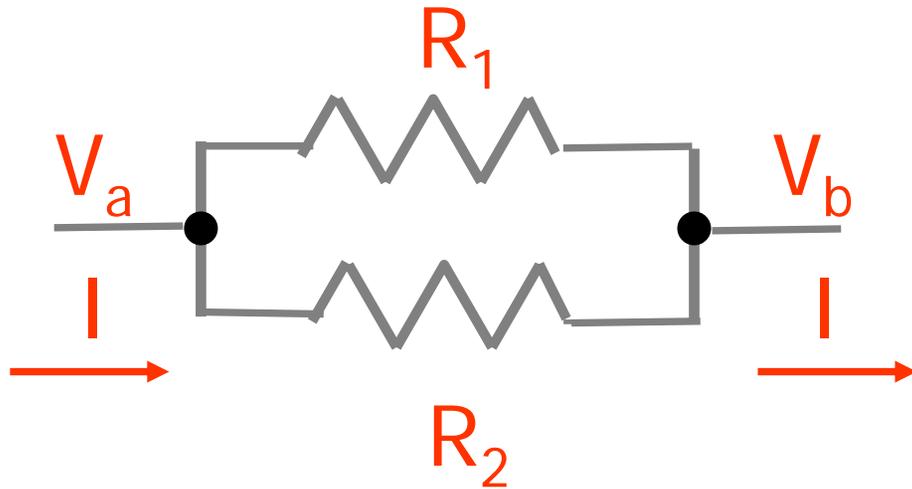

$$I = I_1 + I_2 = V_{ab}/R_1 + V_{ab}/R_2 = V_{ab}/R_{eq}$$


$$\rightarrow 1/R_{eq} = 1/R_1 + 1/R_2$$

Kirchoff's Rules

- Junction rule

At junctions:
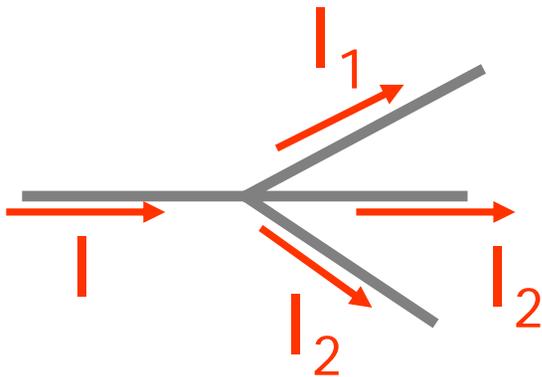
$$\sum I_{\text{in}} = \sum I_{\text{out}}$$



Charge conservation

- Loop rule

Around closed loops:


$$\sum \Delta V_j = 0$$

ΔV for both EMFs
and Voltage drops

Energy conservation

Kirchoff's Rules

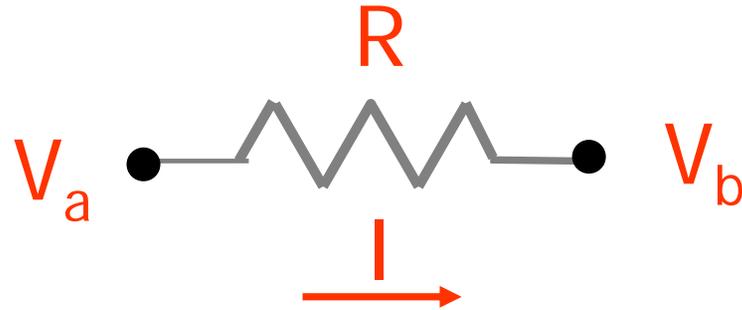
- Kirchoff's rules allow us to calculate currents for complicated DC circuits
- Main difficulty: Signs!
- Rule for resistors:



$\Delta V = V_b - V_a = - I R$, if we go in the direction of I (voltage drop!)


Kirchoff's Rules

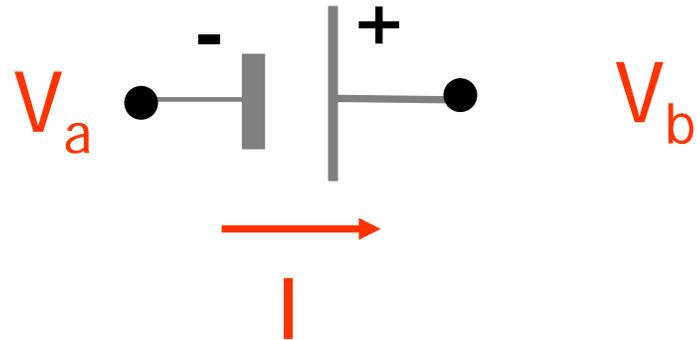- Kirchoff's rules allow us to calculate currents for complicated DC circuits
- Main difficulty: Signs!
- Rule for EMFs:



$$\Delta V = V_b - V_a = \xi, \text{ if we go in the direction of } I$$

Example

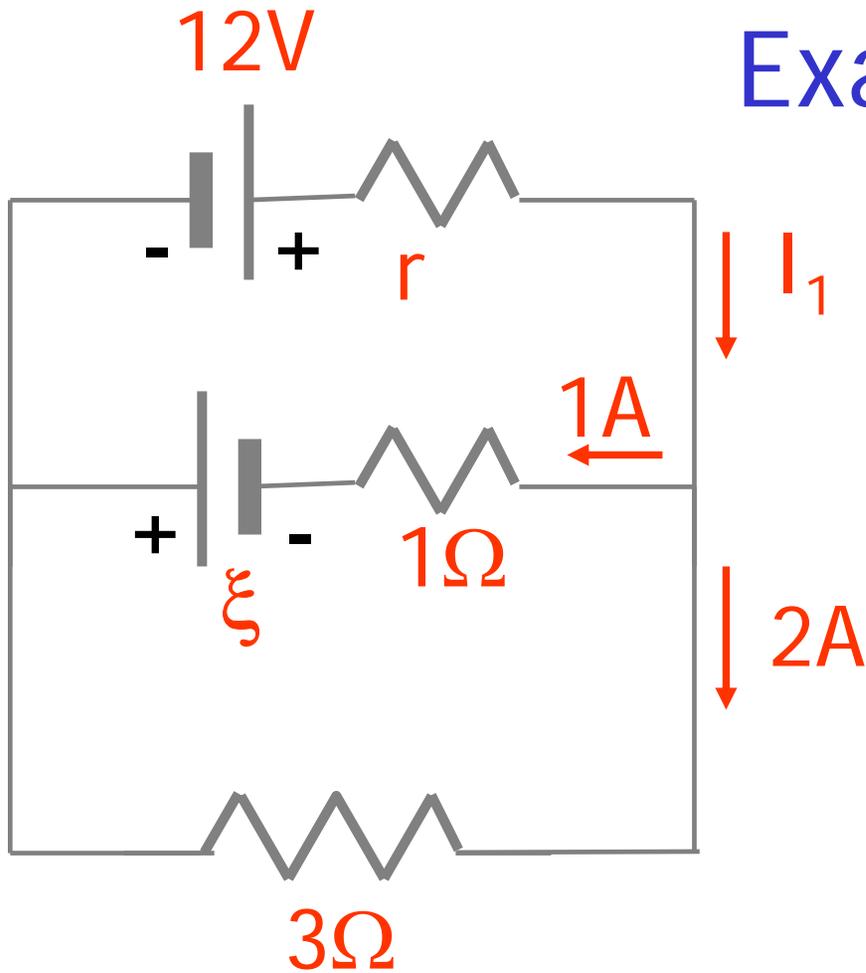

r, ξ, I_1 ? 3 unknowns

- Pick signs for I_1, ξ
- Junction rule
$$I_1 = 1A + 2A = 3A$$
- Loop rule (1)
$$12V - 6V - 3A r = 0$$
$$\rightarrow r = 6/3 \Omega = 2 \Omega$$
- Loop rule (2)
$$12V - 6V - 1V + \xi = 0$$
$$\rightarrow \xi = 5V$$