

Electricity and Magnetism


- Today: Review for Quiz #2
 - Conductors in E-Field/Potential
 - Capacitance/Capacitors
 - Dielectrics/Polarization
 - Current/Current Density
 - Resistance/Resistivity
 - DC circuits
 - Electric Power
 - Kirchoff's Rules
 - RC Circuits

Conductors in Electrostatics

- $E = 0$ inside (in Electro*statics*)
 - otherwise charges would move
- No charges inside
 - Gauss
- $E = \sigma/\epsilon_0$ perpendicular to surface
 - otherwise charges on surface would move
- Potential is constant on conductor

Charge Density

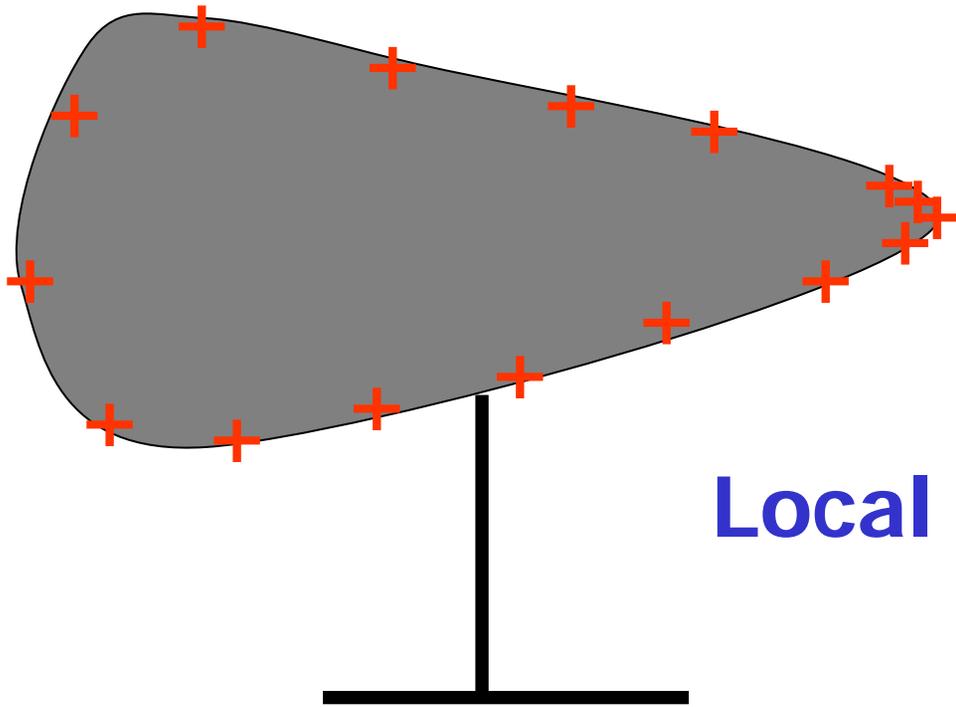**In-Class Demo: Application: Lightning rod -
Biggest E near pointy tip!**



$$\Rightarrow E \propto \frac{1}{r} \propto \sigma$$

Local radius of curvature

Charge distribution and Geometry


$$V_0 = \frac{Q_0}{4\pi\epsilon_0 r_0} =$$

$$V_1 = \frac{Q_1}{4\pi\epsilon_0 r_1}$$


$$\Rightarrow Q_0/r_0 = Q_1/r_1 = 4\pi\epsilon_0 V = \text{const.}$$

$$E_i = \frac{\sigma_i}{2\epsilon_0} = \frac{Q_i}{4\pi\epsilon_0 r_i^2}$$
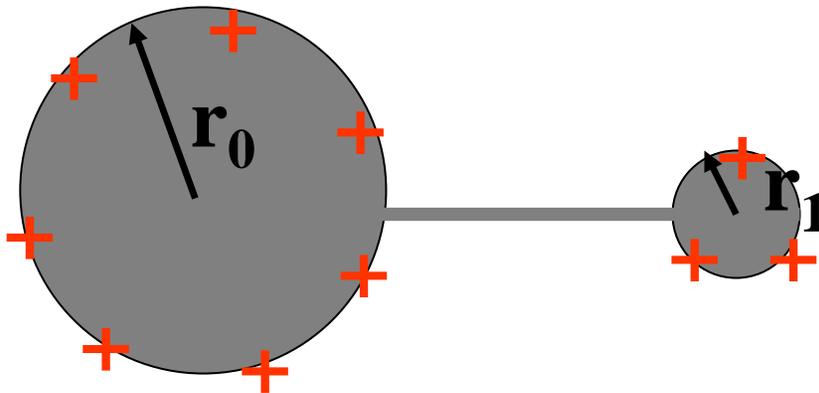
$$\Rightarrow E \propto \frac{1}{r} \propto \sigma$$




Charge and Potential

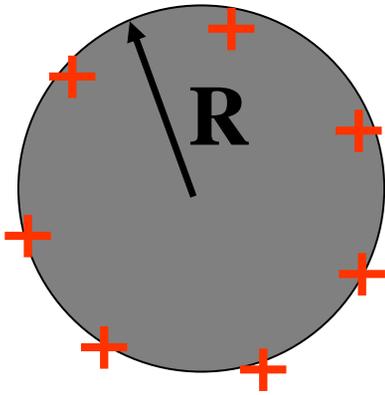

Charged Sphere

$$V = 1/(4 \pi \epsilon_0 R) Q$$

Geometry!

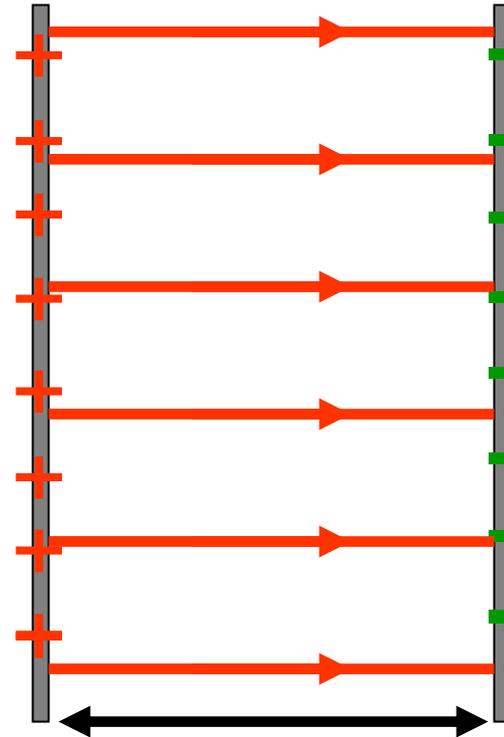


Parallel Plate Capacitor

$$V = d/(A \epsilon_0) Q$$

Charge and Potential

- For given geometry, Potential and Charge are proportional
- Define
 - $Q = C V$ -> **C is Capacitance**
- Measured in $[F] = [C/V]$: Farad
- **C** tells us, how easy it is to store charge on it ($V = Q/C$)

Capacitance

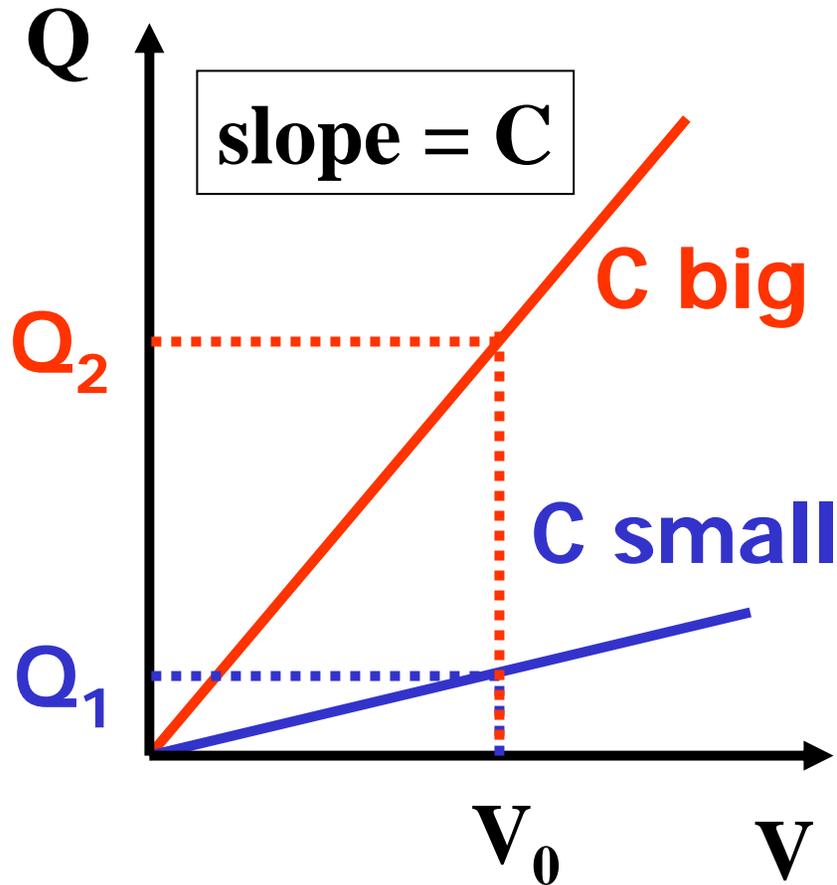


C bigger -> Can store more Charge!

Capacitor

- Def: Two conductors separated by insulator
- Charging capacitor:
 - take charge from one of the conductors and put on the other
 - separate + and - charges

Parallel Plate Capacitor

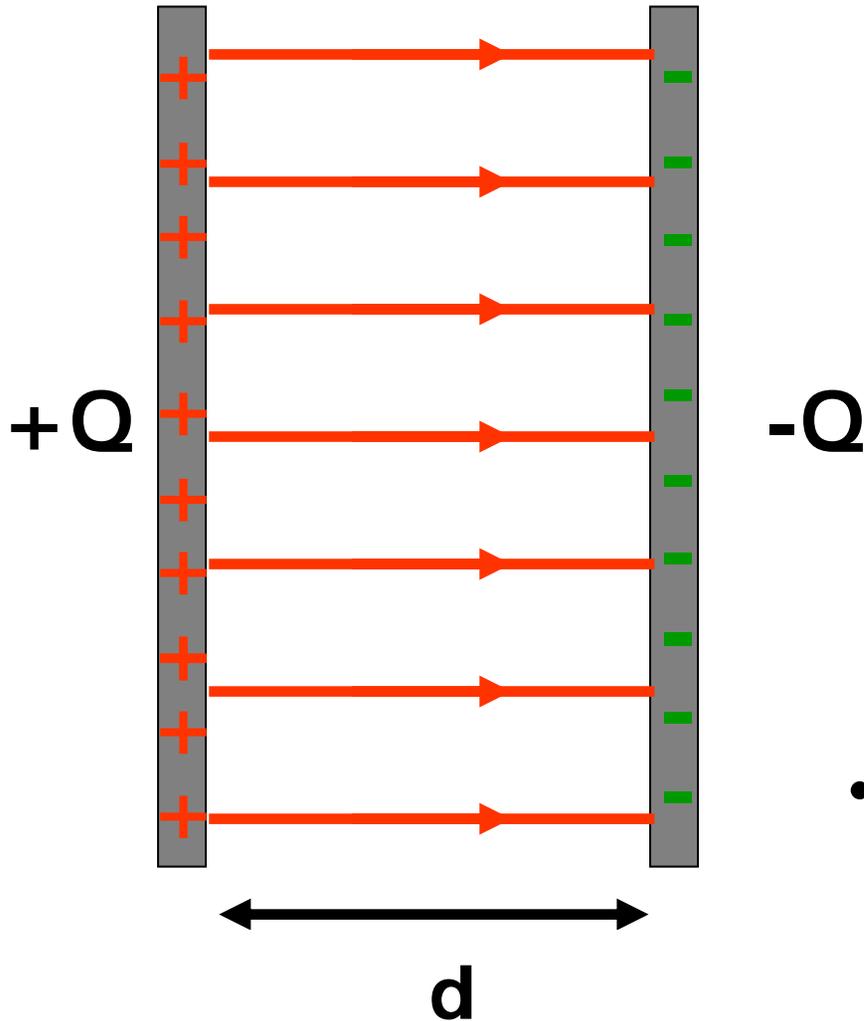

$$\begin{aligned} C &= \frac{Q}{V(a) - V(b)} = \frac{Q}{E d} \\ &= \frac{Q}{\frac{\sigma}{\epsilon_0} d} = \frac{Q}{\frac{Q}{A \epsilon_0} d} = \\ &= \epsilon_0 \frac{A}{d} \end{aligned}$$

- To store lots of charge
 - make A big
 - make d small


Energy stored in Capacitor

$$\begin{aligned}W_{tot} &= \int_{Q_{initial}}^{Q_{final}} V dq = \int_0^Q V dq \\&= \int_0^Q q/C dq = \frac{1}{C} \int_0^Q q dq \\&= \frac{1}{C} \frac{Q^2}{2}\end{aligned}$$

- Work $W = \frac{1}{2} Q^2/C = \frac{1}{2} C V^2$ needed to charge capacitor
- Energy conserved
- But power can be amplified
 - Charge slowly
 - Discharge very quickly

In-Class Demo

$$C = 100\mu\text{F}$$

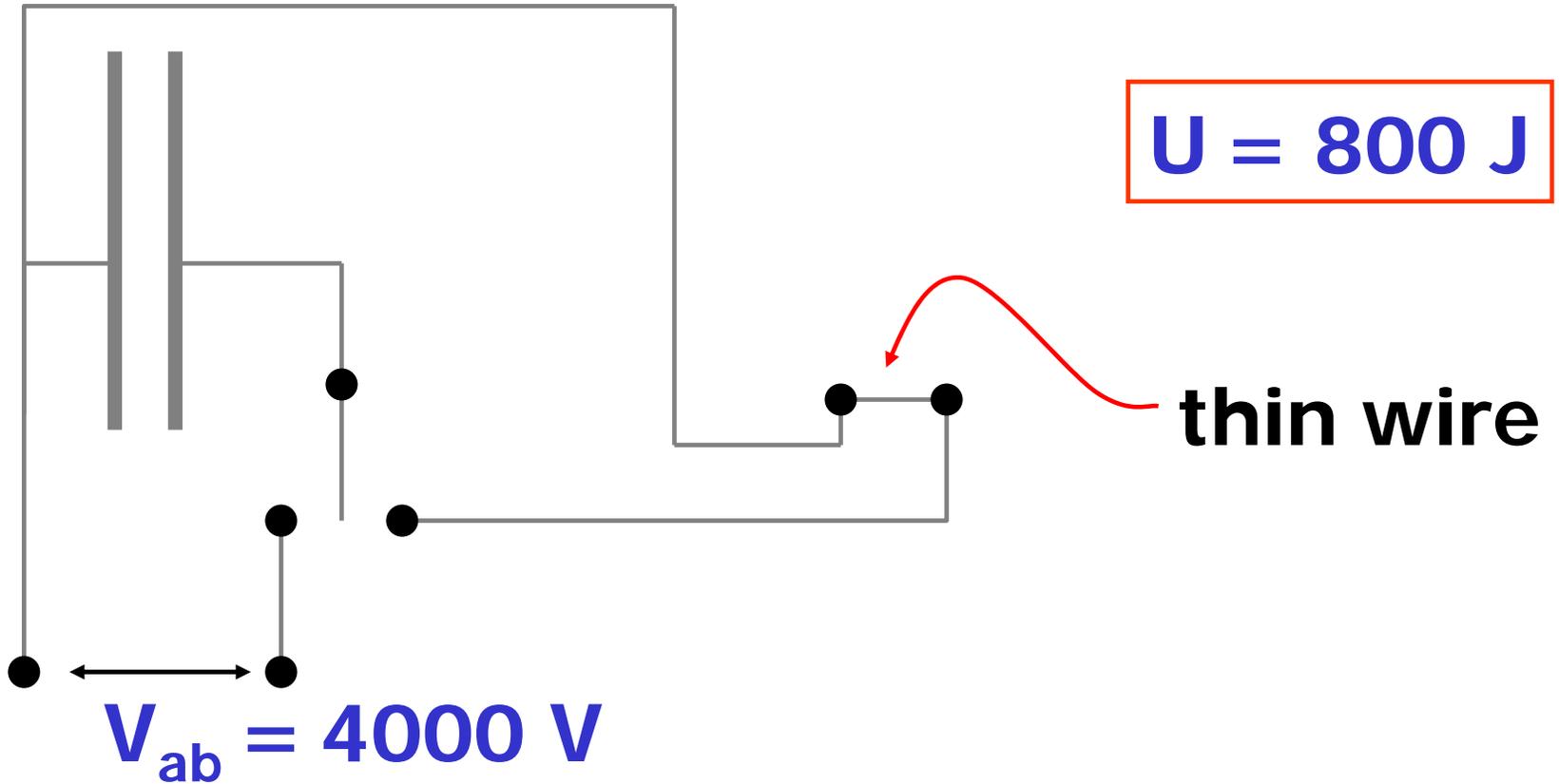


Where is the energy stored?

- Energy is stored in Electric Field

$$U_{stored} = \frac{1}{2}CV^2 = \frac{1}{2}\left(\epsilon_0 \frac{A}{d}\right)(E d)^2$$
$$= \frac{1}{2}\epsilon_0 E^2 \text{ Volume} \quad +Q$$

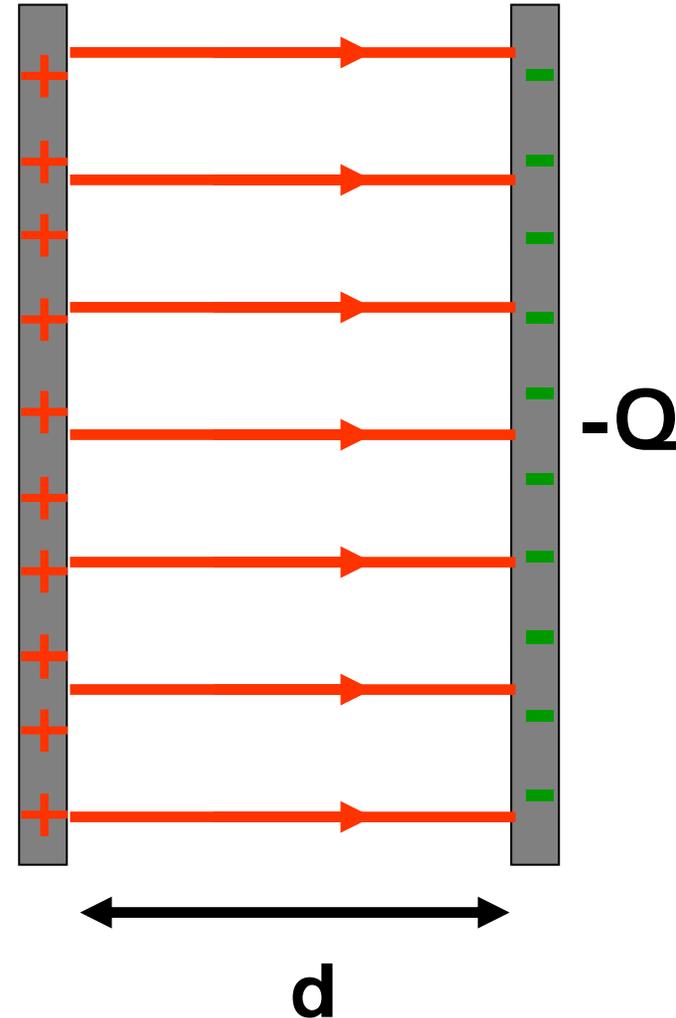- E^2 gives Energy Density:
- $U/\text{Volume} = \frac{1}{2} \epsilon_0 E^2$



Dielectrics

- Parallel Plate Capacitor:
 - $C = \epsilon_0 A/d$
 - Ex. $A = 1\text{m}^2$, $d=0.1\text{mm}$
–> $C \sim 0.1\mu\text{F}$
- How can one get small capacitors with big capacity?


In your toolbox:



2 cm

$C = 1000\mu\text{F}$


Dielectric Demo

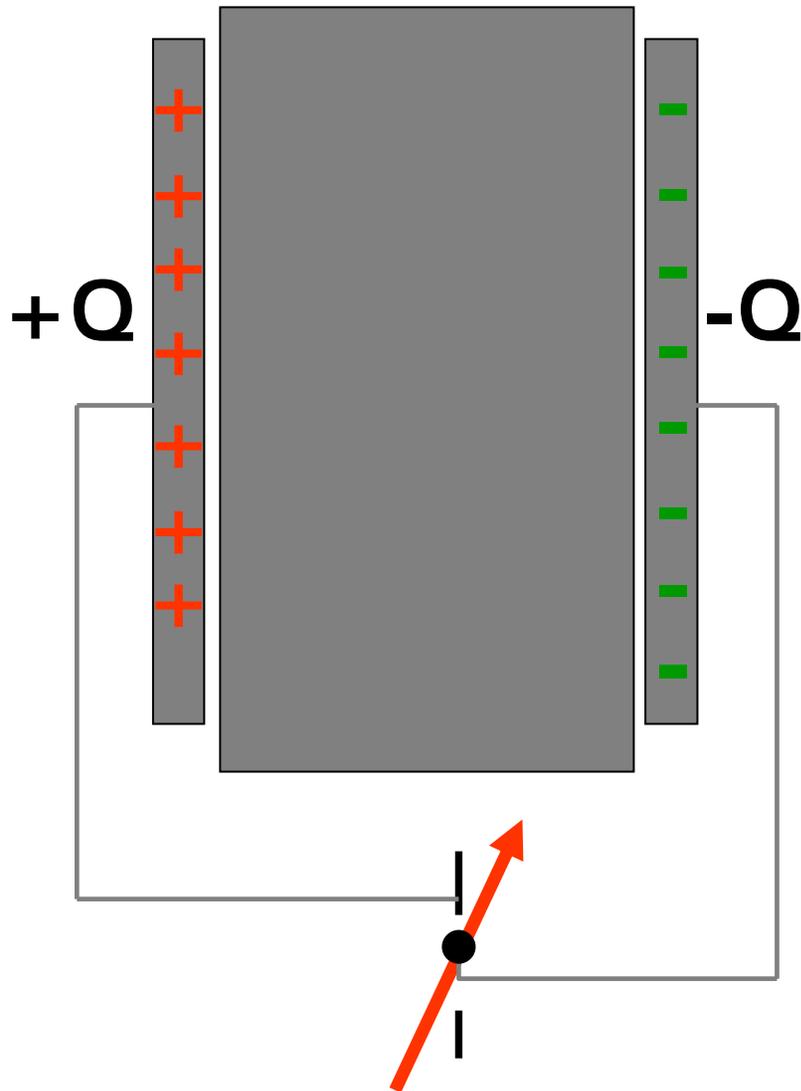

- Start w/ charged capacitor
- **d** big \rightarrow **C** small \rightarrow **V** large
- Insert Glass plate
- Now **V** much smaller
- **C** bigger
- But **A** and **d** unchanged !
- Glass is a Dielectric

Microscopic view

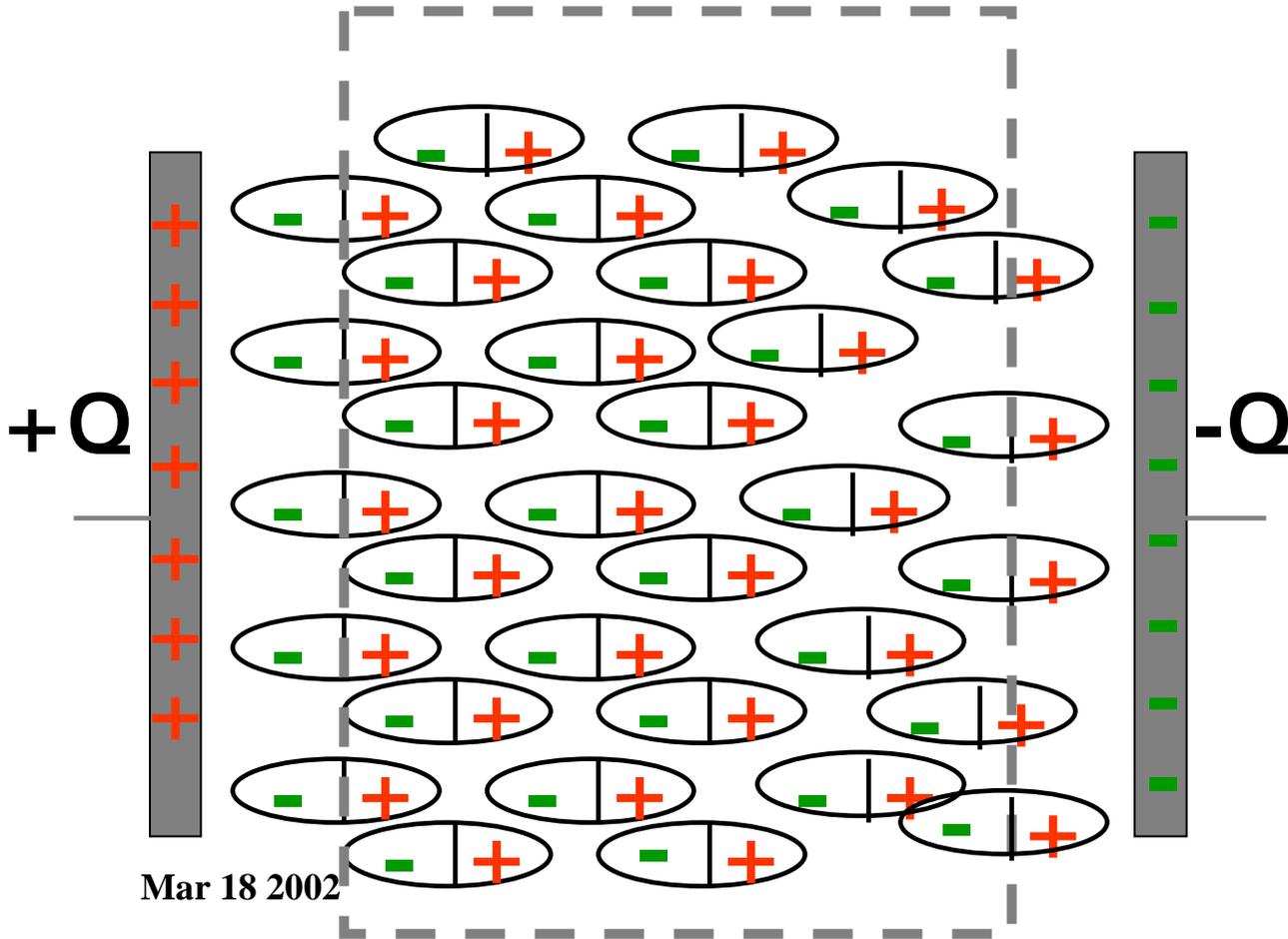
Polarization $\vec{P} = \text{const.}$ $\vec{E} = \epsilon_0 \chi \vec{E}$



Microscopic view

Inside: Charges compensate

Surface: Unbalanced Charges!

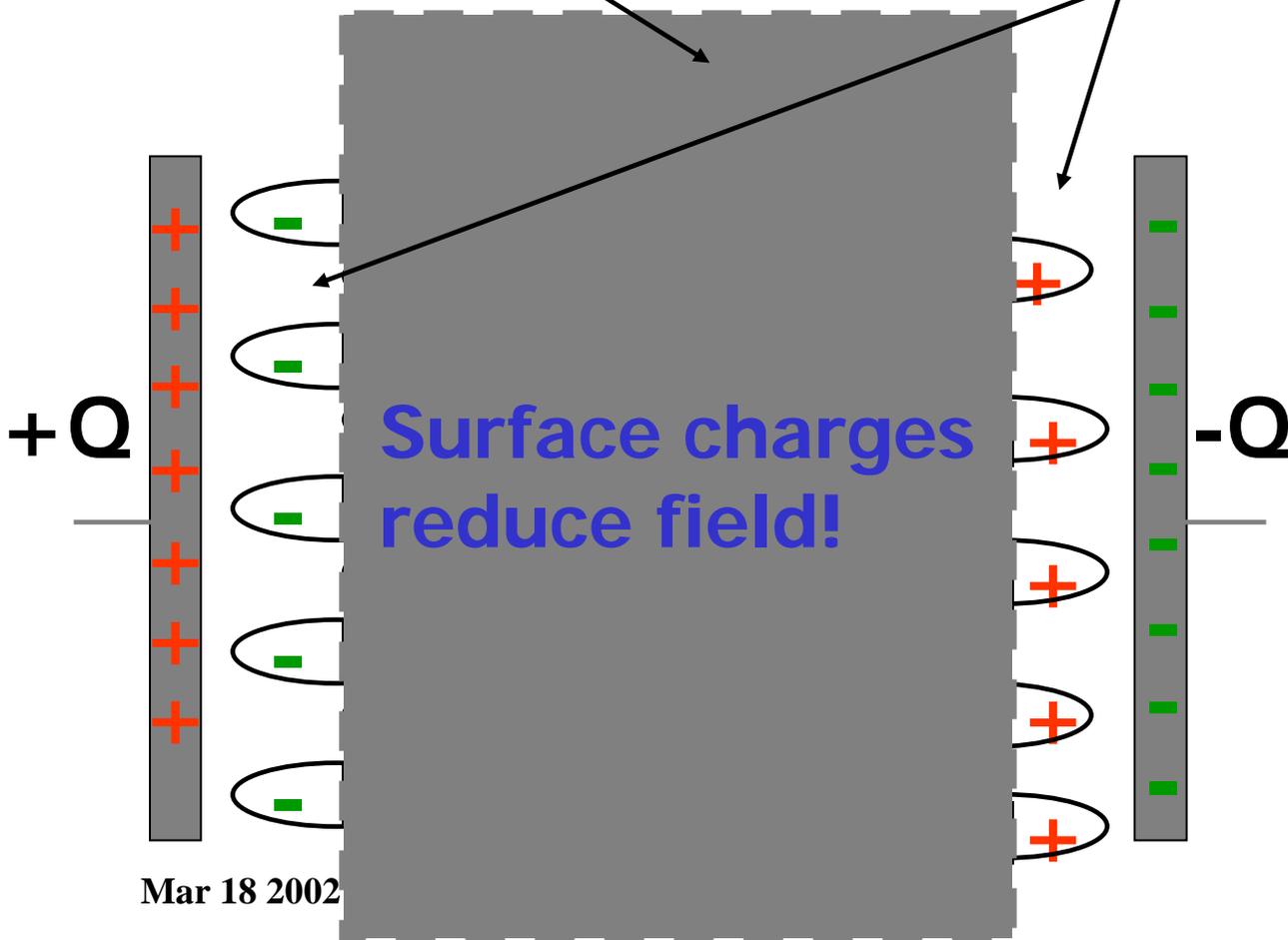

Dielectric Constant

$$E = \frac{\sigma}{2\epsilon_0} + \frac{\sigma}{2\epsilon_0} - \frac{|\sigma_p^+|}{2\epsilon_0} - \frac{|\sigma_p^-|}{2\epsilon_0}$$

Add contributions to E

$$= \frac{\sigma}{\epsilon_0} - \frac{P}{\epsilon_0}$$

E from plates and E from Dielectric surface charge

$$= E_0 + \chi E$$

$$\rightarrow E = \frac{E}{1 + \chi} \equiv \frac{E_0}{K}$$

K: Dielectric Constant

Field w/o Dielectric

Dielectric Constant

- Dielectric reduces field E_0 ($K > 1$)
 - $E = 1/K E_0$
- Dielectric increases Capacitance
 - $C = Q/V = Q/(E d) = K Q/(E_0 d)$
- This is how to make small capacitors with large C !


Electric Current

- We left Electrostatics
 - Now: Charges can move in steady state
- Electric Current I :
 - $I = dQ/dt$
 - Net amount of charge moving through conductor per unit time
- Units:
 - $[I] = C/s = A$ (Ampere)

Electric Current

- Current $I = dQ/dt$ has a direction
 - Convention: Direction of flow of positive charges
 - In our circuits, I carried by electrons
- To get a current:
 - Need mobile charges
 - Need $|E| > 0$ (Potential difference)

Resistivity

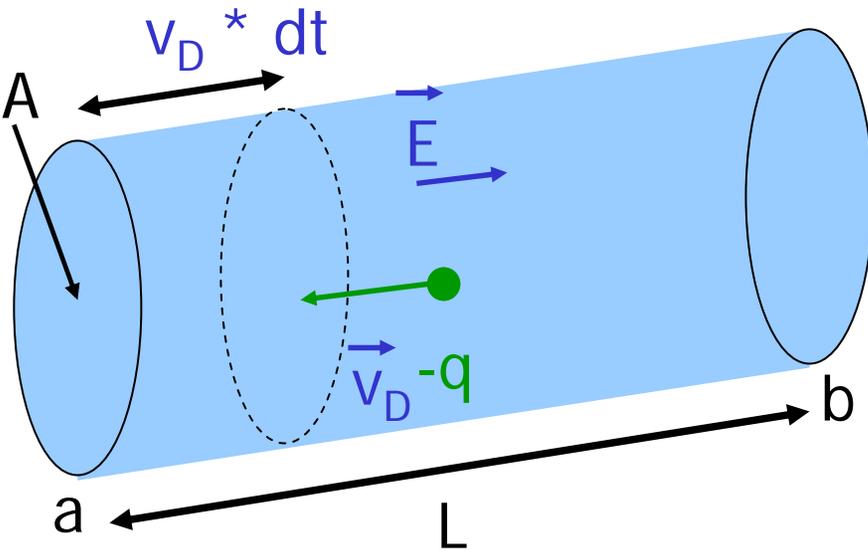

$$I = q n_q v_D A$$

Velocity Area

Current Density $\vec{J} = q n_q v_D$ vs Field \vec{E} ?

Remember: $\vec{v}_D = (q_e \vec{E}) / f \rightarrow \vec{J} = \underbrace{q^2 n_q / f}_{\text{constant}} \vec{E}$

$$\vec{J} = 1/\rho \vec{E}; \rho = f / (q^2 n_q)$$

Resistivity


- Interplay of scattering and acceleration gives an average velocity v_D
- v_D is called 'Drift velocity'
- How fast do the electrons move?
 - Thermal speed is big: $v_{th} \sim 10^6$ m/s
 - Drift velocity is small: $v_D \sim 10^{-3}$ m/s
- All electrons in conductor start to move, as soon as $E > 0$

Resistivity

Ohm

$\rho = f / (q^2 n_q)$: Resistivity

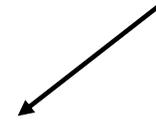Units: $[\rho] = \text{V/m m}^2/\text{A} = \text{m V/A} = \text{m } \Omega$



Material	ρ [m Ω]
Glass	$> 10^{10}$
Pure Water	$2 * 10^5$
Carbon	$3.5 * 10^5$
Silicon	2300
Sea Water	0.2
Gold	$2.4 * 10^{-8}$
Copper	$1.7 * 10^{-8}$

} Insulator

} Semiconductor

} Conductor

Resistance

- Define $R = V/I$: Resistance
- $R = \rho L / A = f / (n_q q^2) L / A$
 - for constant cross section A
- R is measured in Ohm $[W] = [V/A]$
- **Resistivity** ρ is property of material (e.g. glass)
- **Resistance** R is property of specific conductor, depending on material (ρ) and geometry


Resistance

- $R = \rho L / A = f / (n_q q^2) L / A$
 - assuming constant cross-section A
- What if $A = A(x)$?
- Ex. hollow cylinder, R between inner and outer surface
- Slice into pieces with constant A

$$\begin{aligned} dR &= \rho \, dr / A(r) \\ &= \rho \, dr / (2 \pi r L) \end{aligned}$$

- Integrate

$$R = \rho / (2 \pi L) \ln(r_2 / r_1)$$

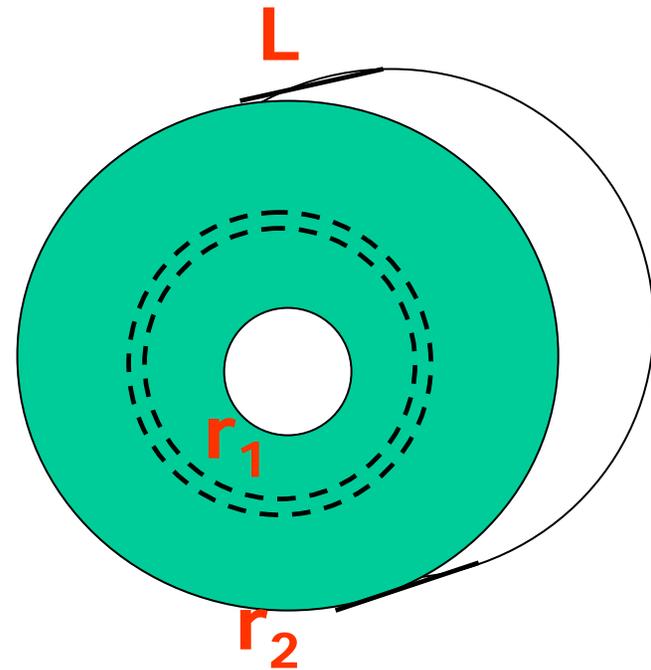

Ohm's law

$$V = R I$$

- Conductor is 'Ohmic', if R does not depend on V, I
- For real conductors, that's is only approximately true (e.g. $R = R(T)$ and $T = T(I)$)
- Approximation
 - valid for resistors in circuits
 - not valid for e.g. light bulbs


Electric Power

- Use moving charges to deliver power

$$\begin{aligned} \text{Power} &= \text{Energy/time} = \\ dW/dt &= (dq V)/dt = \\ dq/dt V &= \underline{I V} = I^2 R = V^2/R \end{aligned}$$

Electric Circuits



Resistor

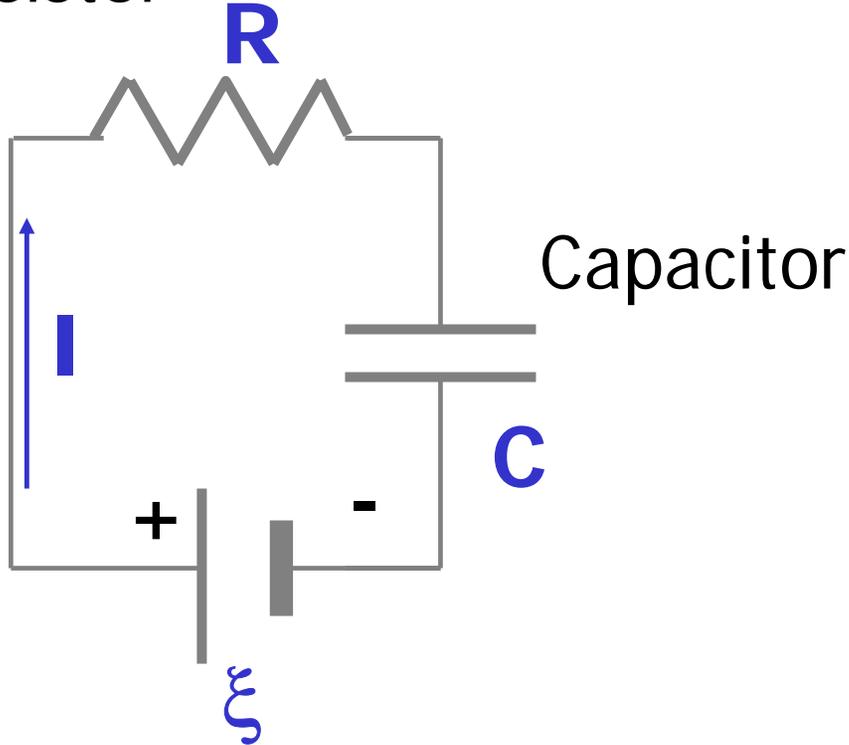

Source of EMF


Electromotive Force EMF

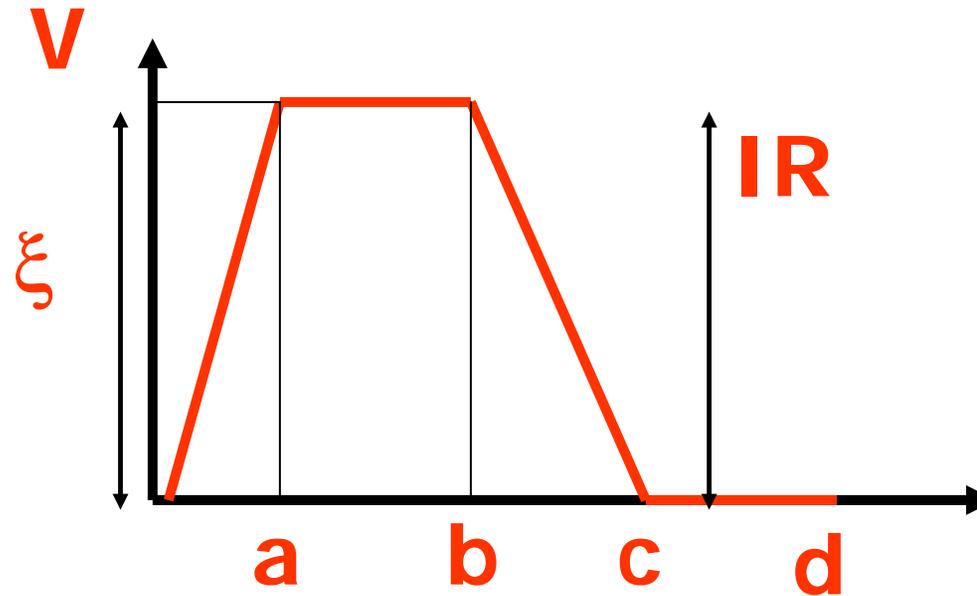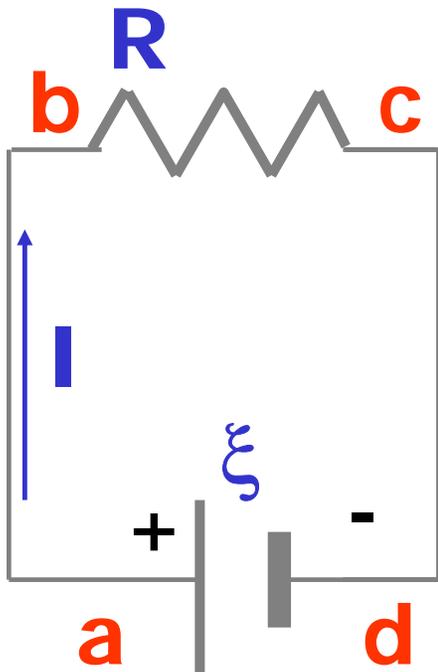- Def: $\xi = \text{Work/unit charge}$
- ξ is 'Electromotive Force' (EMF)
- Units are [V]



Internal Resistance

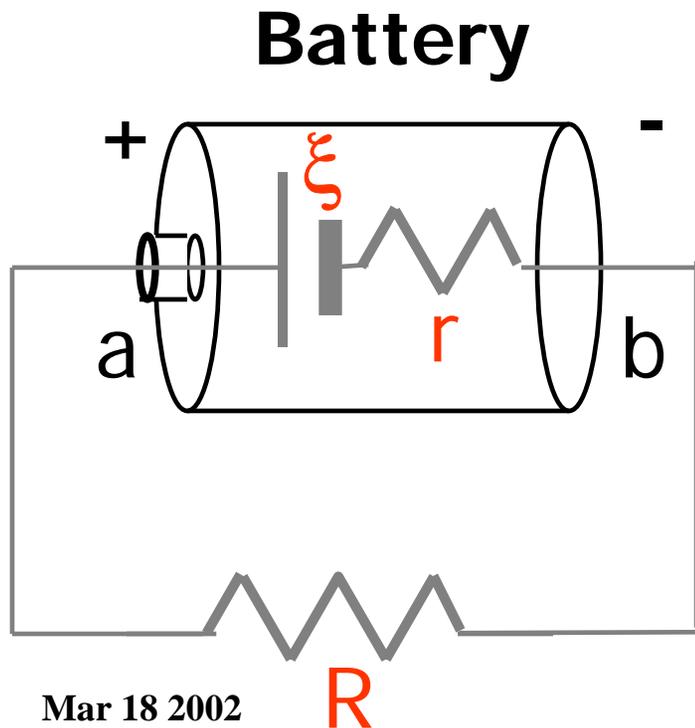- Sources of EMF have internal resistance r
- Can't supply infinite power




$$V_{ab} = \xi - I r$$

$$= IR$$

$$\rightarrow I = \xi / (r + R)$$

Electric Circuits

Resistors in series

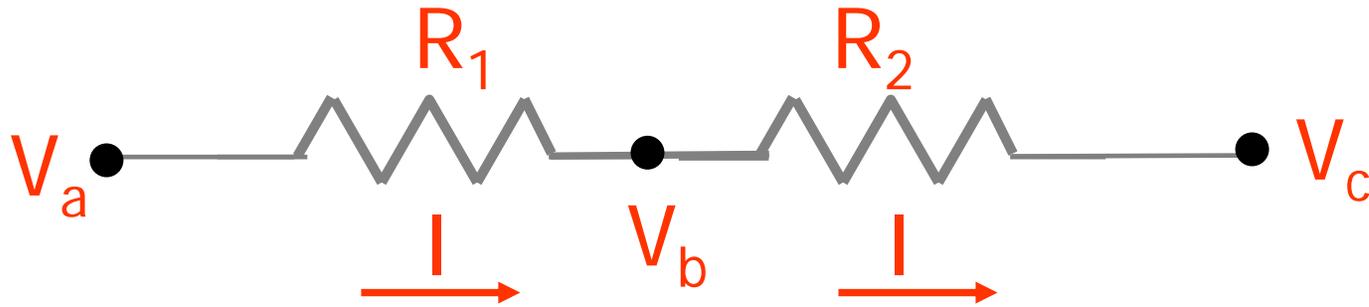


$$V_{ac} = V_{ab} + V_{bc} = I R_1 + I R_2 = I (R_1 + R_2)$$

$$= I R_{eq} \text{ for } R_{eq} = (R_1 + R_2)$$

Electric Circuits


Resistors in parallel

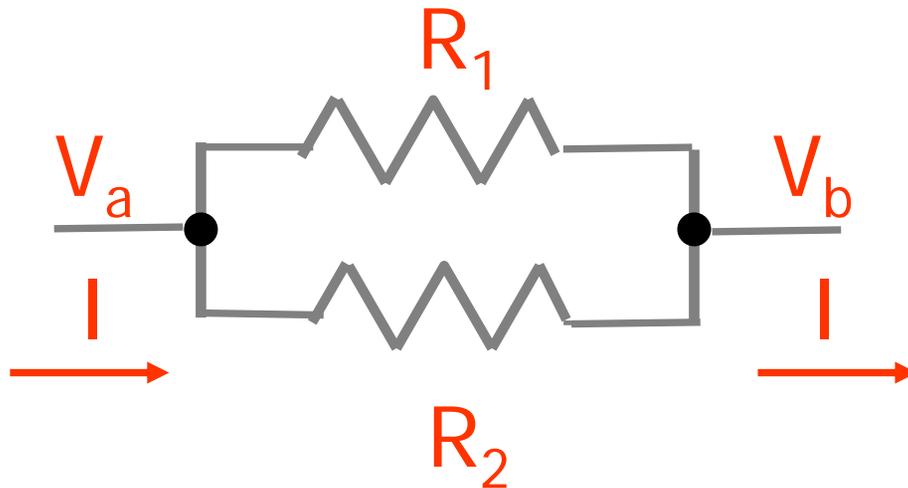

$$I = I_1 + I_2 = V_{ab}/R_1 + V_{ab}/R_2 = V_{ab}/R_{eq}$$


$$\rightarrow \boxed{1/R_{eq} = 1/R_1 + 1/R_2}$$

Electric Circuits

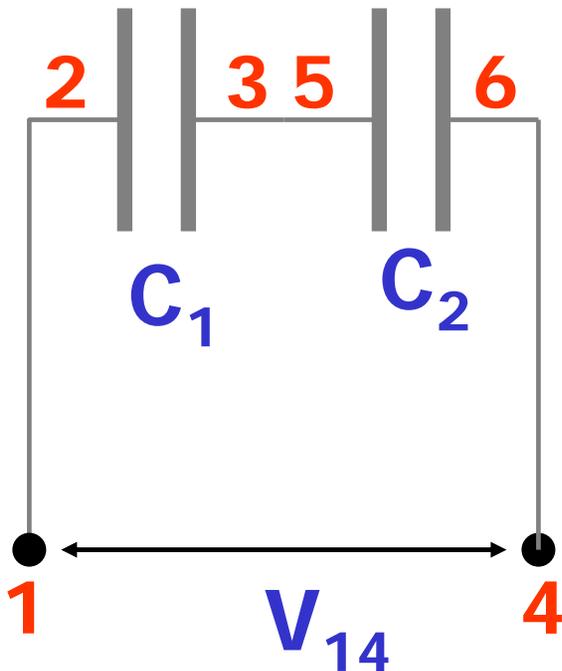

- Two capacitors in **series**
- $V_{14} = V_{23} + V_{56}$
- $Q = Q_1 = Q_2$
- $V_{\text{tot}} = Q_1/C_1 + Q_2/C_2 = Q/(C_1 + C_2)$
- $1/C_{\text{tot}} = 1/C_1 + 1/C_2$
- **Inverse Capacitances add!**

Electric Circuits

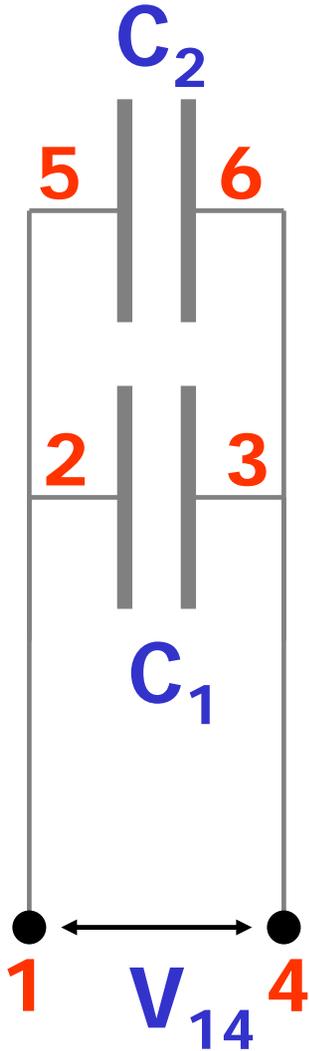


- Two capacitors in **parallel**
- $V_{56} = V_{23} = V_{14}$ (after capacitor is charged)
- $Q_1/C_1 = Q_2/C_2 = V_{14}$
- $Q_{\text{tot}} = Q_1 + Q_2$
- $C_{\text{tot}} = (Q_1 + Q_2)/V_{14} = C_1 + C_2$
- Capacitors in **parallel** -> **Capacitances add!**

Kirchoff's Rules

- Junction rule

At junctions:
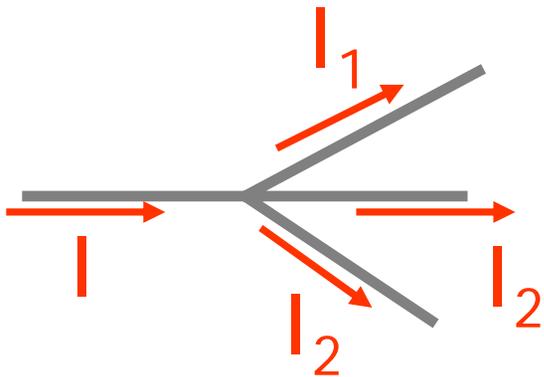
$$\sum I_{\text{in}} = \sum I_{\text{out}}$$



Charge conservation

- Loop rule

Around closed loops:


$$\sum \Delta V_j = 0$$

ΔV for both EMFs
and Voltage drops

Energy conservation

Kirchoff's Rules

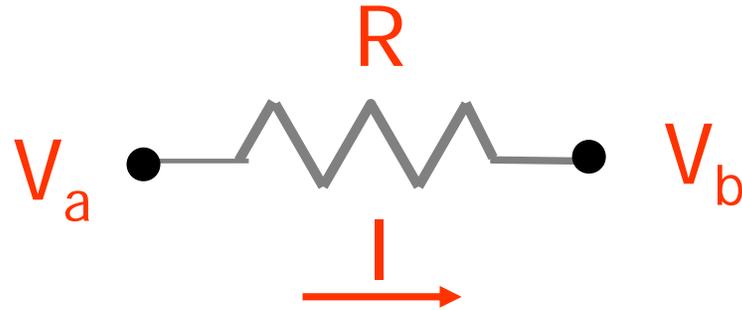
- Kirchoff's rules allow us to calculate currents for complicated DC circuits
- Main difficulty: Signs!
- Rule for resistors:



$\Delta V = V_b - V_a = - I R$, if we go in the direction of I (voltage drop!)


Kirchoff's Rules

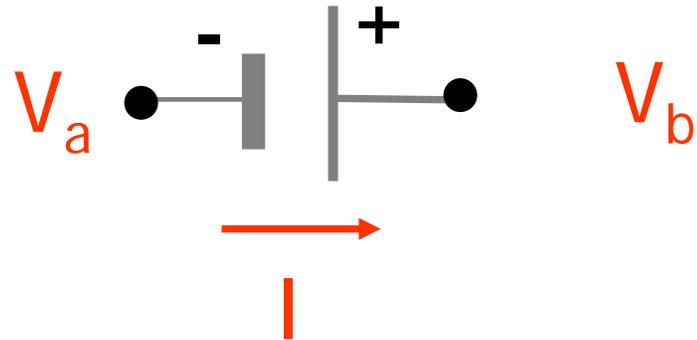- Kirchoff's rules allow us to calculate currents for complicated DC circuits
- Main difficulty: Signs!
- Rule for EMFs:



$$\Delta V = V_b - V_a = \xi, \text{ if we go in the direction of } I$$

Example

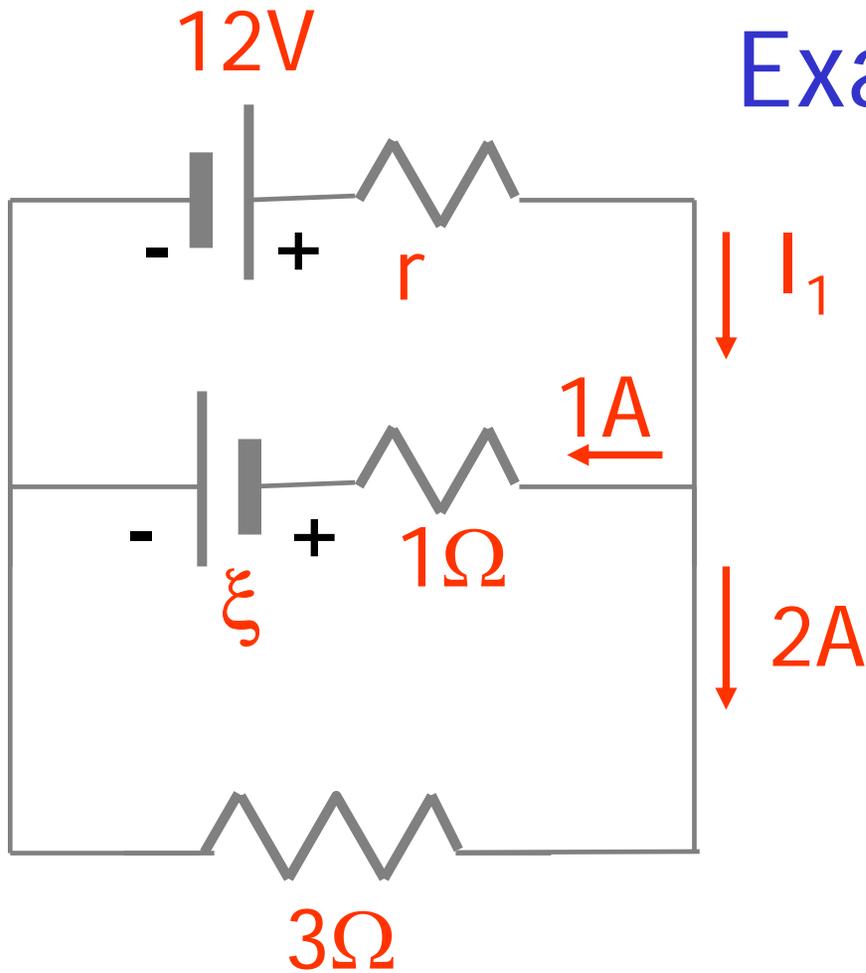


r, ξ, I_1 ? 3 unknowns

- Pick signs for I_1, ξ
- Junction rule
$$I_1 = 1A + 2A = 3A$$
- Loop rule (1)
$$12V - 6V - 3A r = 0$$
$$\rightarrow r = 6/3 \Omega = 2 \Omega$$
- Loop rule (2)
$$12V - 6V - 1V - \xi = 0$$
$$\rightarrow \xi = 5V$$

RC Circuits

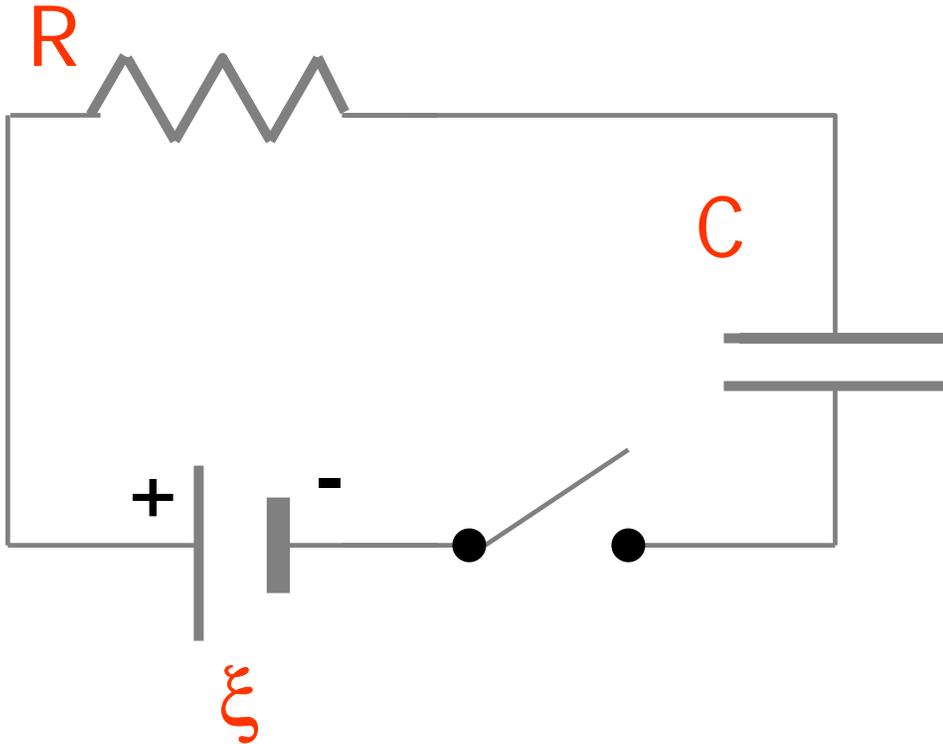
- Currents change with time
- Example: Charging a capacitor



$$\begin{aligned}t &= 0 \\q &= 0 \\V_c &= q/C\end{aligned}$$

RC Circuits

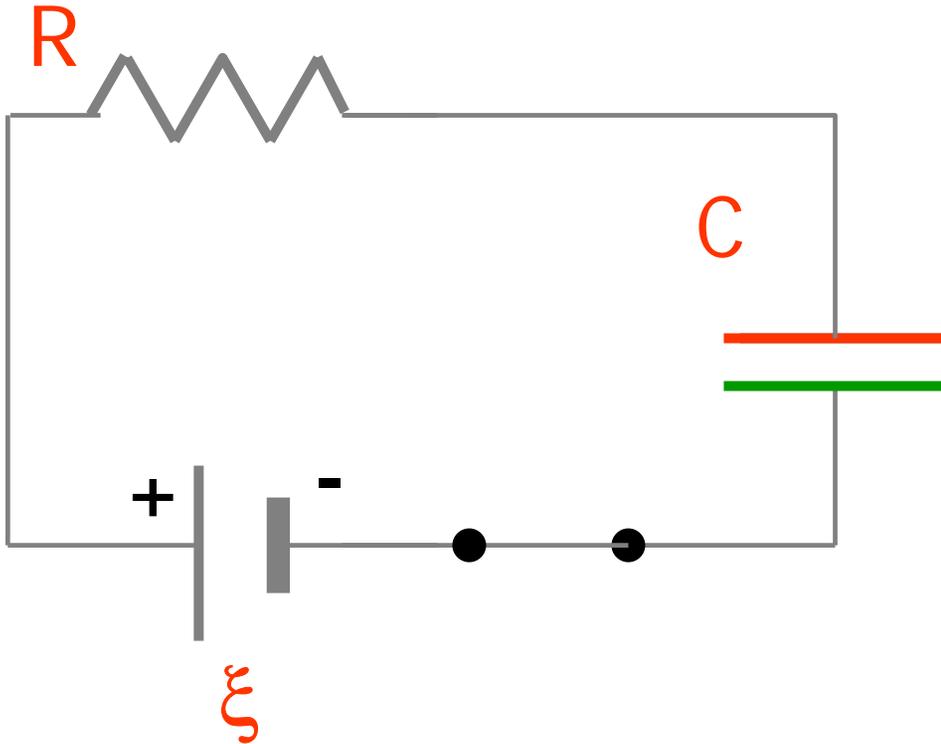
- Currents change with time
- Example: Charging a capacitor






$$t = \text{infinity}$$
$$q = C \xi$$
$$V_c = q/C = \xi$$

RC Circuits

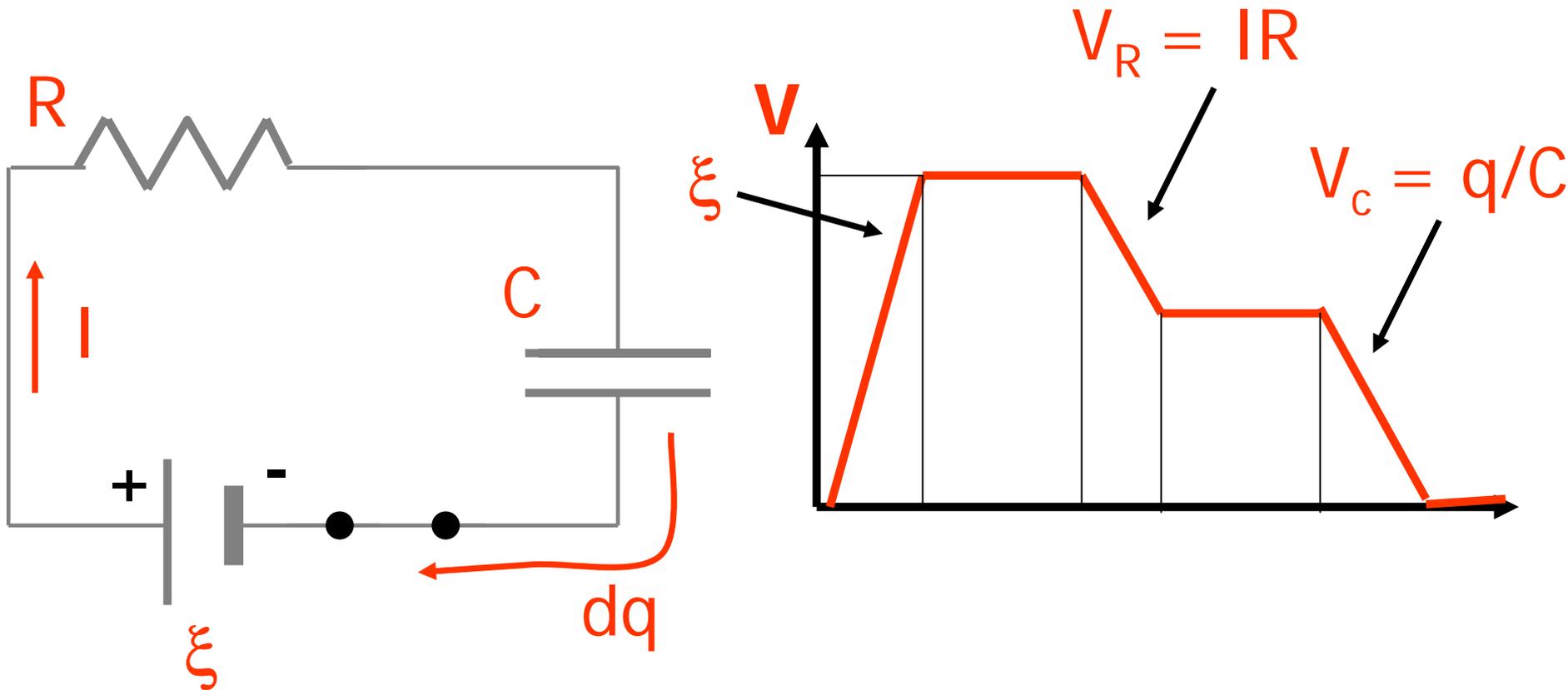- What happens between $t=0$ and infinity?



Charging C

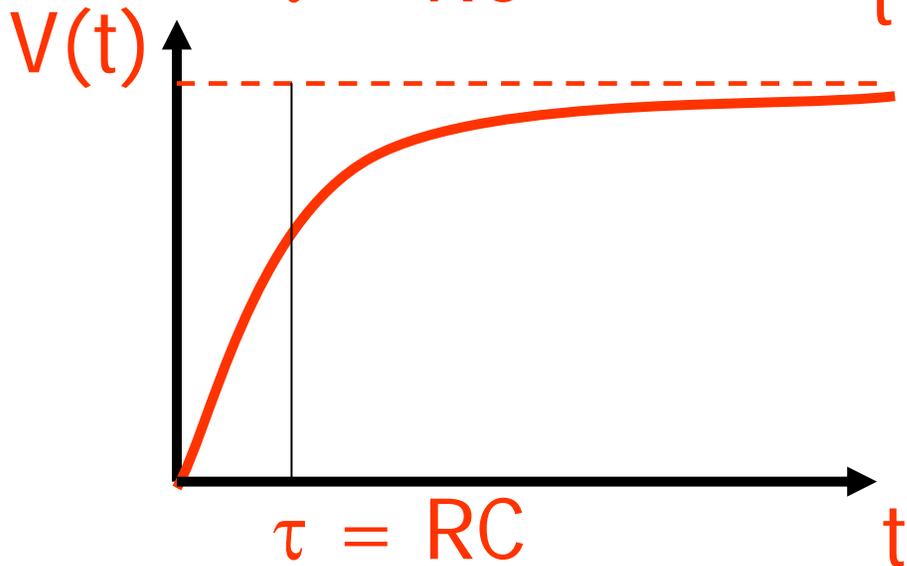
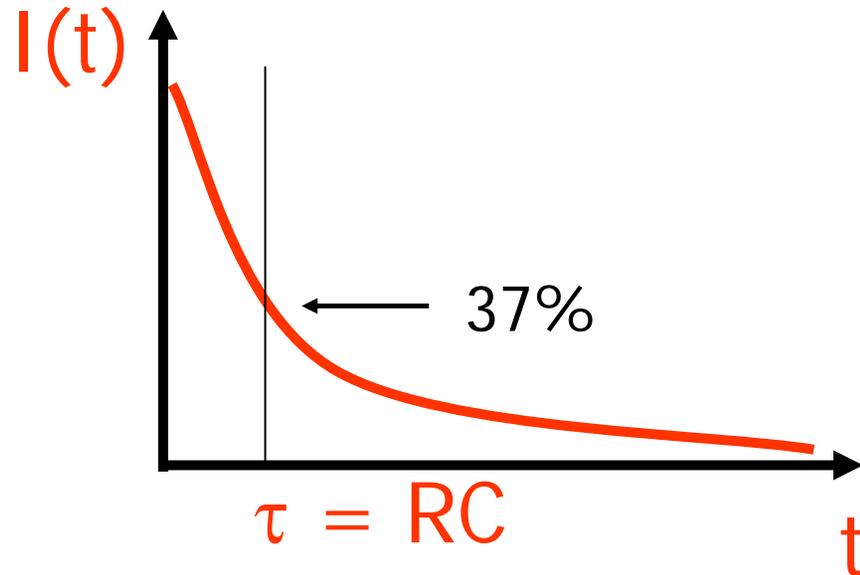
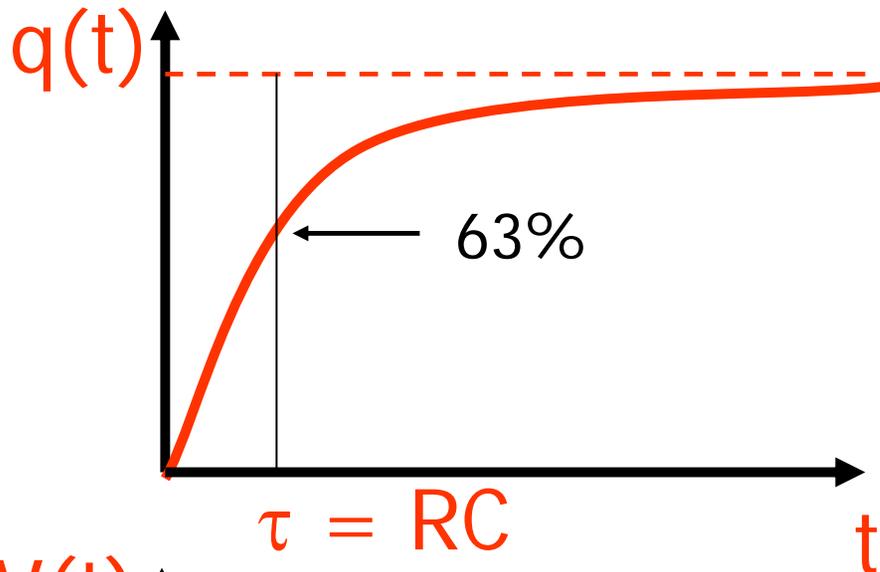


$$q(t) = \xi C [1 - \exp(-t/\tau)]$$

$$I(t) = dq/dt = \xi/R \exp(-t/\tau)$$

$$V(t) = \xi [1 - \exp(-t/\tau)]$$

Charging C

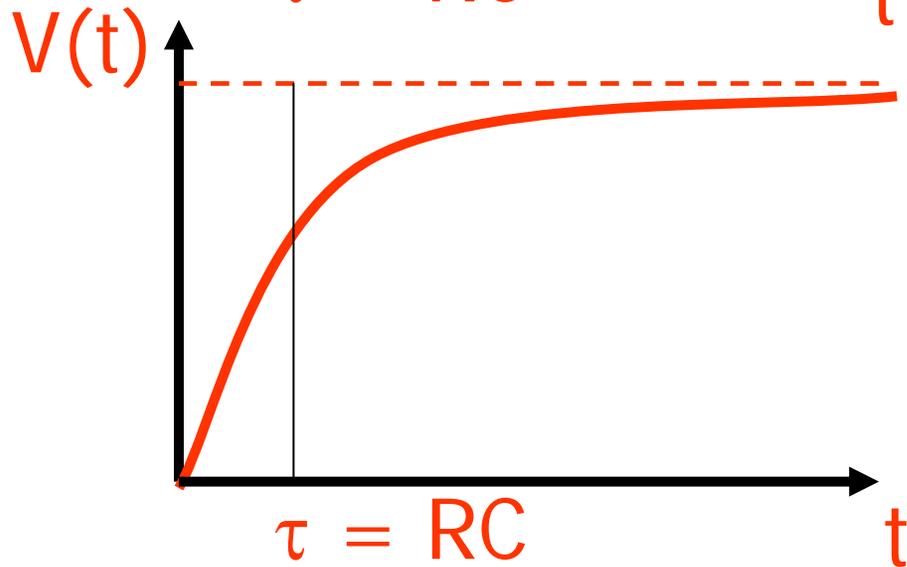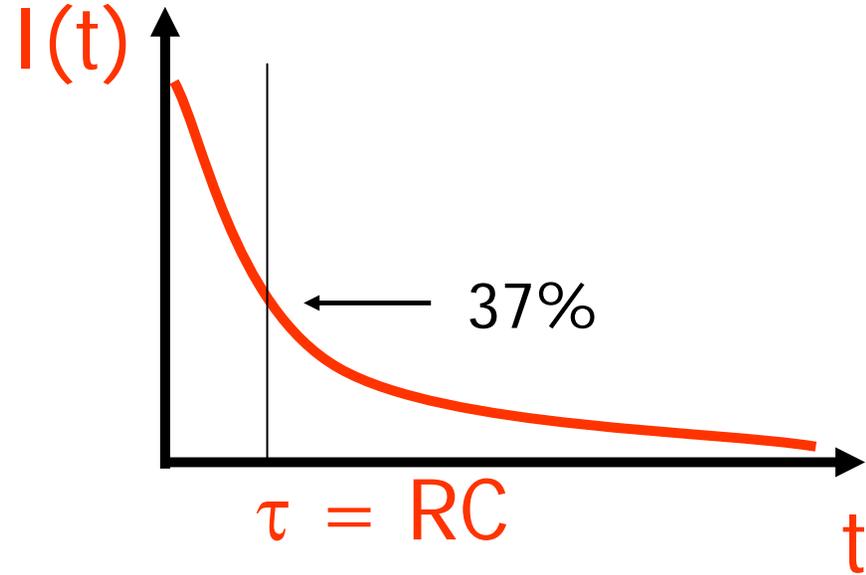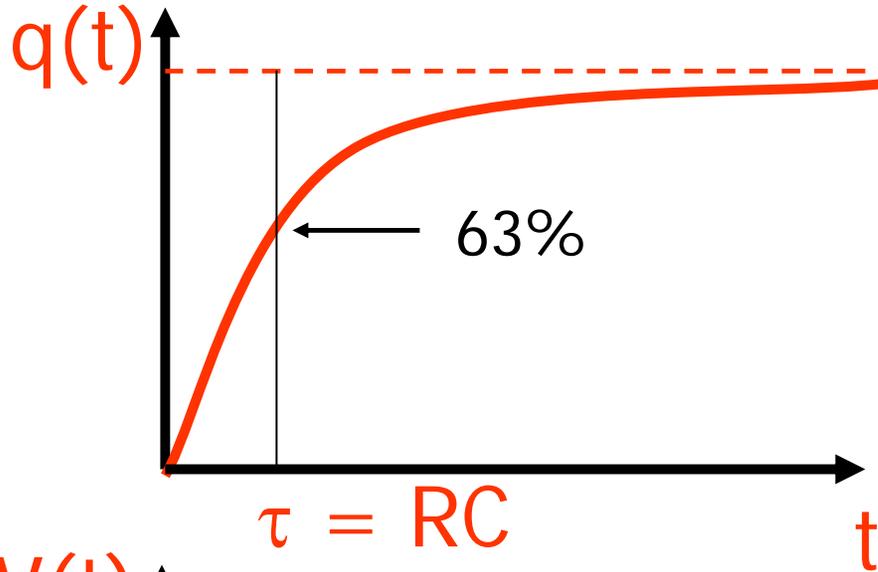


At $t = \tau$,




$$q(t) = (1 - 1/e) q_{\max}$$
$$= \underline{63 \%} \underline{q_{\max}}$$

In-Class Demo

Discharging a capacitor

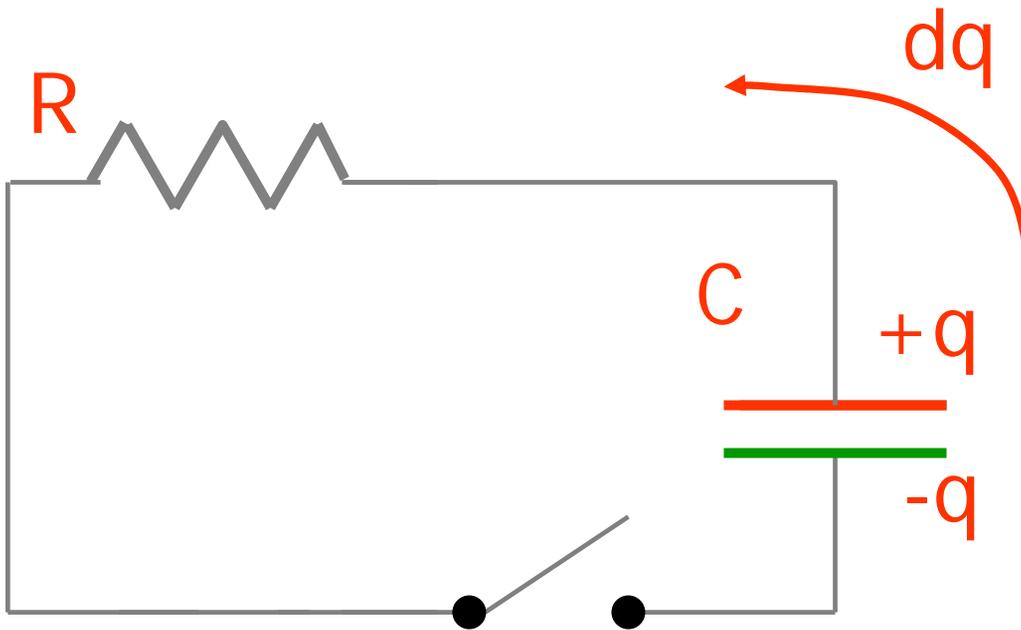

Discharging C

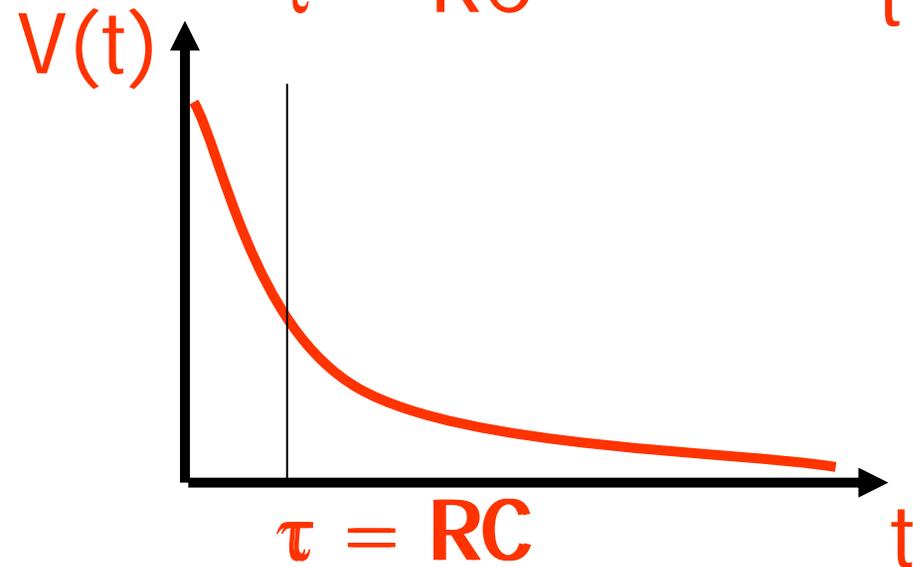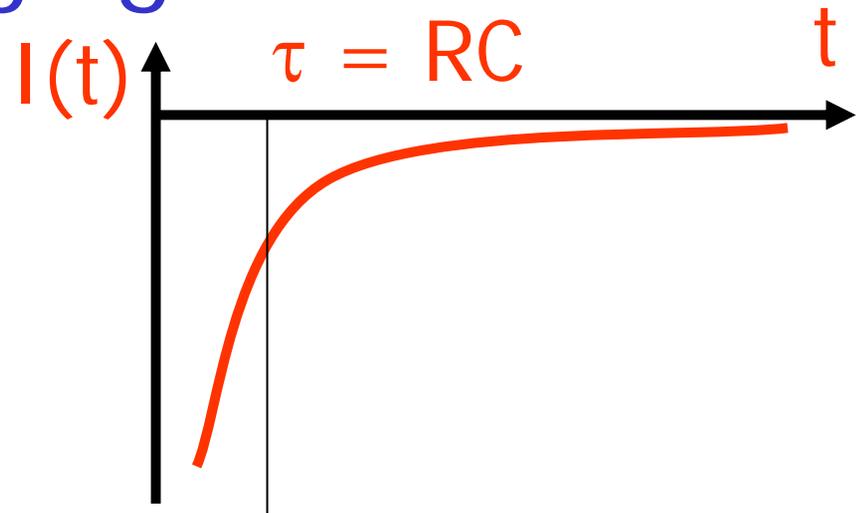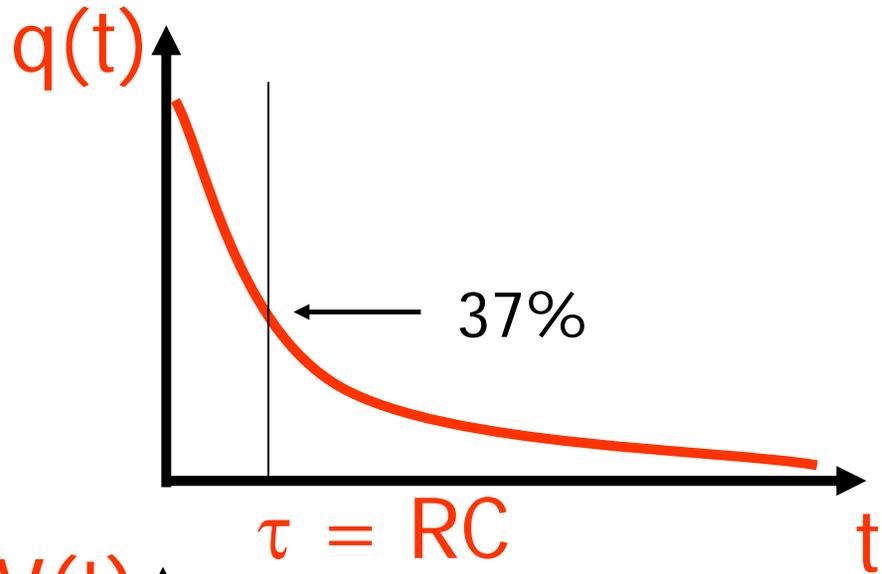


$$q(t) = \xi C \exp(-t/\tau)$$

$$I(t) = dq/dt = -\xi/R \exp(-t/\tau)$$

$$V(t) = \xi \exp(-t/\tau)$$

Experiment EF

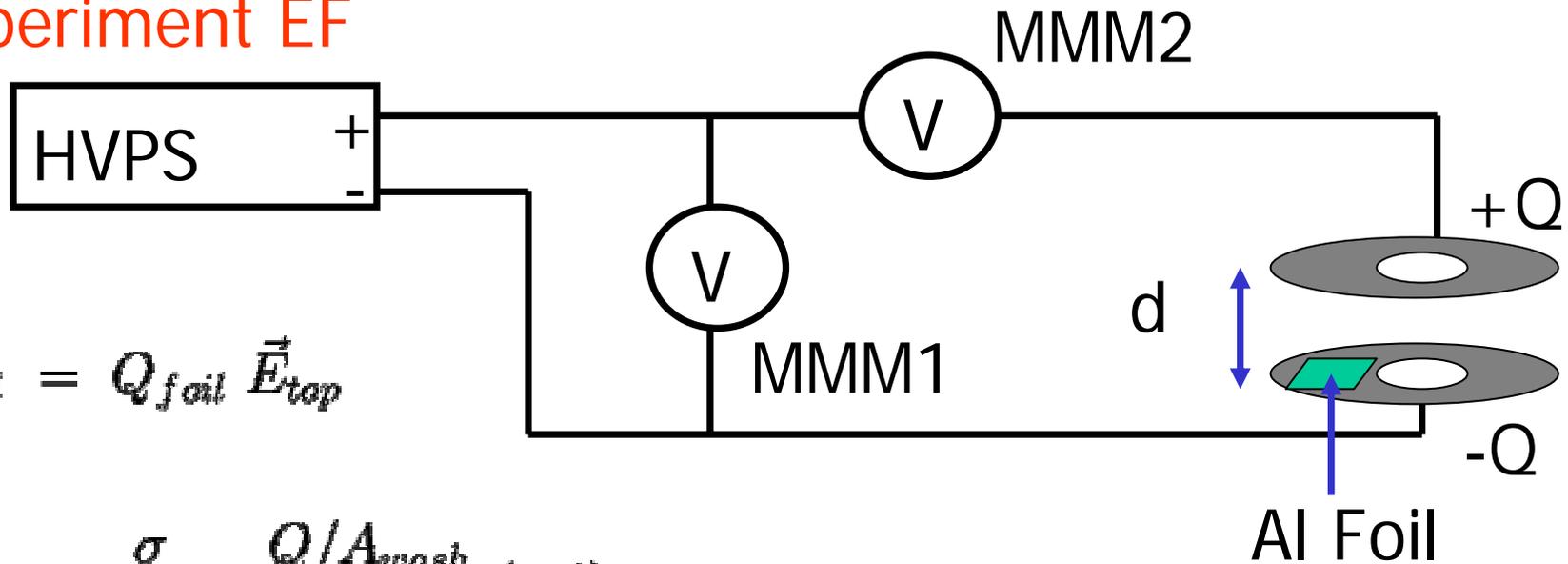

$$\vec{F}_{on\,foil} = Q_{foil} \vec{E}_{top}$$

$$\vec{E}_{top} = \frac{\sigma}{2\epsilon_0} = \frac{Q/A_{wash}}{2\epsilon_0} (-\hat{y})$$

$$Q_{foil} = -Q \frac{A_{foil}}{A_{wash}}$$

$$Q = CV = \epsilon_0 A/d V$$

$$\Rightarrow \vec{F}_{on\,foil} = -Q \frac{A_{foil}}{A_{wash}} \frac{Q}{A_{wash} 2\epsilon_0} (-\hat{y}) \Rightarrow \vec{F}_{on\,foil} = \frac{(\epsilon_0 V A_{wash}/d)^2}{A_{wash}^2} \frac{A_{foil}}{2\epsilon_0} \hat{y}$$

$$= \frac{Q^2}{A_{wash}^2} \frac{A_{foil}}{2\epsilon_0} \hat{y}$$

$$= \frac{\epsilon_0 V^2}{2d^2} A_{foil} \hat{y}$$