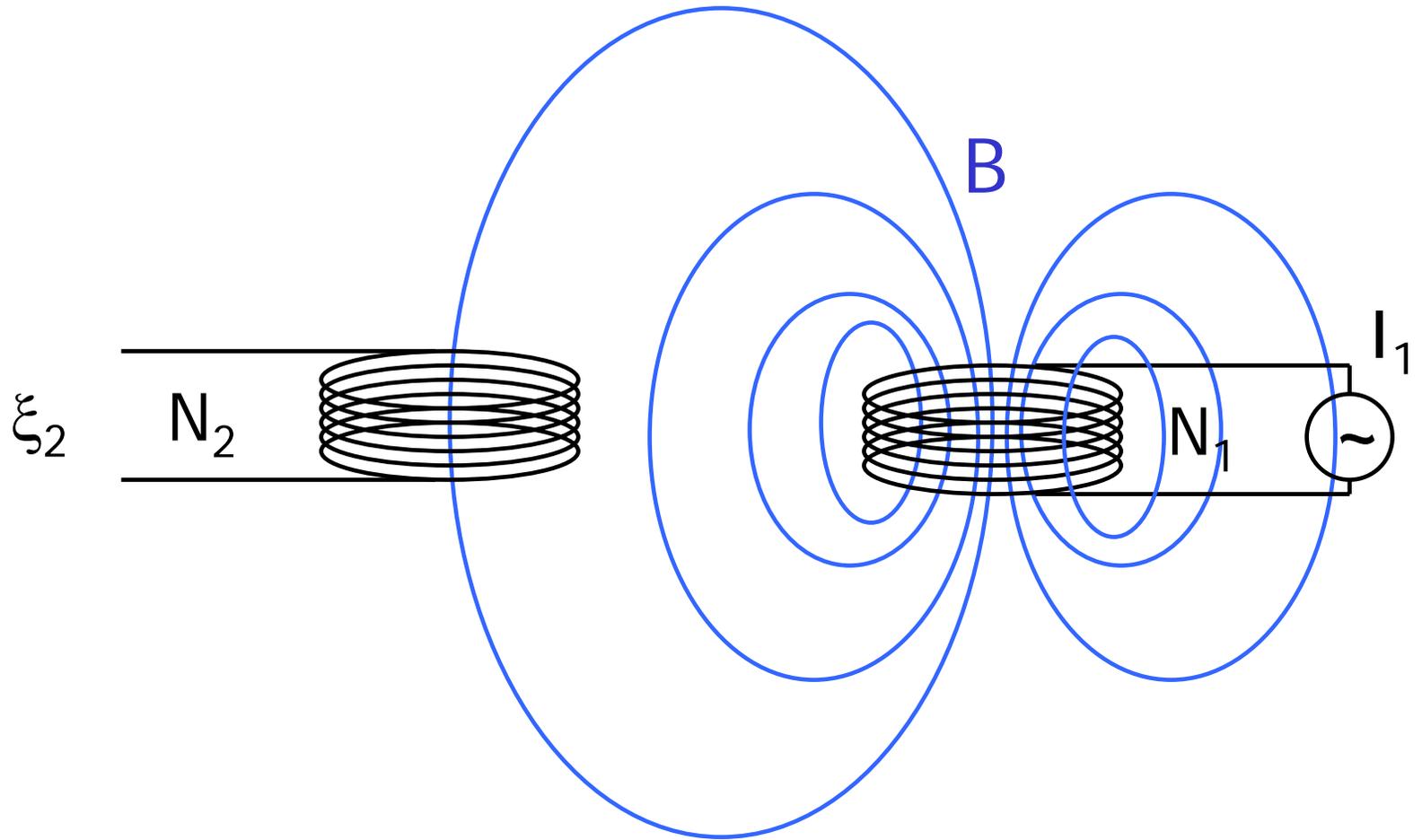


Electricity and Magnetism

- Reminder
 - Mutual- and Self-Inductance
 - Inductance and AC circuits
 - Phase shift between $I(t)$ and $V(t)$
- Today
 - RL circuits
 - Energy in B-Field


Inductance



Inductance

$$\xi_2 = - N_2 \frac{d\Phi_B}{dt} = - M \frac{dI_1}{dt}$$

$$\text{with } M = N_2 \Phi_B / I_1$$

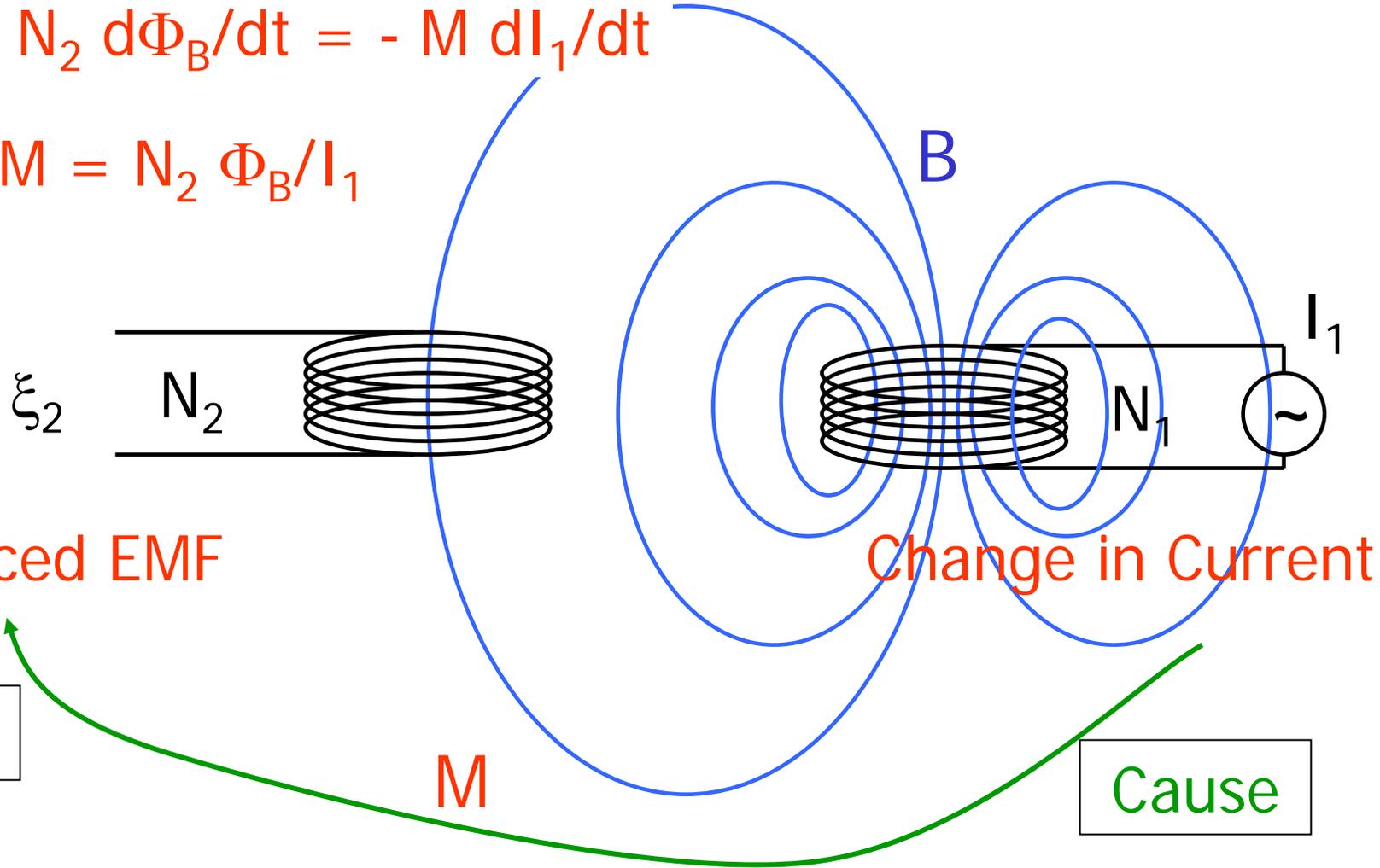


Mutal Inductance

- Coupling is symmetric: $M_{12} = M_{21} = M$
- M depends only on Geometry and Material
- Mutual inductance gives strength of coupling between two coils (conductors):

$$\xi_2 = - N_2 d\Phi_B/dt = - M dI_1/dt$$


- M relates ξ_2 and I_1 (or ξ_1 and I_2)
- Units: $[M] = V/(A/s) = V s /A = H$ ('Henry')

In-Class Demo: Two Coils

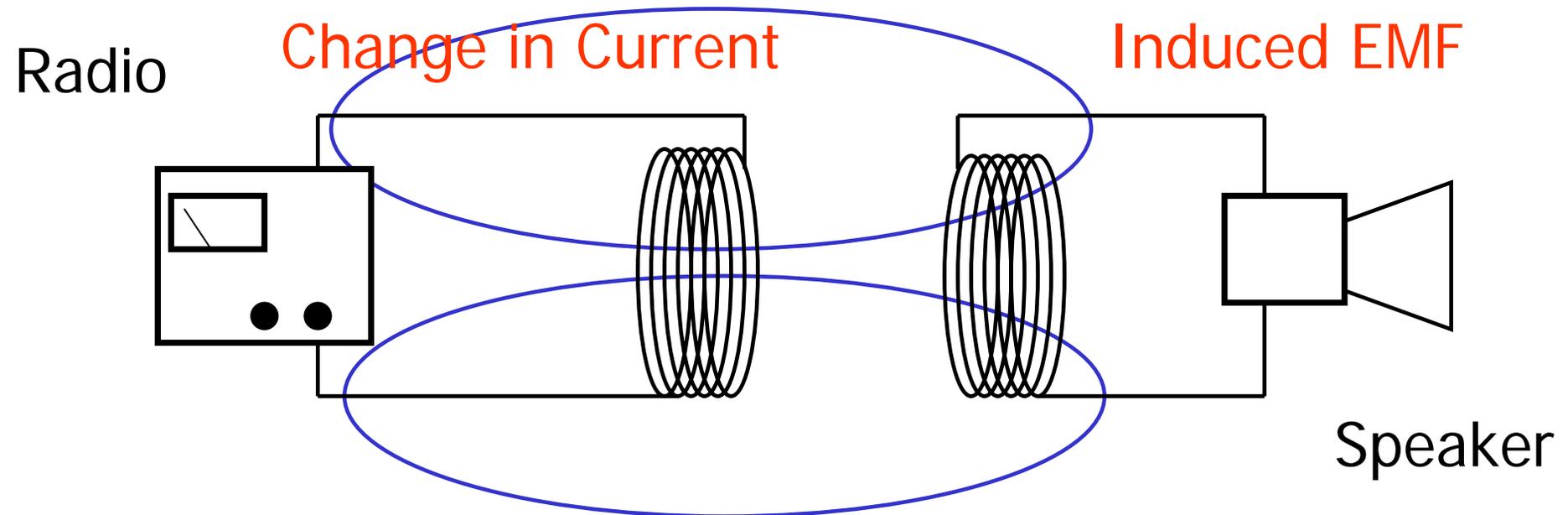


- Signal transmitted by varying Field
- Coupling depends on Geometry (angle, distance)

In-Class Demo: Levitating Coil

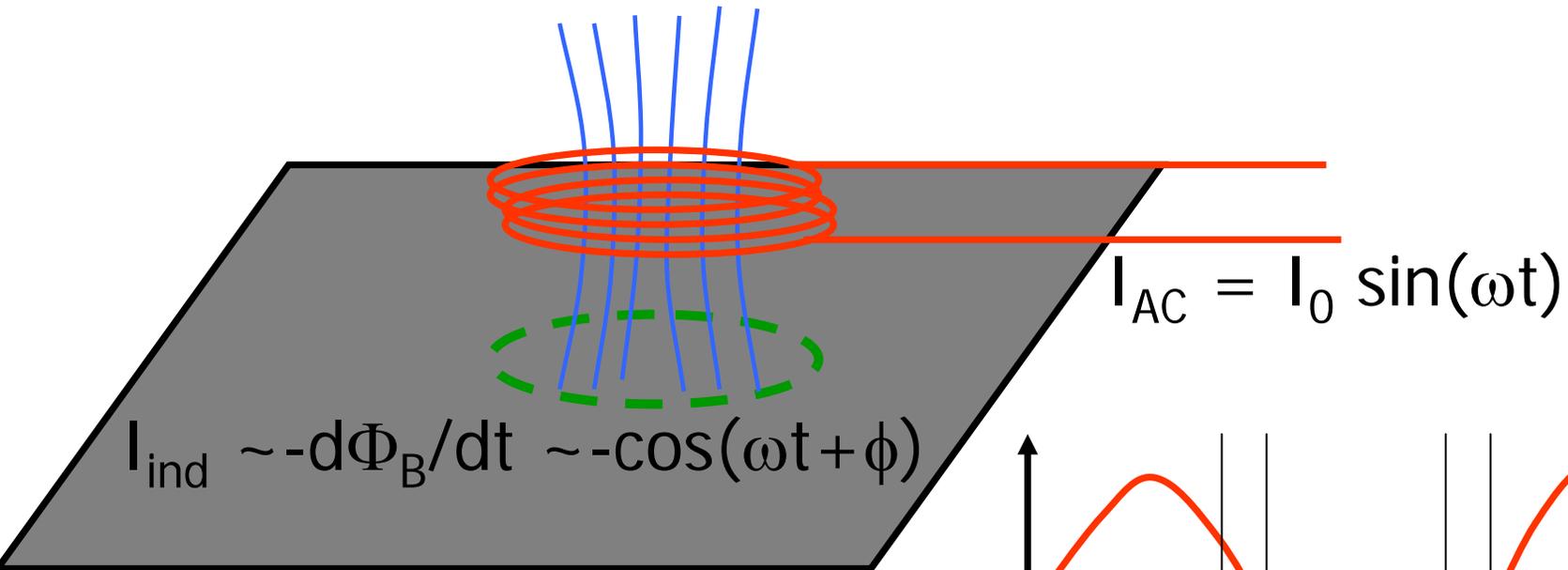


With delay ($\phi > 0$):

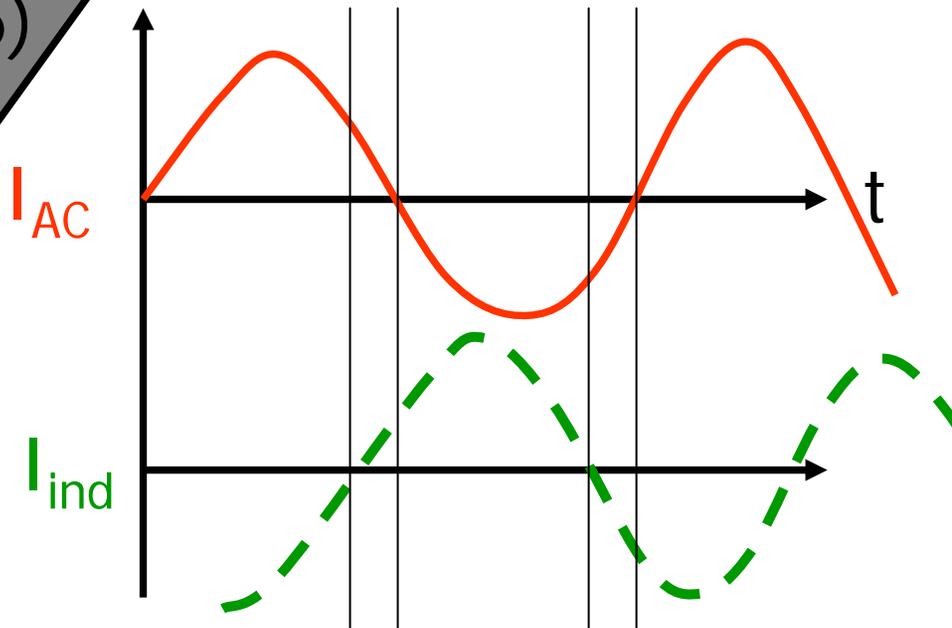Net repulsion (currents are opposite most of the time)



Self Inductance

Circuit sees flux generated by it self

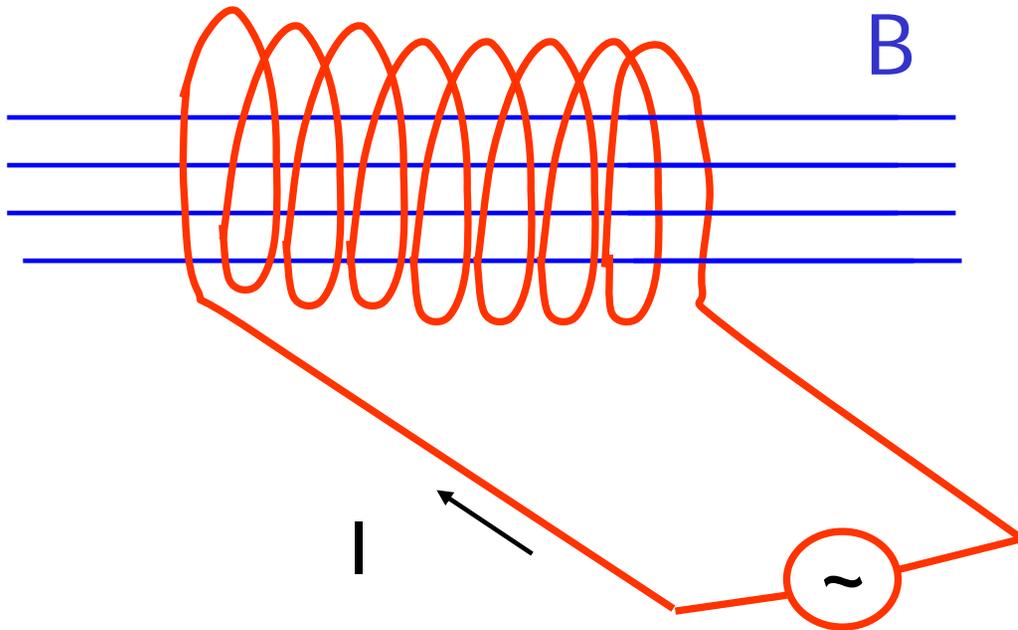

Def.: $L = N \Phi_B / I$

Self-Inductance

Example: Solenoid

Q: How big is L ?

A: $L = \mu_0 N^2 A / L$



Self Inductance

- L is also measured in [H]
- L connects induced EMF and variation in current:

$$\xi = - L \, dI/dt$$

- Remember Lenz' Rule:
 - Induced EMF will 'act against' change in current -> effective 'inertia'
- Delay between current and voltage

RL Circuits

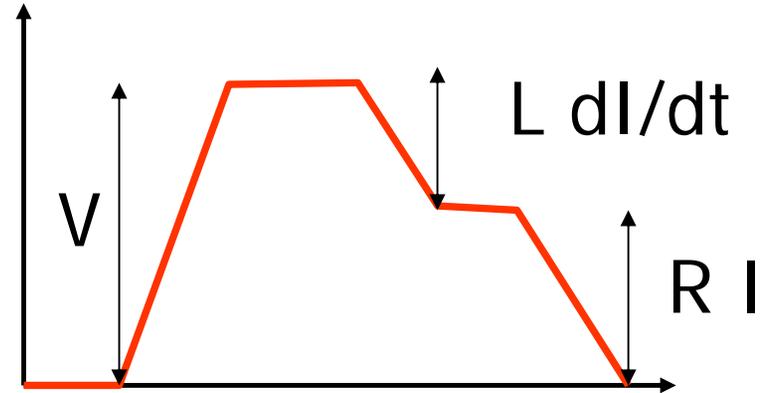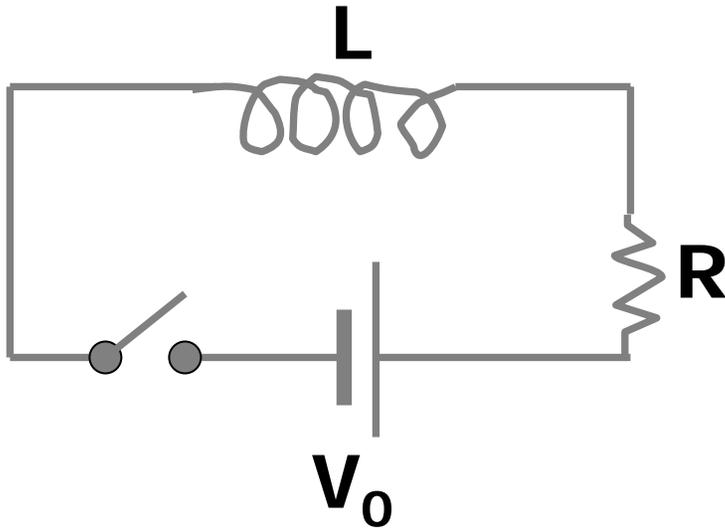


Kirchoffs Rule: $V_0 + \xi_{\text{ind}} = R I \rightarrow V_0 = L \frac{dI}{dt} + R I$


Q: What is $I(t)$? Note: Not an AC circuit

A: $I(t) = V_0/R [1 - \exp(-t/\tau)]$ with $\tau = L/R$

RL Circuits

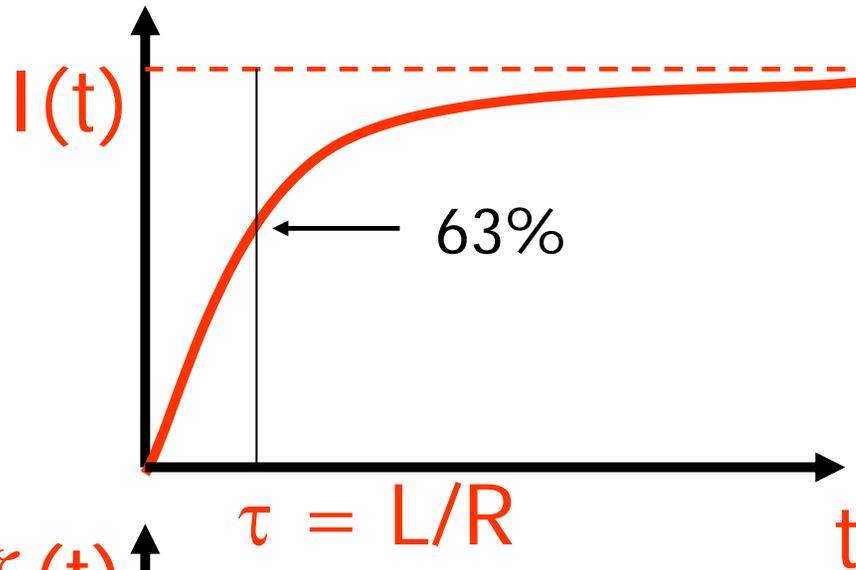

$$I(t) = V_0/R [1 - \exp(-t/\tau)]$$

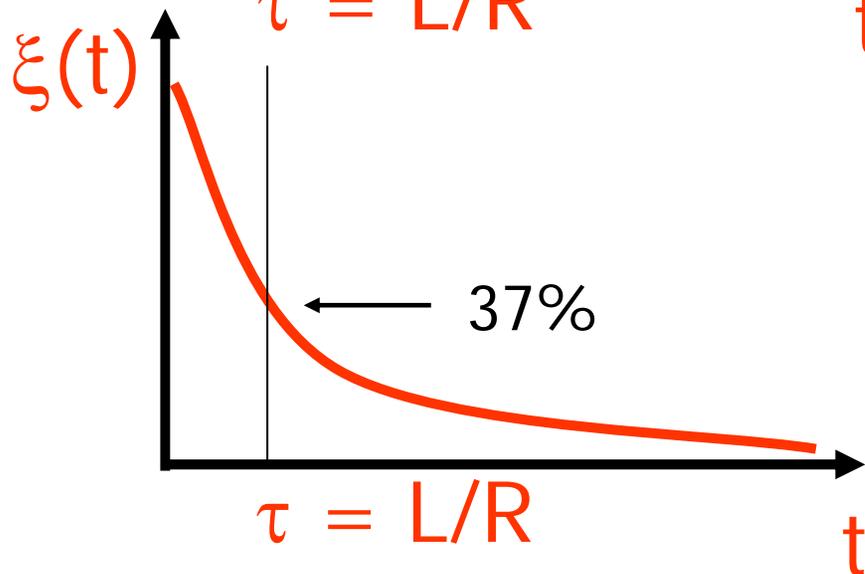


$$\xi(t) = V_0 \exp(-t/\tau)$$

RL Circuits


- Inductance leads to 'delay' in reaction of current to change of voltage V_0
- All practical circuits have some L and R
 - change in I never instantaneous

In-Class Demo: Large L

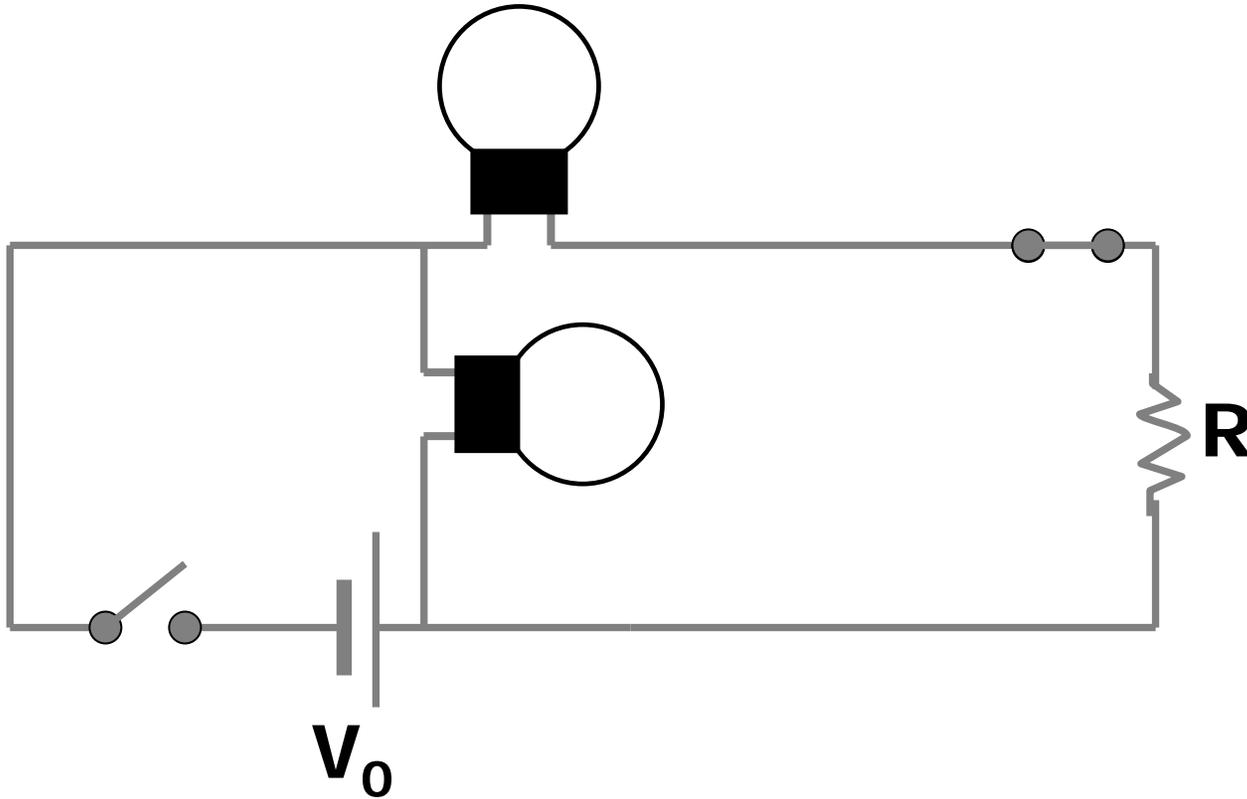


First: No L

In-Class Demo: Large L

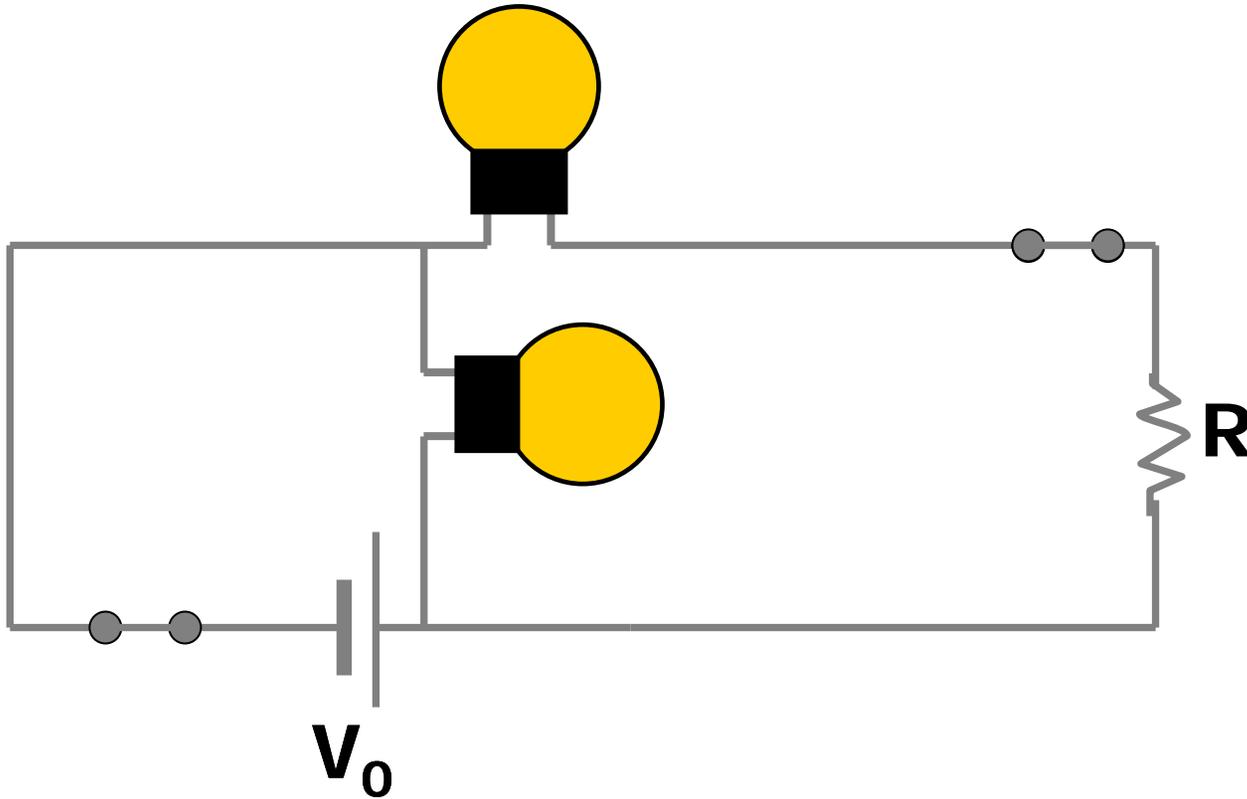


First: No L - no delay between I and V

In-Class Demo: Large L

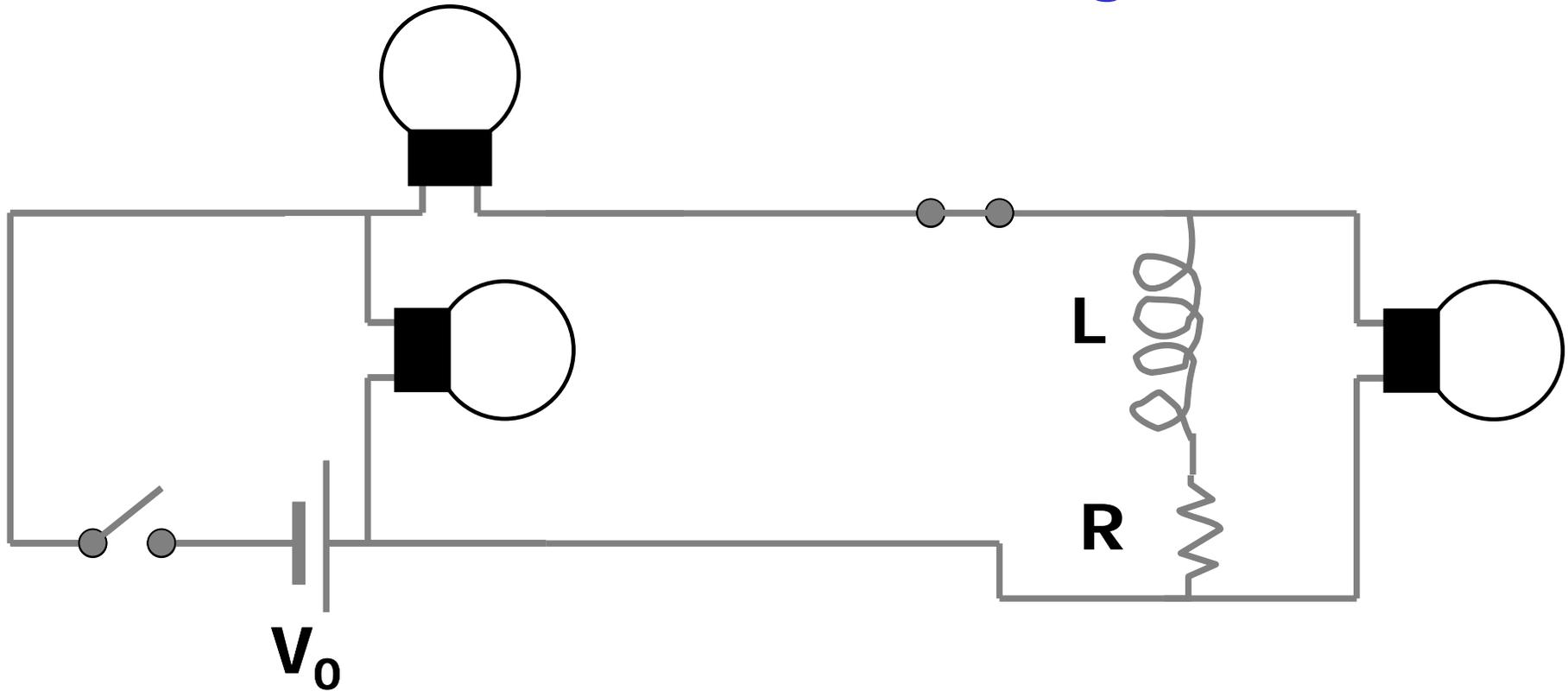


Then: Large L (30H)

In-Class Demo: Large L

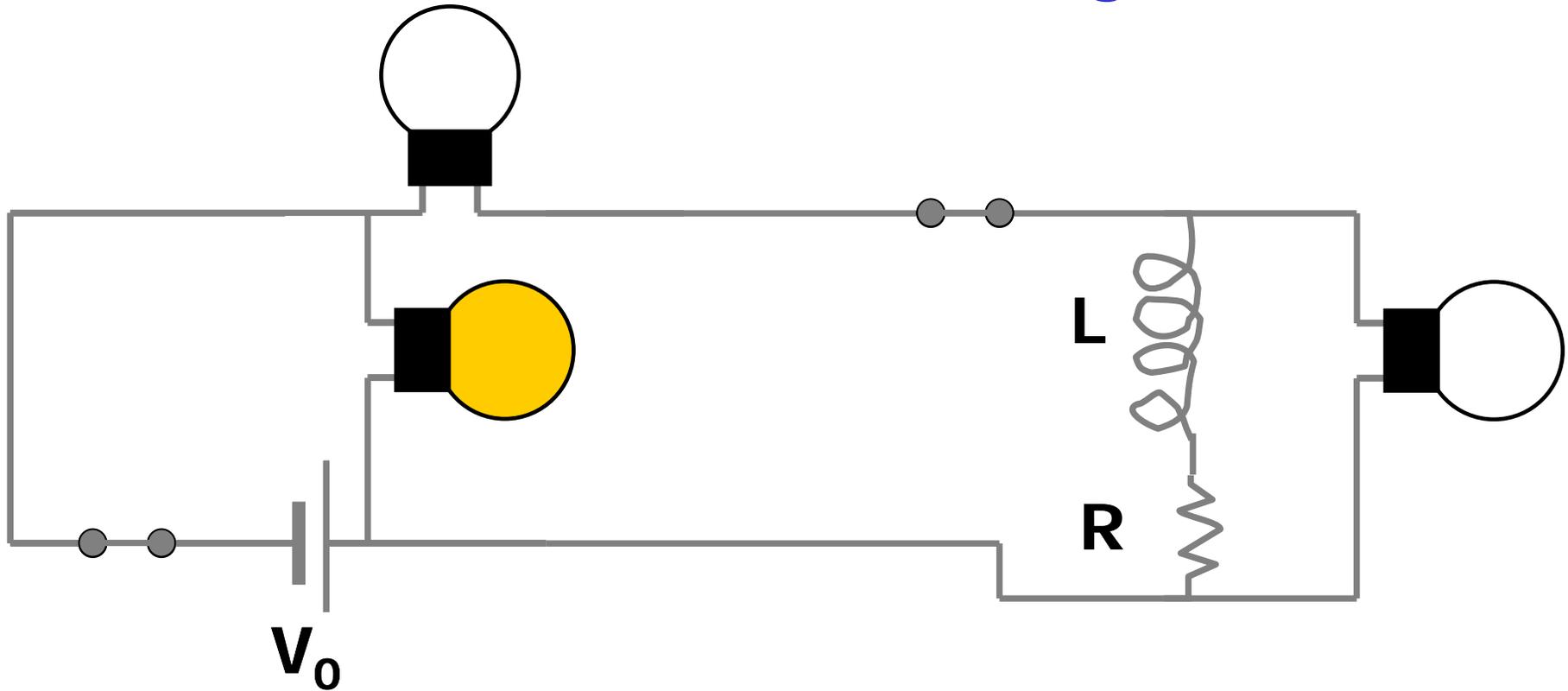


Then: Large L (30H)

In-Class Demo: Large L

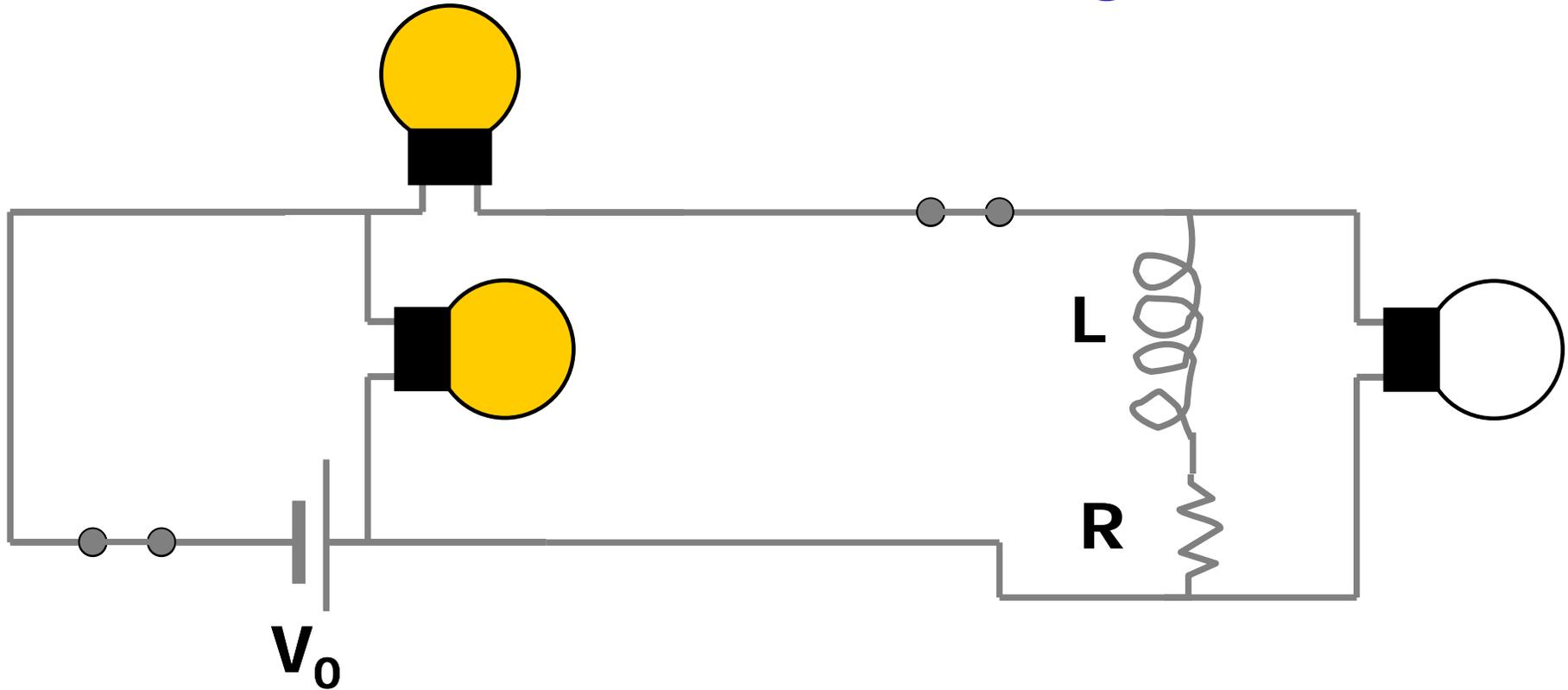


Then: Large L (30H)

In-Class Demo: Large L

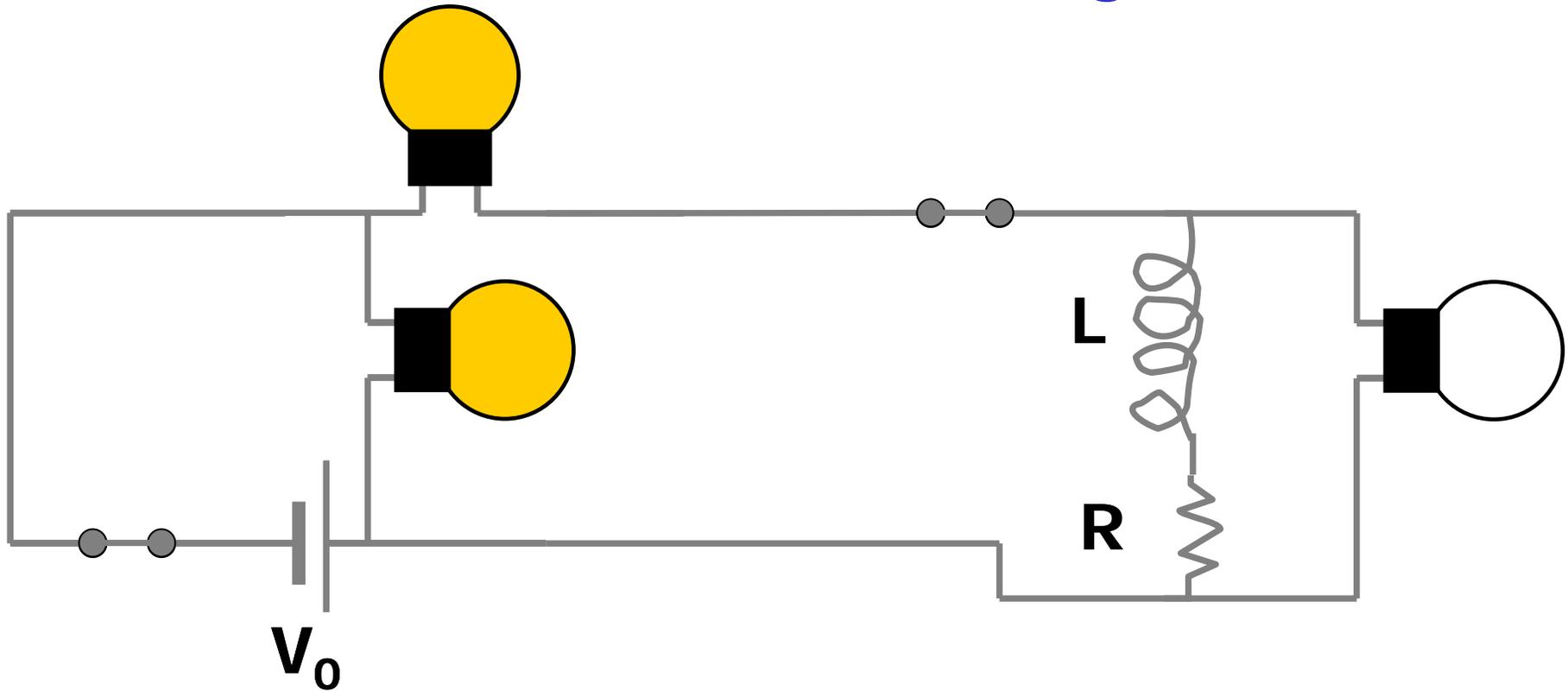


Then: Large L (30H) - Delay in I

In-Class Demo: Large L

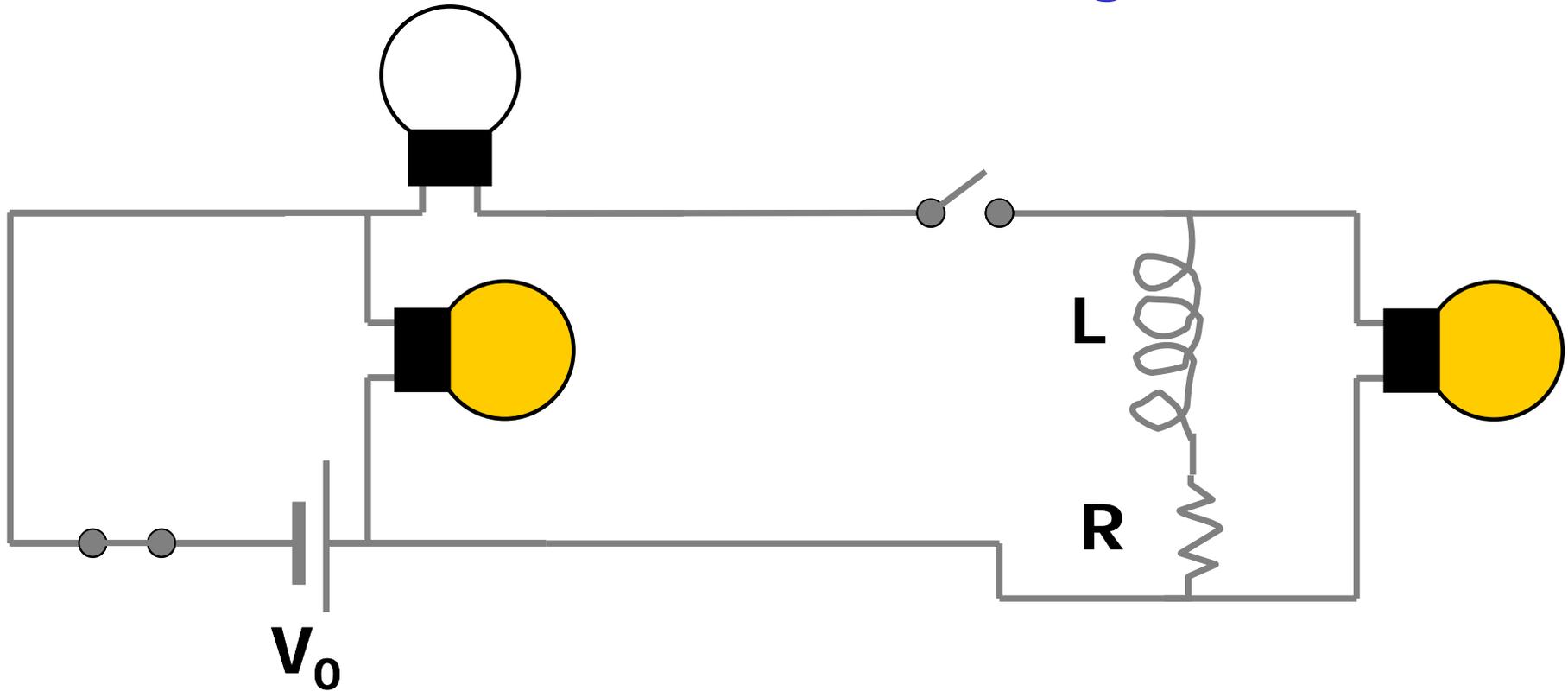


Then: Large L (30H)

In-Class Demo: Large L

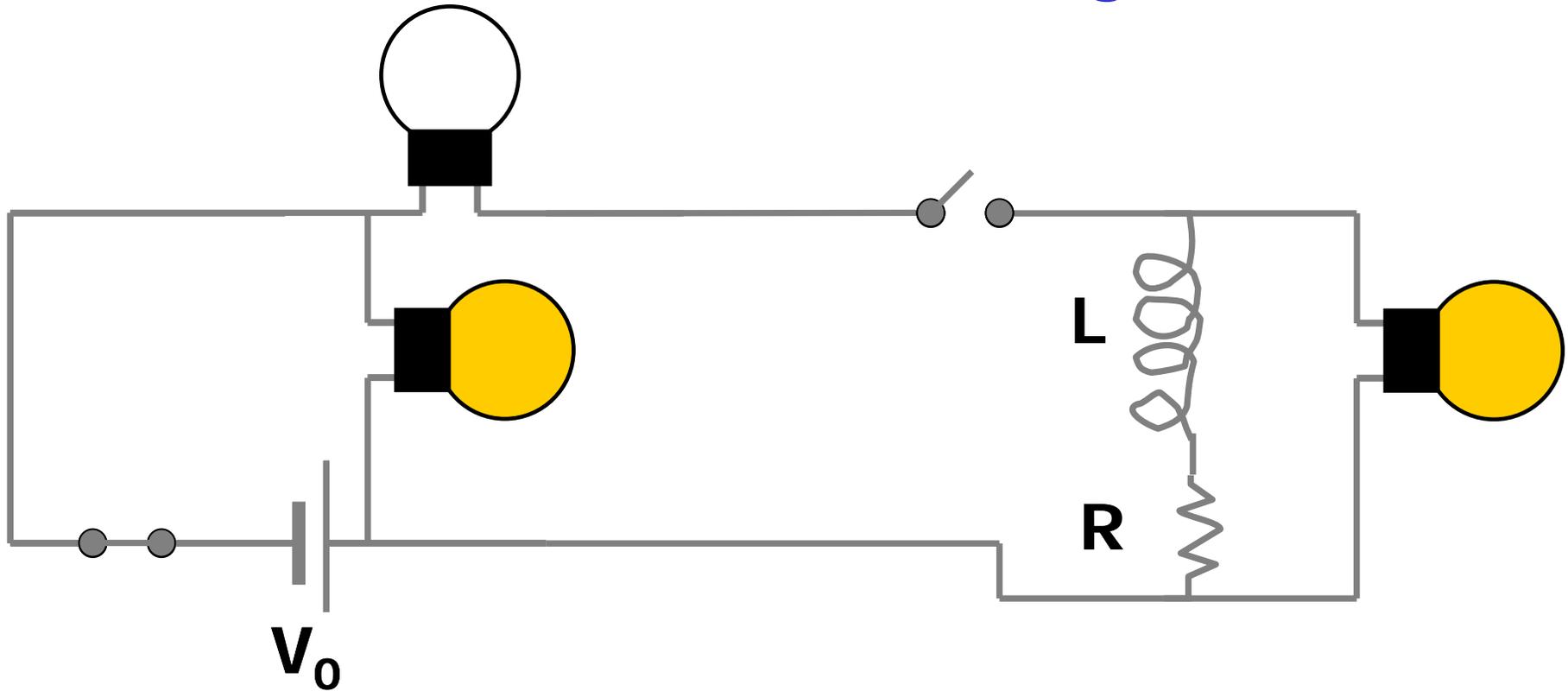

Then: Large L (30H)

In-Class Demo: Large L

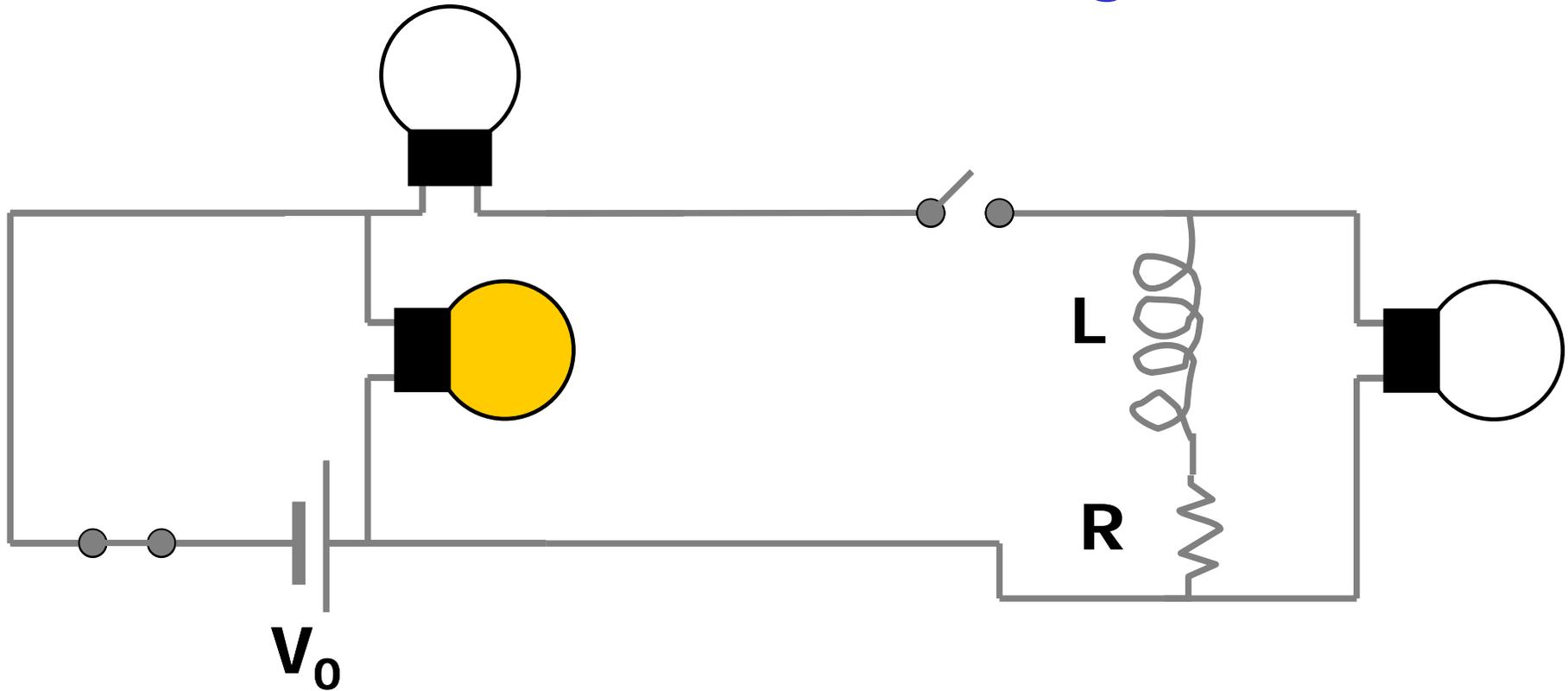


Then: Large L (30H)


In-Class Demo: Large L

- L counteracts change in current both ways
 - Resists increase in I when closing switch
 - Resists decrease in I when opening switch
 - 'Back EMF'
- That's what causes spark when switching off e.g. appliance, light


'Back EMF'

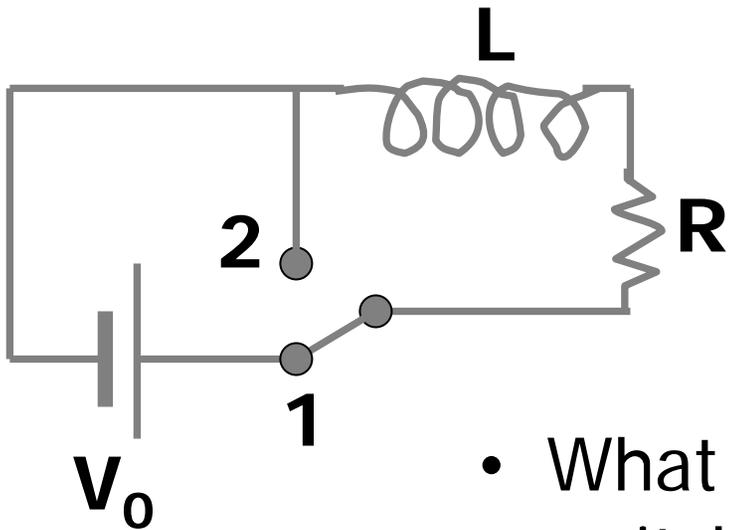

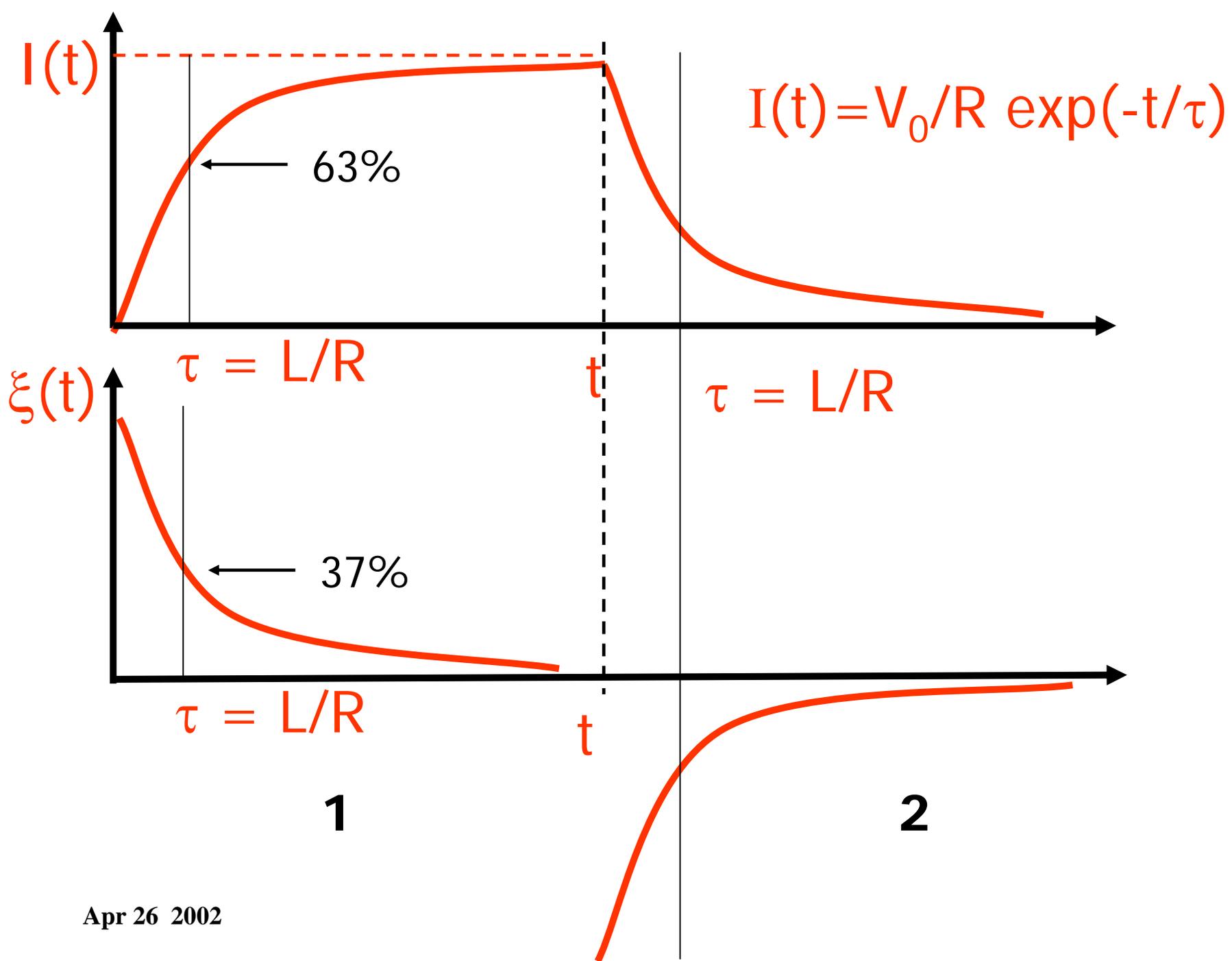
- What happens if we move switch to position 2?




In-Class Demo: Square Wave V_0

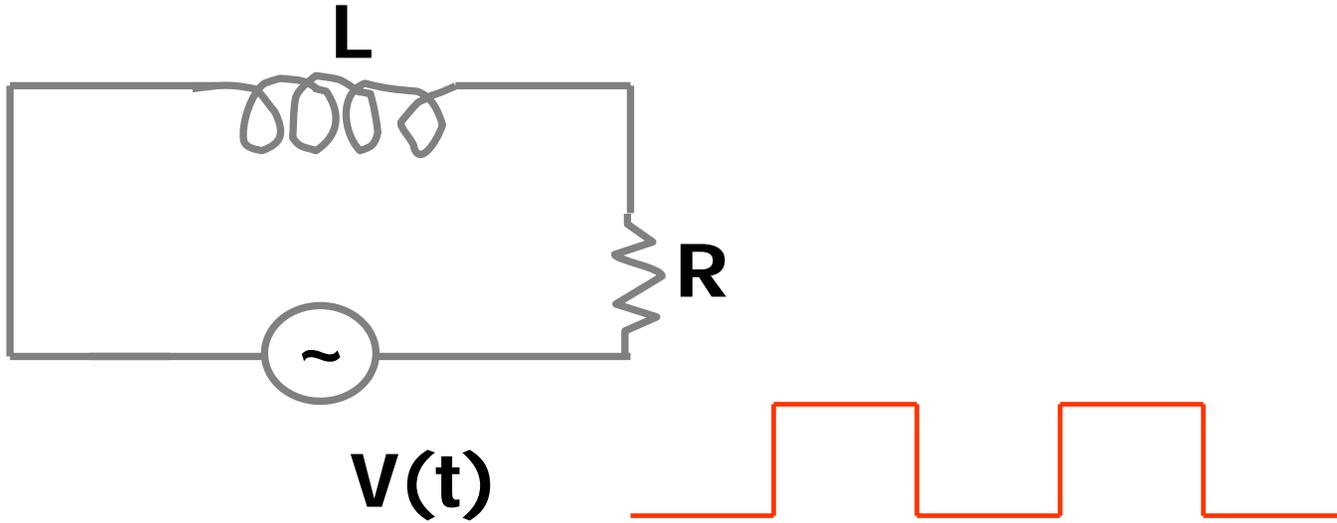

In-Class Demo

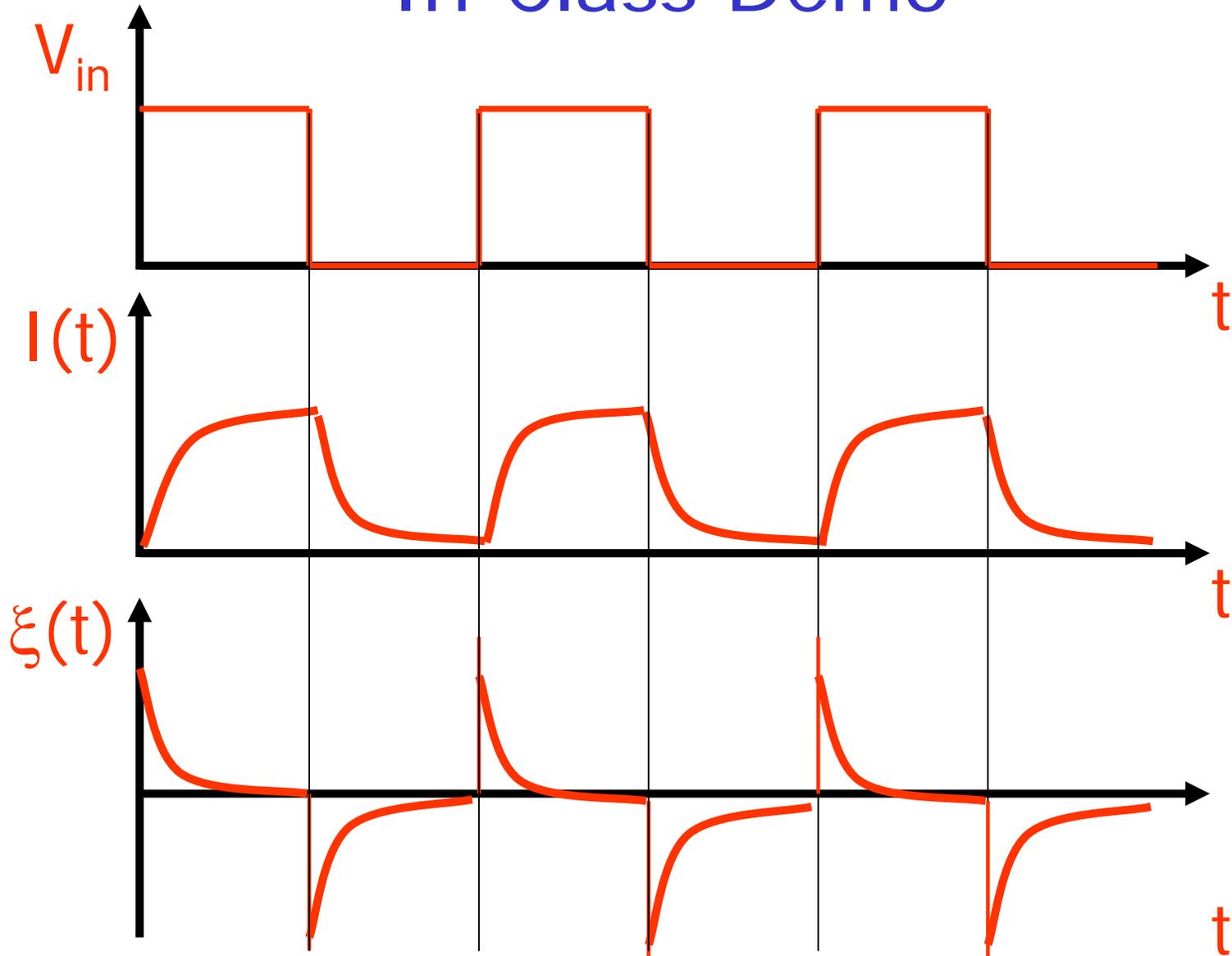

In-Class Demo

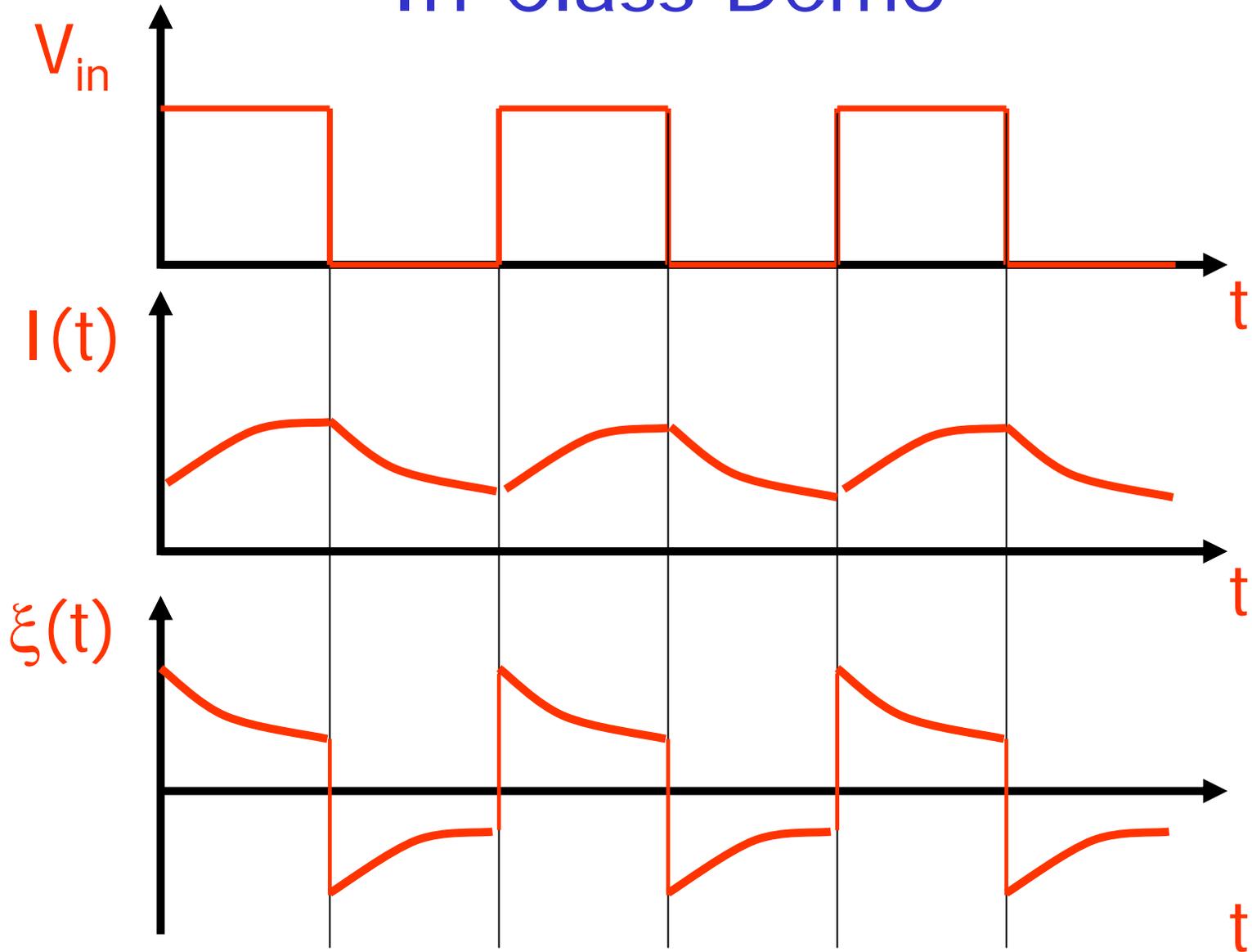

RL as low-pass filter

- Again, like RC circuits, RL circuits act as low-pass filters
- Sharp edges/high frequencies are removed
 - > In-Class Demo...
- RC circuit: Energy gets stored in C when Voltage switched on, released when Voltage switched off
- Energy storage in RL circuits?

Energy Storage in Inductor

- Power $P = |\xi I| = L \, dI/dt \, I = dU/dt$

-> $dU = L \, dI \, I$

-> $U = \frac{1}{2} L I^2$

- Where is the Energy stored?

$$U/\text{Volume} = \frac{1}{2} B^2/\mu_0$$


Summary of Circuit Components



$$\mathbf{V} \quad \mathbf{V(t)}$$



$$\mathbf{R} \quad \mathbf{V_R = IR}$$

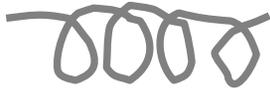

$$\mathbf{L} \quad \mathbf{V_L = L \, dI/dt}$$



$$\mathbf{C} \quad \mathbf{V_C = 1/C \int I dt}$$