
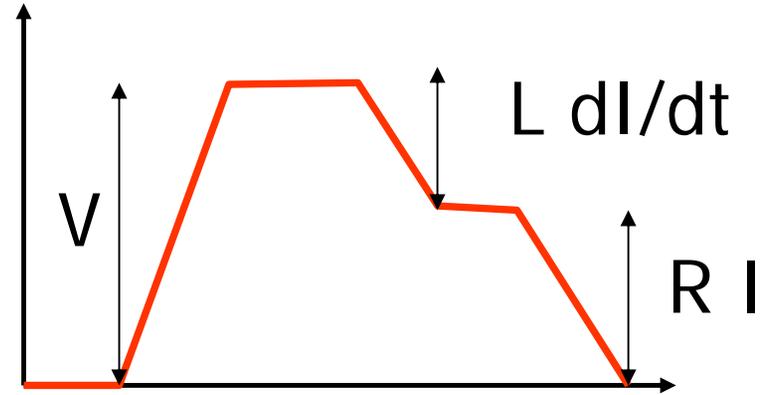


Electricity and Magnetism

- Reminder
 - RL Circuits
 - Energy storage in Inductor
- Today
 - RLC circuits
 - Resonance in RLC AC circuit


RL Circuits

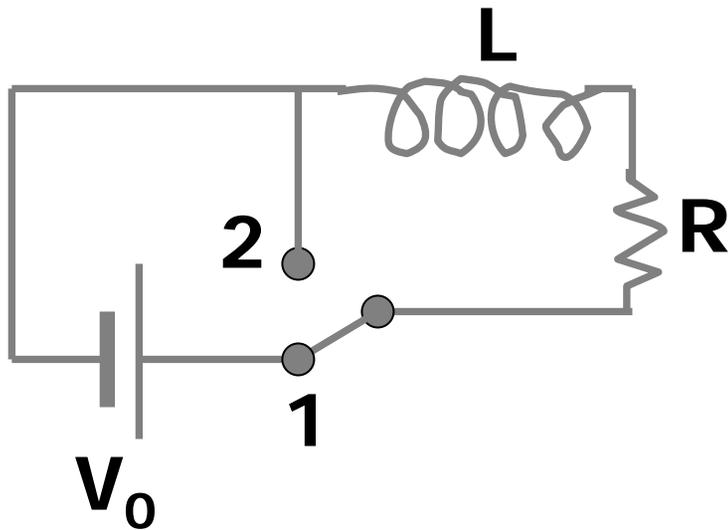


Kirchoffs Rule: $V_0 + \xi_{\text{ind}} = R I \rightarrow V_0 = L \, dI/dt + R I$

Q: What is $I(t)$?

RL Circuits

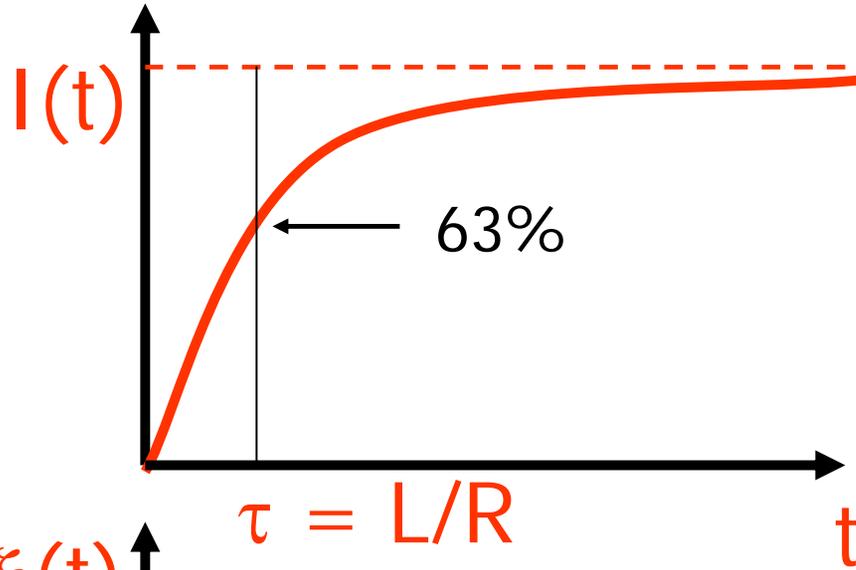

$$I(t) = V_0/R [1 - \exp(-t/\tau)]$$

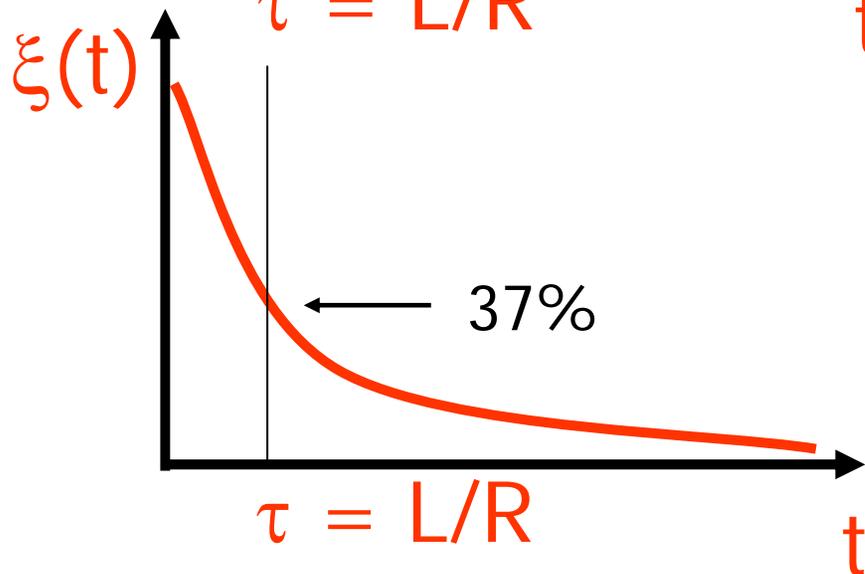


$$\xi(t) = V_0 \exp(-t/\tau)$$


RL Circuits

- Inductance leads to 'delay' in reaction of current to change of voltage V_0
- All practical circuits have some L and R
 - change in I never instantaneous

'Back EMF'

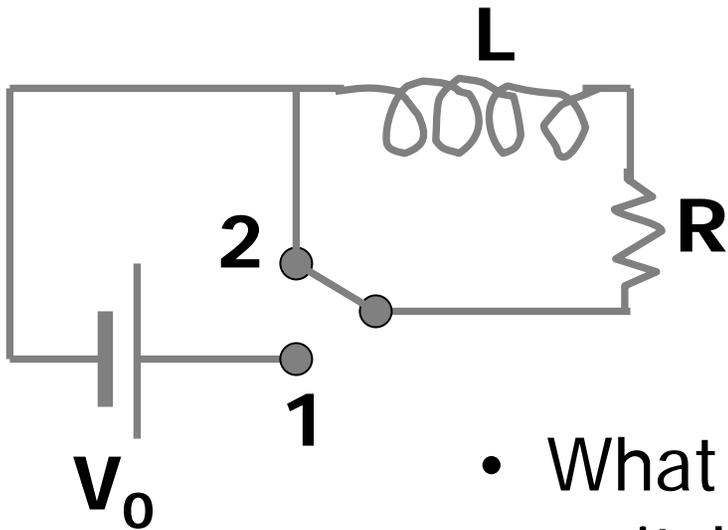

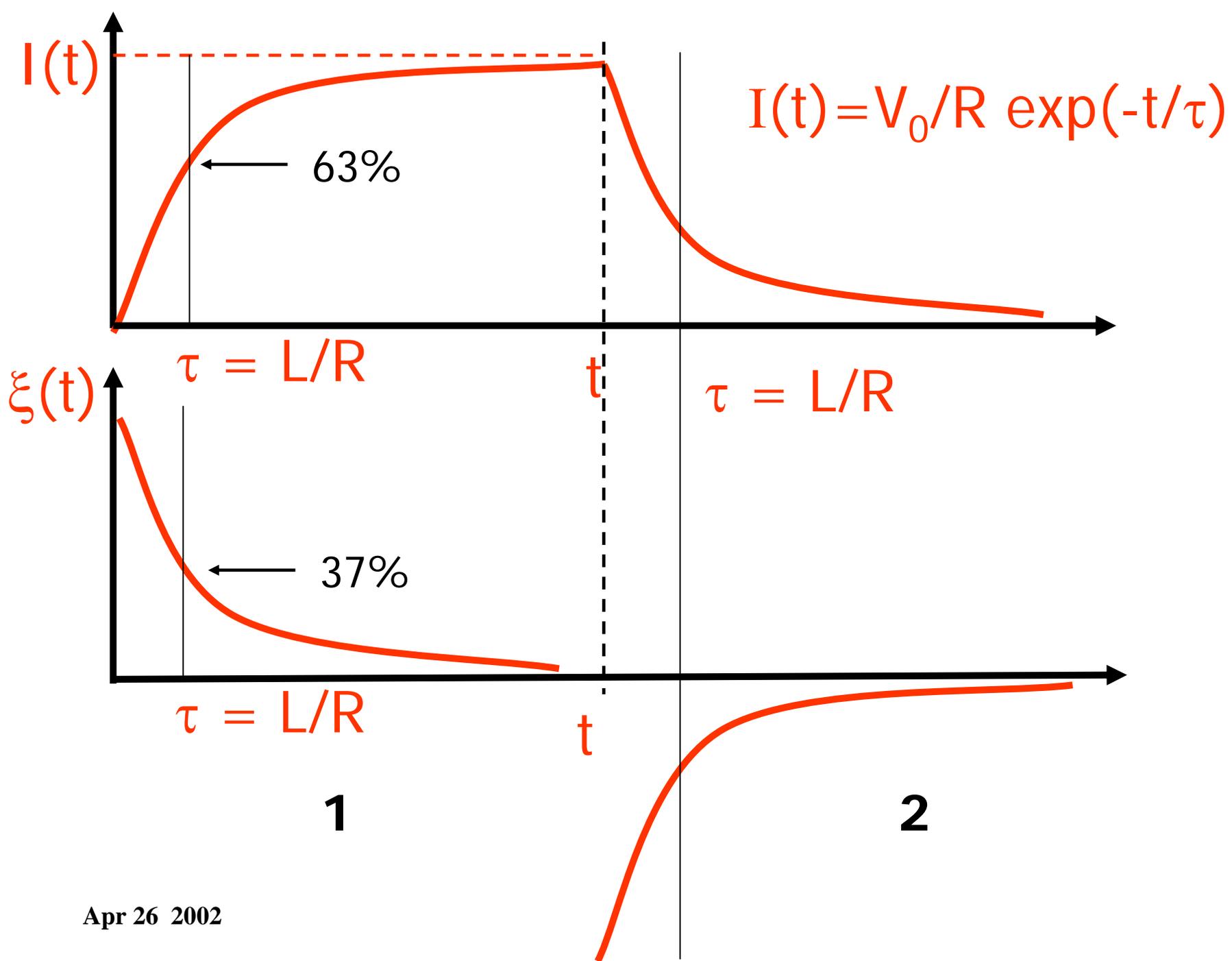
- What happens if we move switch to position 2?




RL Circuits

- L counteracts change in current both ways
 - Resists increase in I when connecting voltage source
 - Resists decrease in I when disconnecting voltage source
 - 'Back EMF'
- That's what causes spark when switching off e.g. appliance, light

In-Class Demo: Square Wave V_0

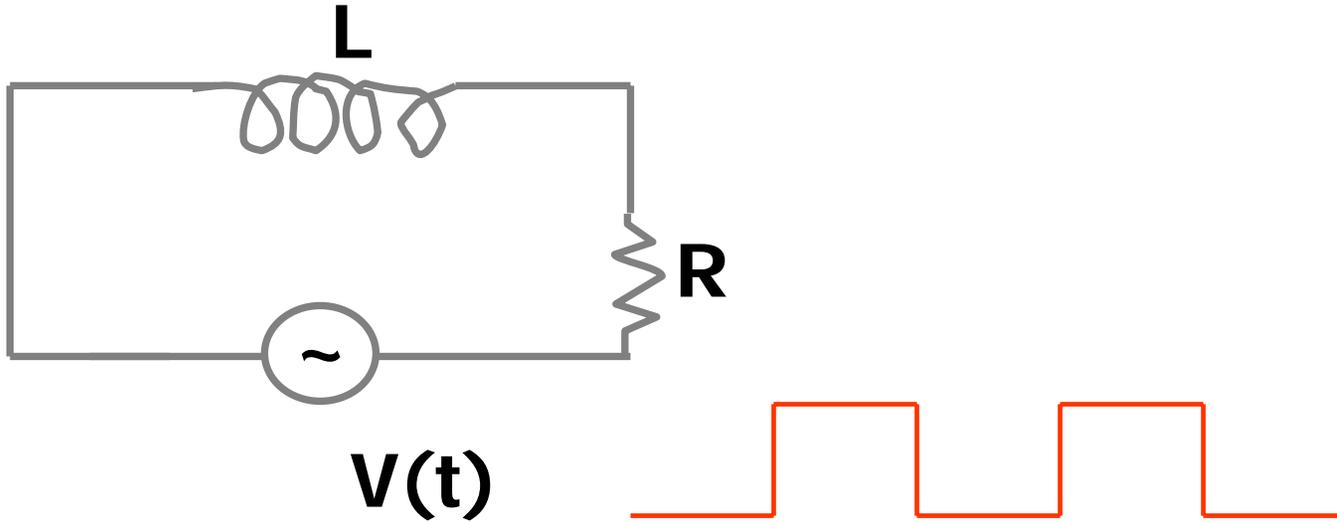

In-Class Demo

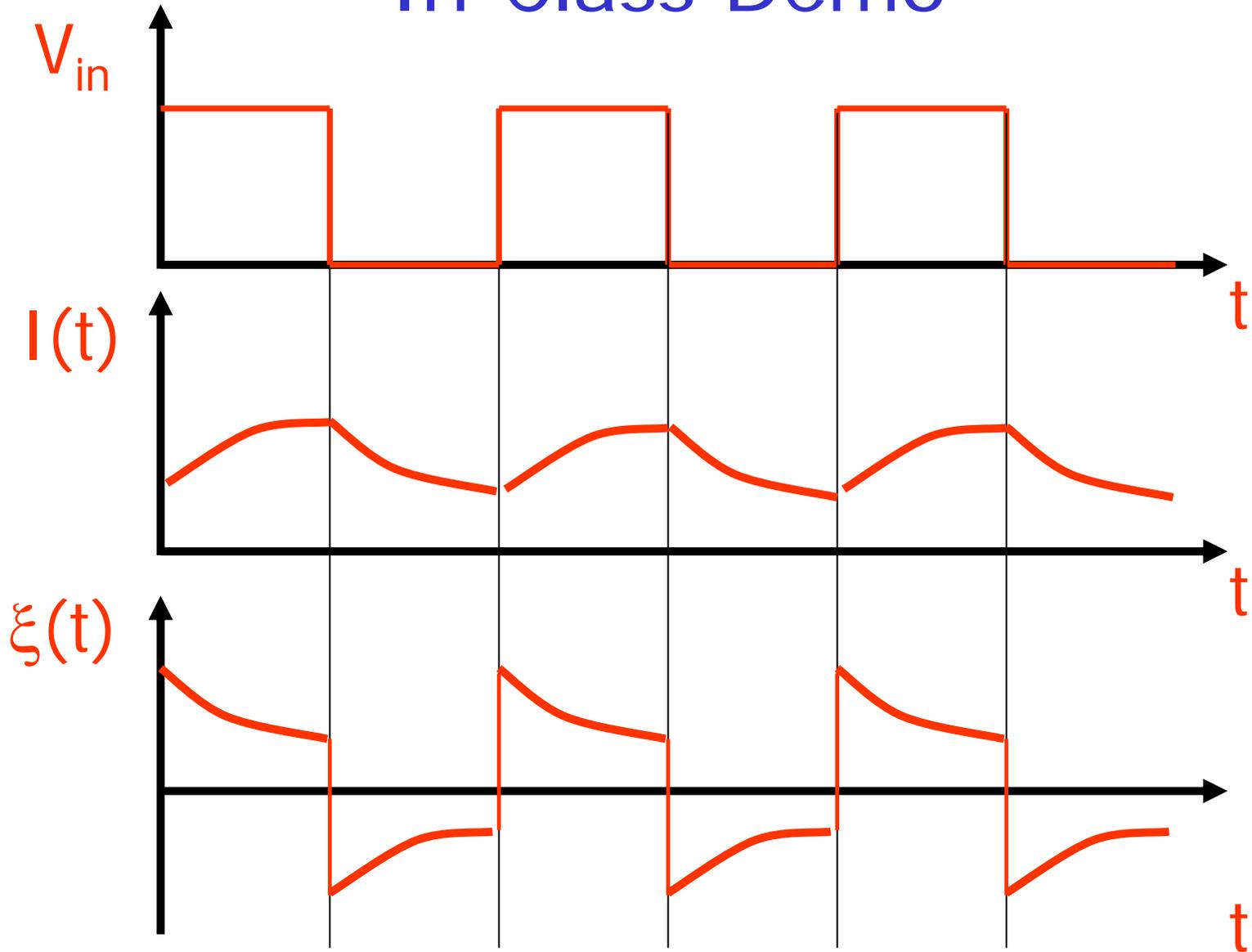

RL as low-pass filter

- Again, like RC circuits, RL circuits act as low-pass filters
- Sharp edges/high frequencies are removed
 - > In-Class Demo...
- RC circuit: Energy gets stored in C when Voltage switched on, released when Voltage switched off
- Energy storage in RL circuits?

Energy Storage in Inductor

- Energy in Inductor
 - Start with Power $P = \xi I = L \frac{dI}{dt} I = \frac{dU}{dt}$
 - > $dU = L dI I$
 - > $U = \frac{1}{2} L I^2$
- Where is the Energy stored?
 - Example: Solenoid
 - $U/\text{Volume} = \frac{1}{2} B^2/\mu_0$

RLC circuits

- Combine everything we know...
- Resonance Phenomena in RLC circuits
 - Resonance Phenomena known from mechanics (and engineering)
 - Great practical importance
 - video...

Summary of Circuit Components



$$\mathbf{V} \quad \mathbf{V(t)}$$



$$\mathbf{R} \quad \mathbf{V_R = IR}$$



$$\mathbf{L} \quad \mathbf{V_L = L \, dI/dt}$$



$$\mathbf{C} \quad \mathbf{V_C = 1/C \int I \, dt}$$


R,L,C in AC circuit

- AC circuit
 - $I(t) = I_0 \sin(\omega t)$
 - $V(t) = V_0 \sin(\omega t + \phi)$

same ω !
- Relationship between V and I can be characterized by two quantities
 - Impedance $Z = V_0/I_0$
 - Phase-shift ϕ

ϕ/ω

Z and ϕ


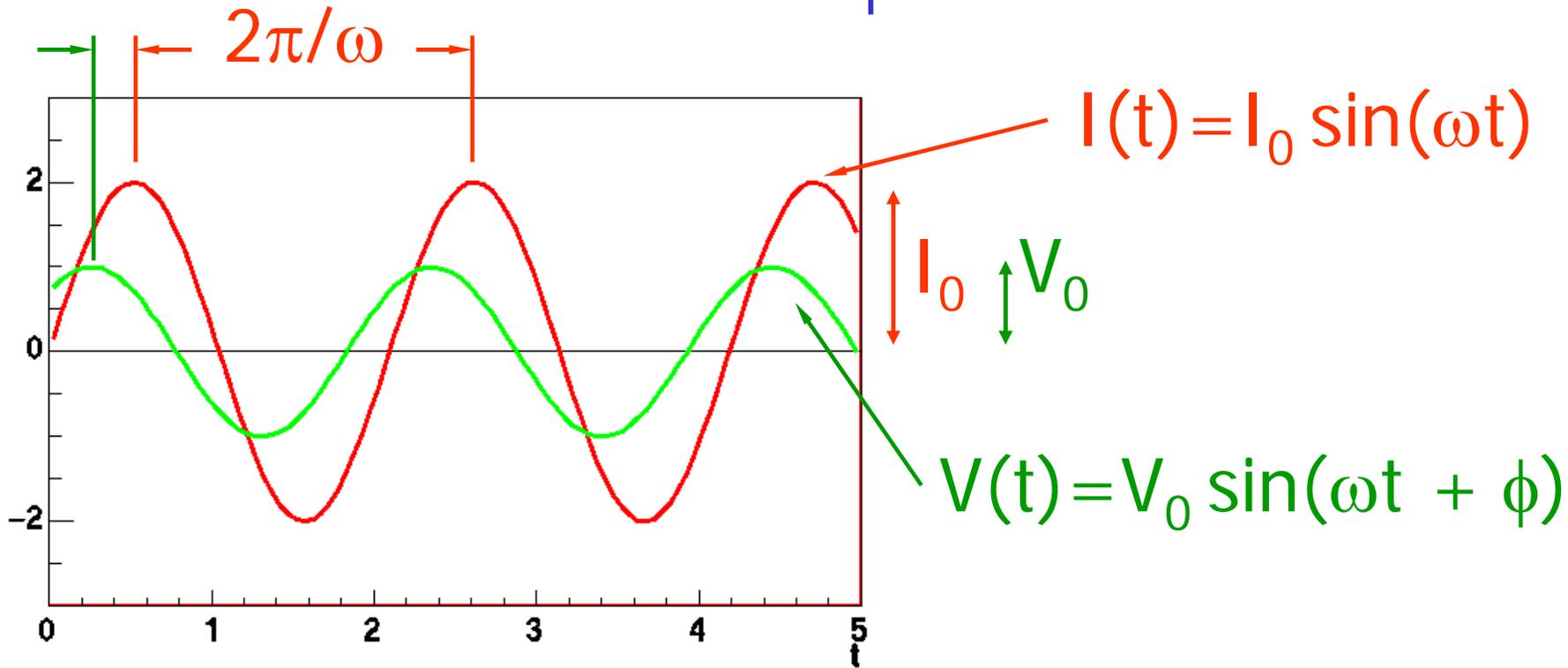


Impedance $Z = V_0/I_0$

Z and ϕ

- First look at impedance and phase-shift for circuits containing only R,C or L
- Then RLC circuit...



Z and ϕ : Capacitance C

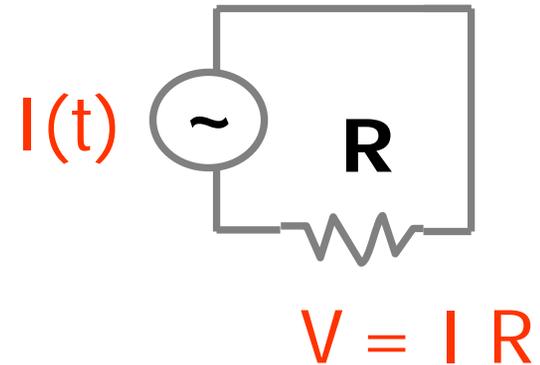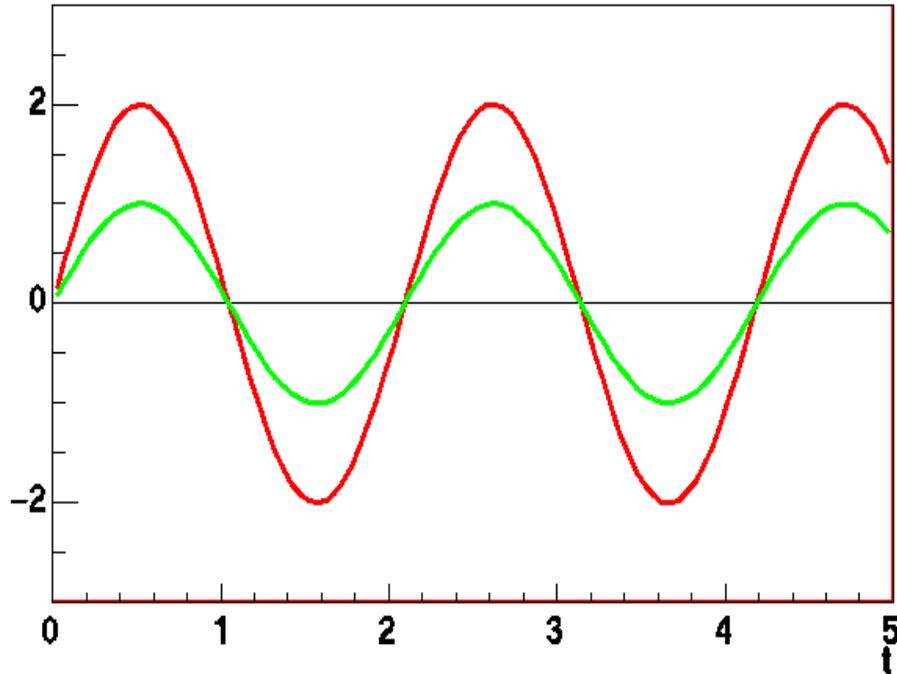

Impedance $Z = v / I = R$

Phase-shift $\phi = 0$

Z and ϕ : Capacitance C

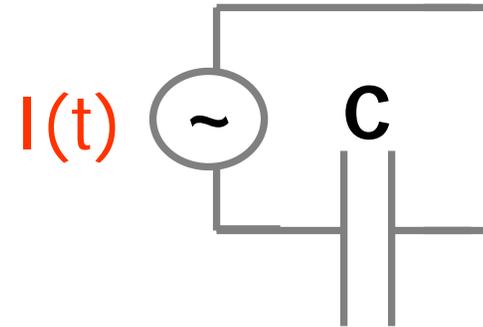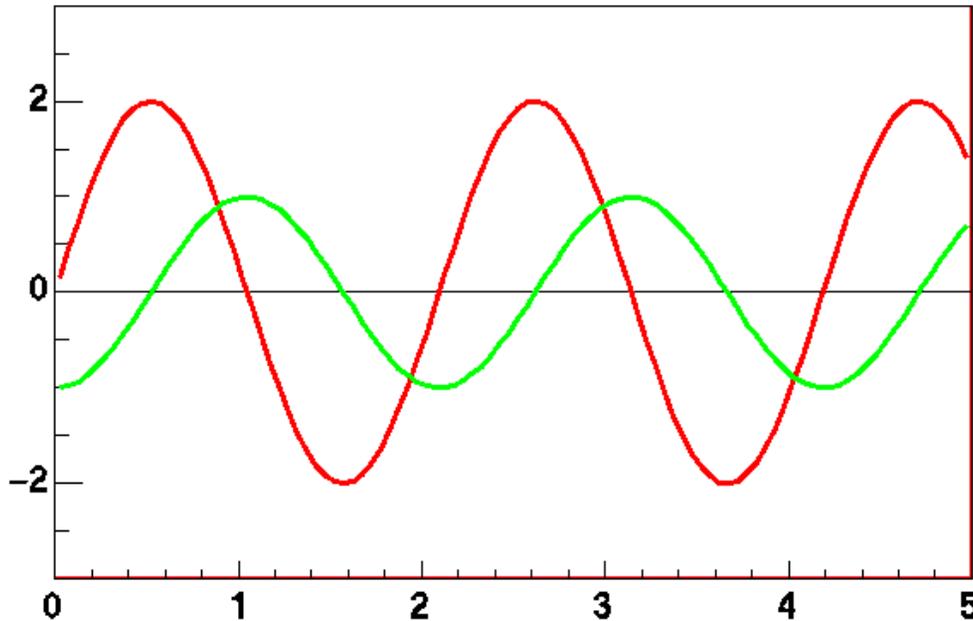



$$V = Q/C = 1/C \int I dt$$

Impedance $Z = 1/(\omega C)$

Phase-shift $\phi = -\pi/2$

V lags I by 90°

Z and ϕ : Inductance L

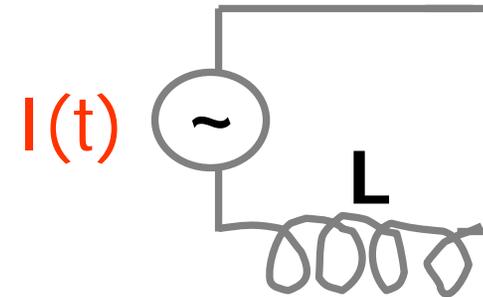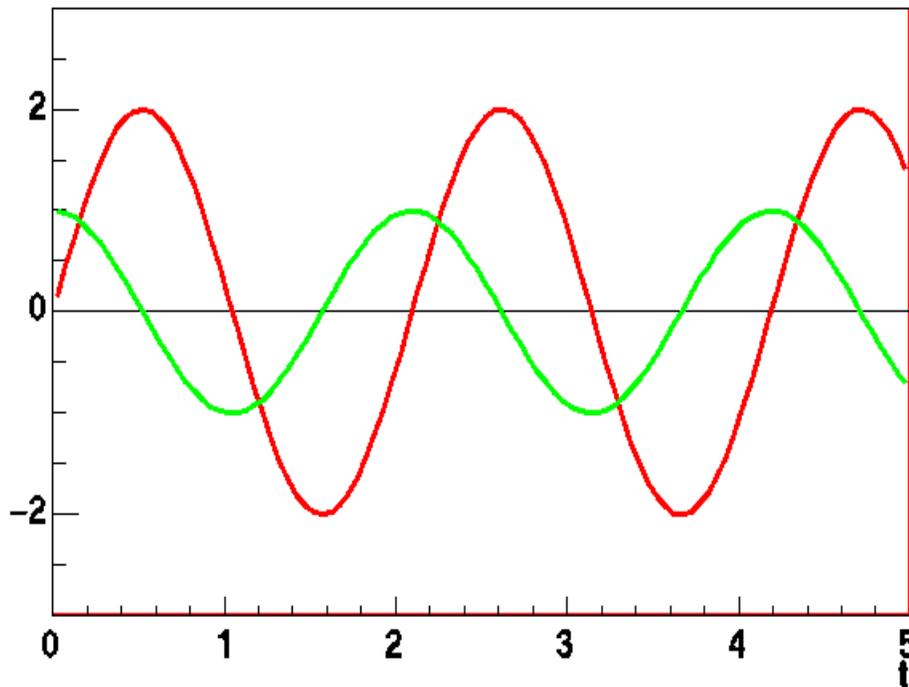


$$V = L \, dI/dt$$

Impedance $Z = \omega L$

Phase-shift $\phi = \pi/2$

I lags V by 90°

RLC circuit

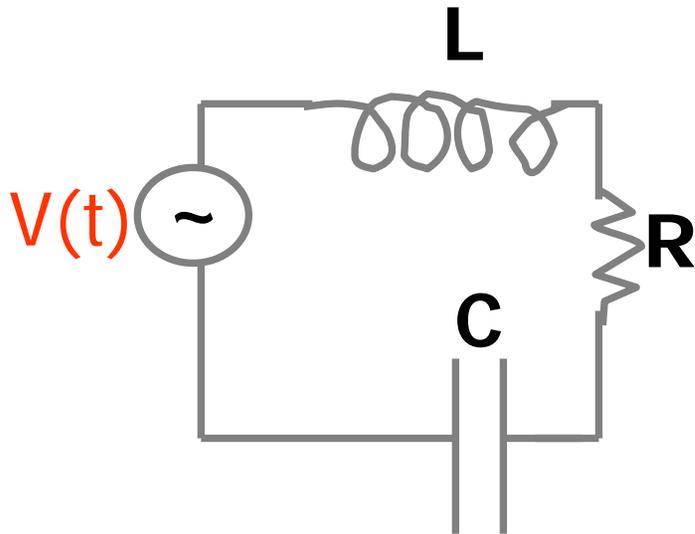


$$V - L \frac{dI}{dt} - IR - \frac{Q}{C} = 0$$

$$L \frac{d^2Q}{dt^2} = -\frac{1}{C} Q - R \frac{dQ}{dt} + V$$

2nd order differential equation

RLC circuit

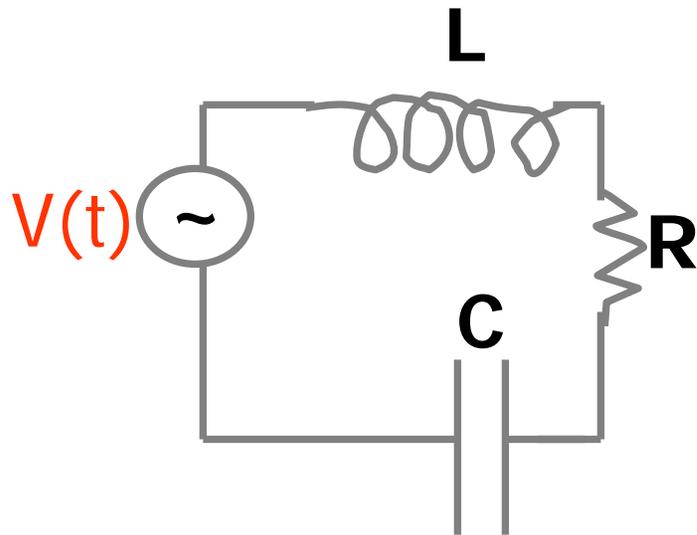

$$V - L \frac{dI}{dt} - IR - Q/C = 0$$

$$L \frac{d^2Q}{dt^2} = -1/C Q - R \frac{dQ}{dt} + V$$



'Inertia'


'Spring'



'Drag'


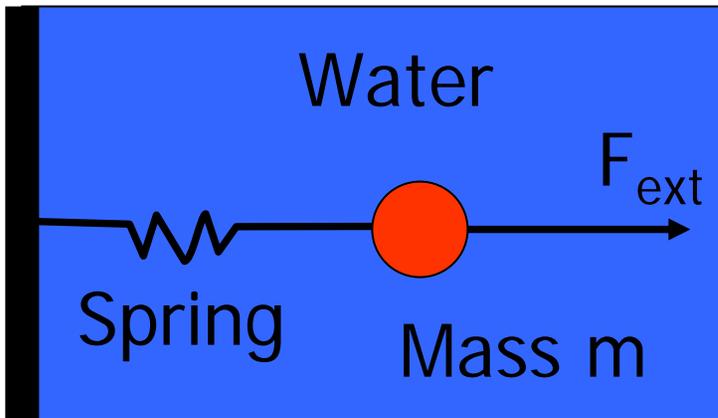
$$m \frac{d^2x}{dt^2} = -k x - f \frac{dx}{dt} + F_{\text{ext}}$$



RLC circuit

- Solve $L \frac{d^2Q}{dt^2} = -\frac{1}{C} Q - R \frac{dQ}{dt} + V$
 - for AC circuit: $V = V_0 \sin(\omega t)$, $I = I_0 \sin(\omega t - \phi)$
- If $I = I_0 \sin(\omega t - \phi)$ then
 - $Q(t) = -I_0 / \omega \cos(\omega t - \phi)$
 - $dQ/dt = I_0 \sin(\omega t - \phi)$
 - $d^2Q/dt^2 = I_0 \omega \cos(\omega t - \phi)$

RLC circuit

$$V_0 \sin(\omega t) = I_0 \{ [\omega L - 1/(\omega C)] \cos(\omega t - \phi) + R \sin(\omega t - \phi) \}$$

Solution (requires two tricks):


$$I_0 = V_0 / ([\omega L - 1/(\omega C)]^2 + R^2)^{1/2} = V_0 / Z$$

$$\tan(\phi) = [\omega L - 1/(\omega C)] / R$$

-> For $\omega L = 1/(\omega C)$, Z is minimal and $\phi = 0$

i.e. $\omega = 1/(LC)^{1/2}$ Resonance Frequency

Resonance

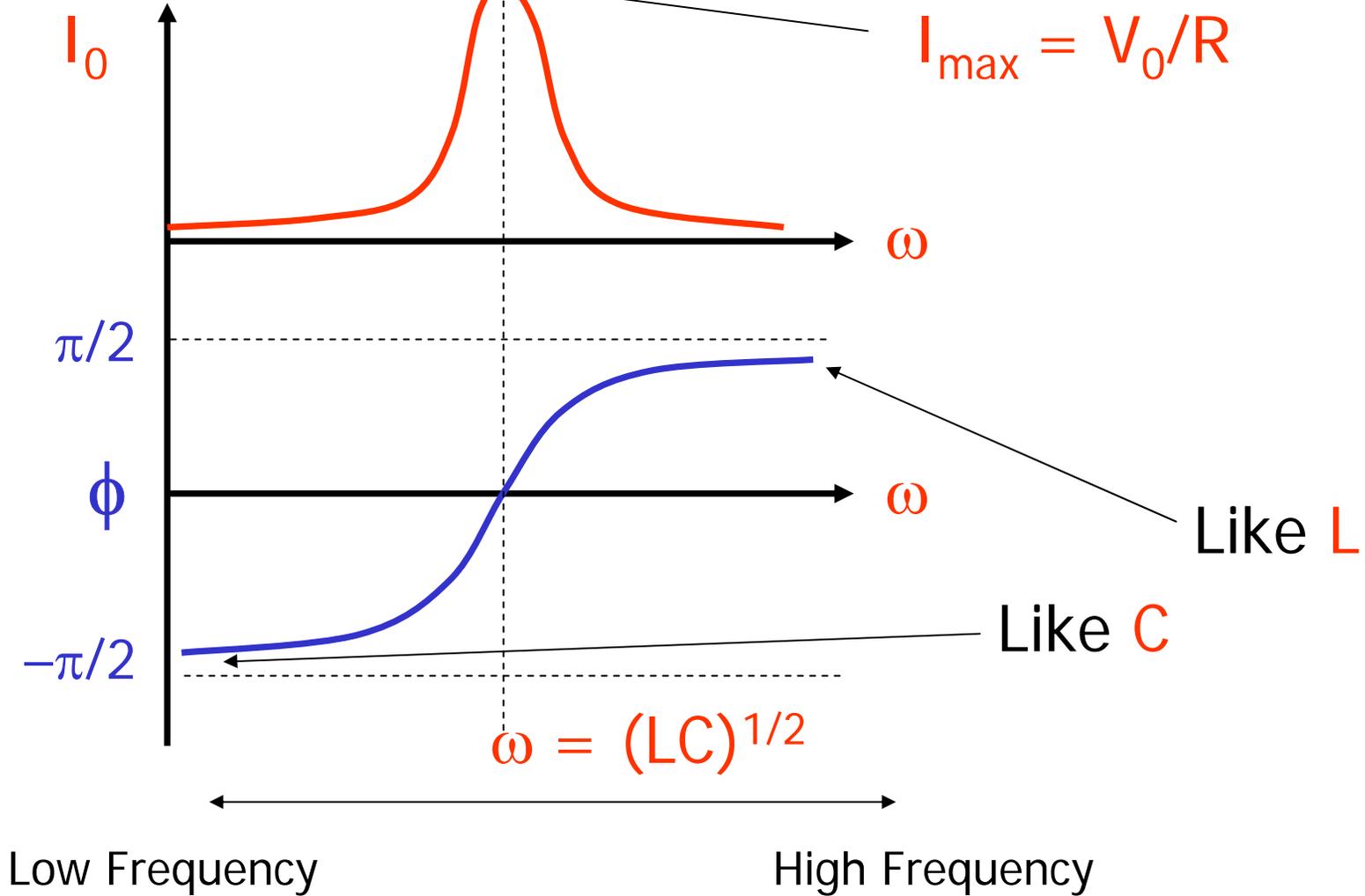

In-Class Demo (on scope)

