

Electricity and Magnetism

- Reminder
 - RLC Circuits
 - Resonance
- Today
 - LC circuits / Oscillations
 - Displacement current
 - Maxwell's equations


AC Circuit

- AC circuit
 - $I(t) = I_0 \sin(\omega t)$
 - $V(t) = V_0 \sin(\omega t + \phi)$

same ω !
- Relationship between V and I can be characterized by two quantities
 - Impedance $Z = V_0/I_0$
 - Phase-shift ϕ

ϕ/ω


AC Circuit

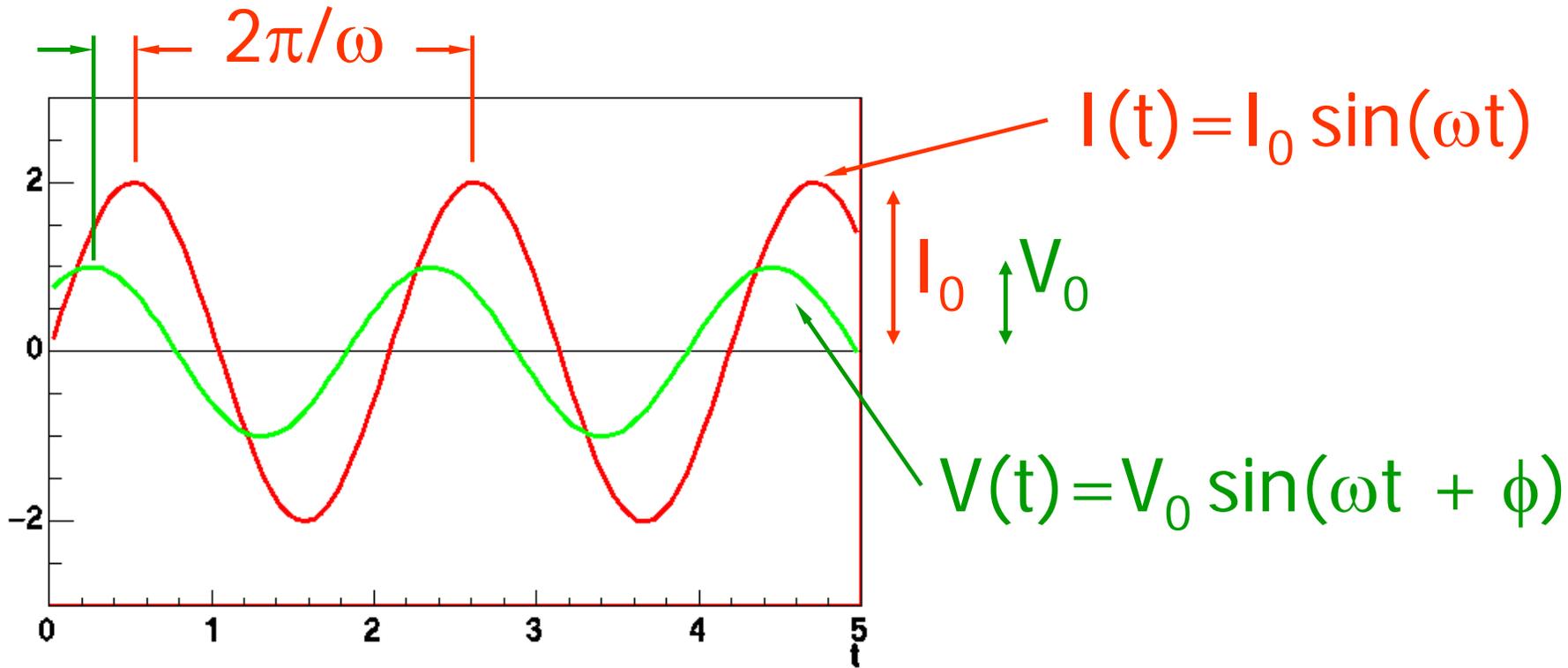

Impedance $Z = V_0/I_0$

Phase-shift ϕ

First: Look at the components

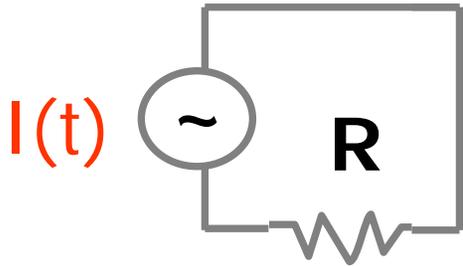


$$V = I R$$

$$Z = R$$

$$\phi = 0$$

V and I in phase

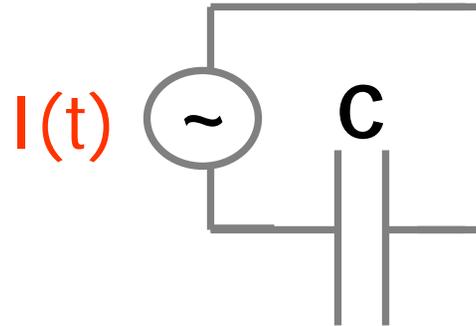


$$V = Q/C = 1/C \int I dt$$

$$Z = 1/(\omega C)$$

$$\phi = -\pi/2$$

V lags I by 90°

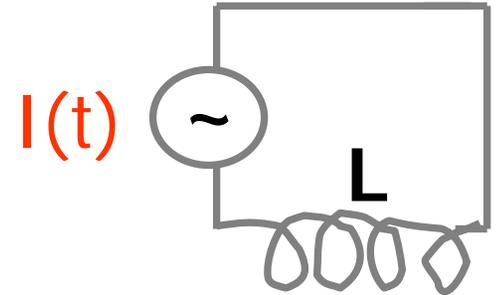


$$V = L dI/dt$$

$$Z = \omega L$$

$$\phi = \pi/2$$

I lags V by 90°

RLC Circuit

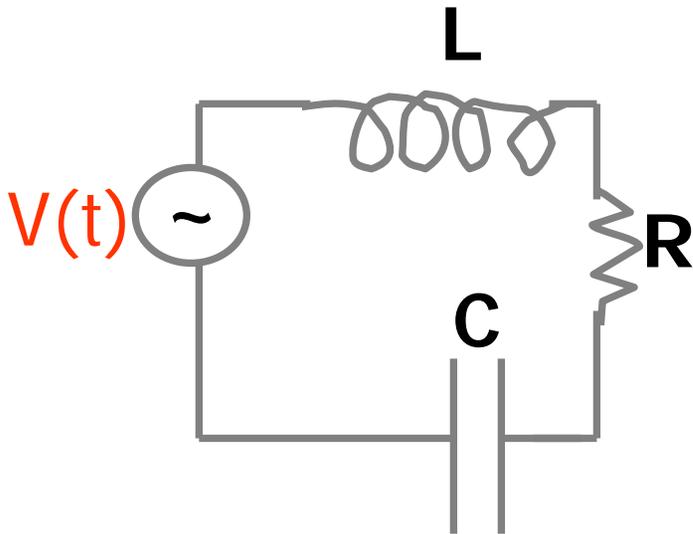

$$V - L \frac{dI}{dt} - IR - Q/C = 0$$


$$L \frac{d^2Q}{dt^2} = -1/C Q - R \frac{dQ}{dt} + V$$

'Inertia'

'Spring'

'Drag'
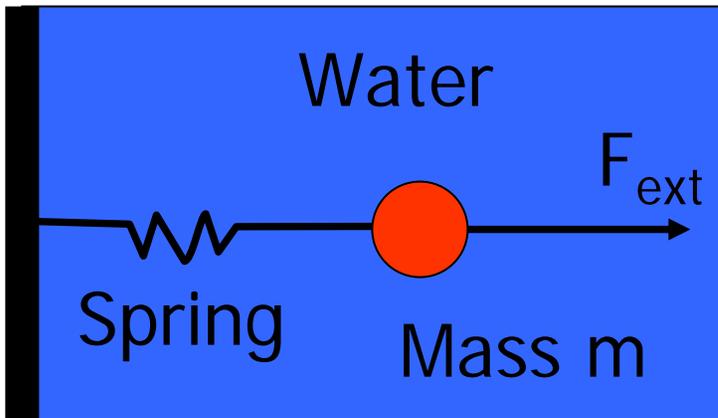
$$m \frac{d^2x}{dt^2} = -k x - f \frac{dx}{dt} + F_{\text{ext}}$$



RLC Circuit

$$V_0 \sin(\omega t) = I_0 \{ [\omega L - 1/(\omega C)] \cos(\omega t - \phi) + R \sin(\omega t - \phi) \}$$

Solution (requires two tricks):


$$I_0 = V_0 / ([\omega L - 1/(\omega C)]^2 + R^2)^{1/2} = V_0 / Z$$

$$\tan(\phi) = [\omega L - 1/(\omega C)] / R$$


-> For $\omega L = 1/(\omega C)$, Z is minimal and $\phi = 0$

i.e. $\omega_0 = 1/(LC)^{1/2}$ Resonance Frequency

In-Class Demo (on scope)

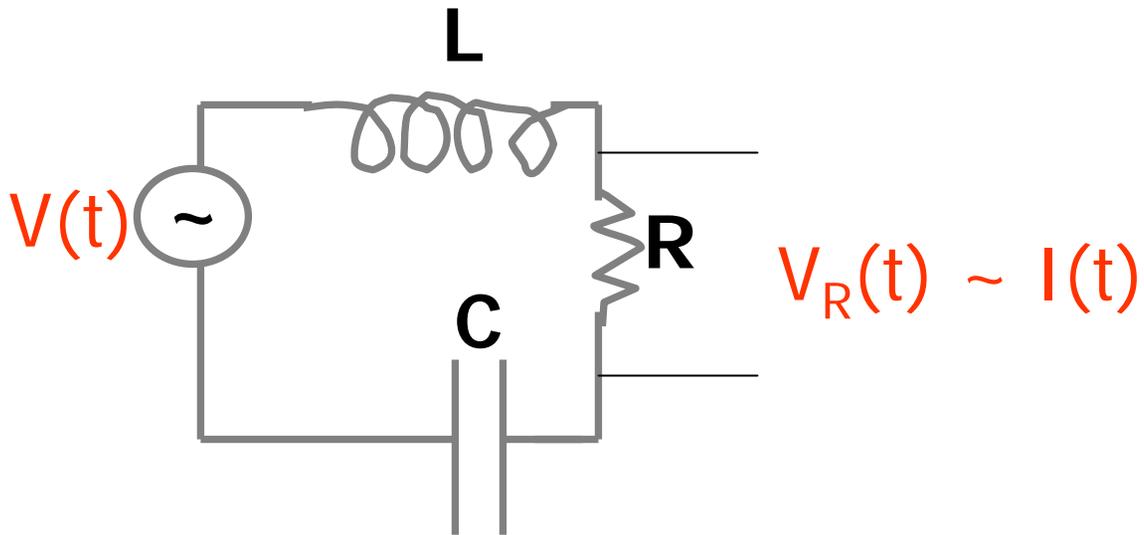

Resonance

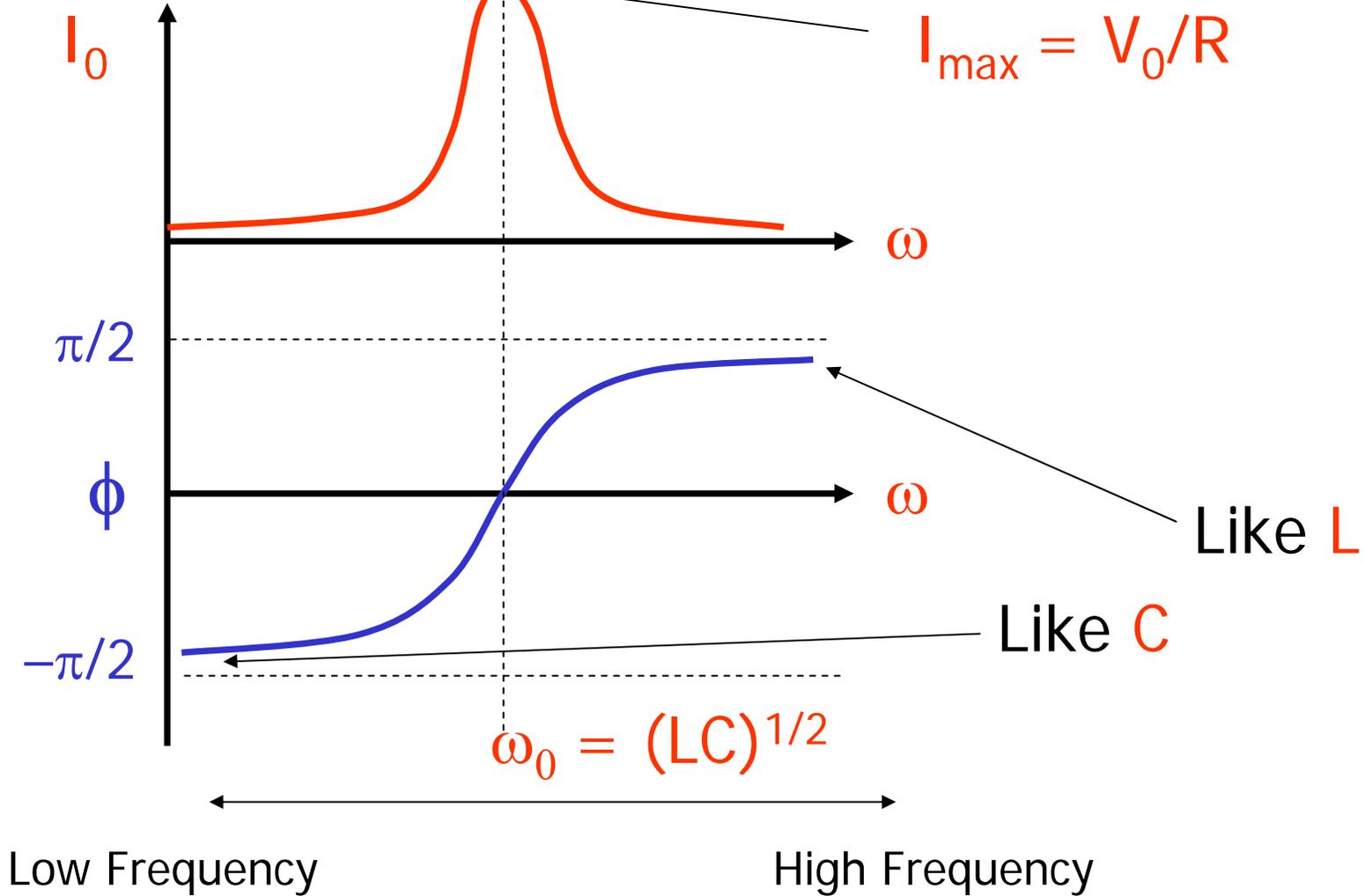


Resonance

- Practical importance
 - ‘Tuning’ a radio or TV means adjusting the resonance frequency of a circuit to match the frequency of the carrier signal

LC Circuit

- What happens if we open switch?

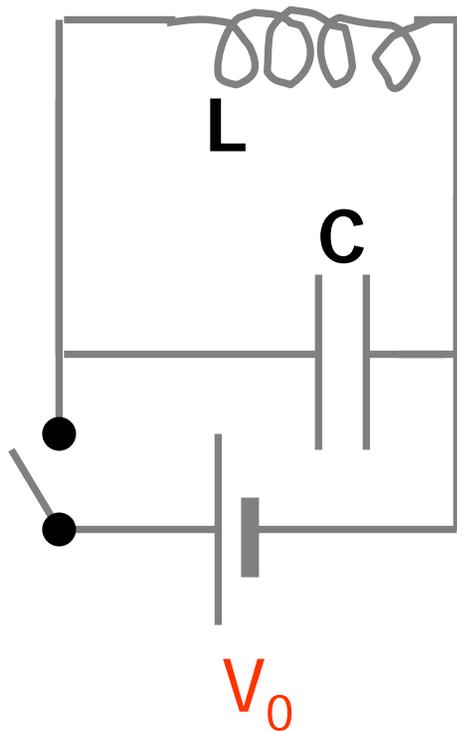

$$-L \frac{dI}{dt} - Q/C = 0$$


$$L \frac{d^2Q}{dt^2} + Q/C = 0$$



$$\frac{d^2x}{dt^2} + \omega_0^2 x = 0$$


Harmonic Oscillator!

LC Circuit

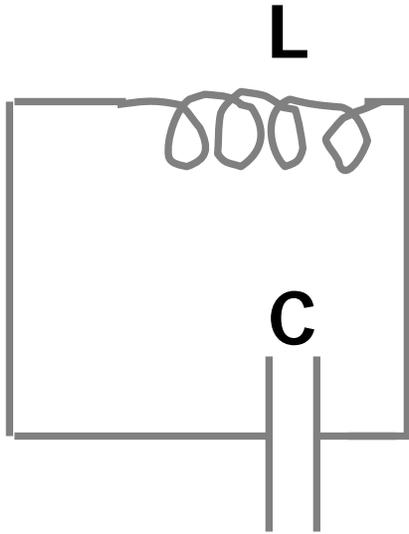

$$d^2Q/dt^2 + 1/(LC) Q = 0$$


$$\omega_0^2 = 1/(LC)$$

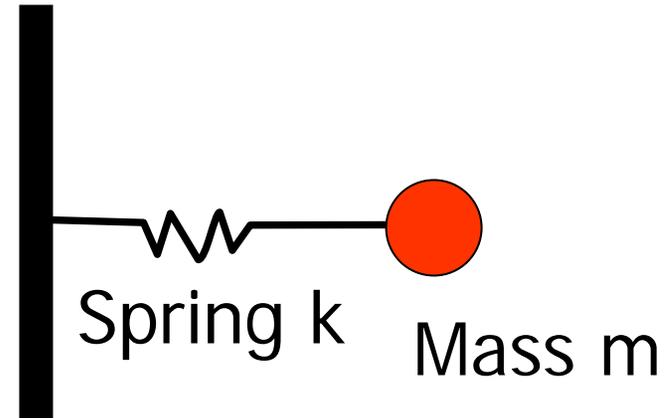

$$d^2x/dt^2 + k/m x = 0$$

$$\omega_0^2 = k/m$$

LC Circuit

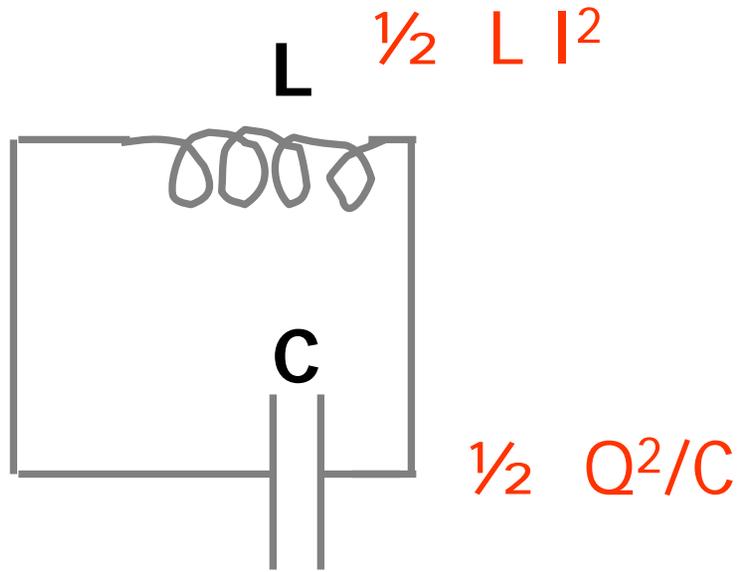


Energy in E-Field



Oscillation

Energy in B-Field

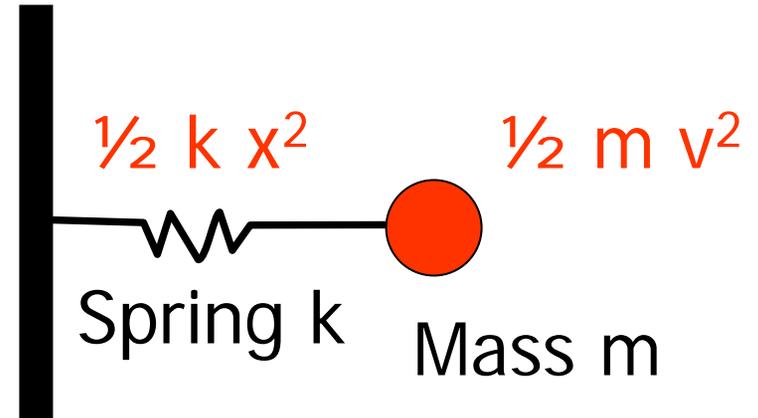

Potential Energy



Oscillation

Kinetic Energy

Electromagnetic Oscillations

- In an LC circuit, we see oscillations:

Energy in E-Field



Energy in B-Field

- Q: Can we get oscillations without circuit?
- A: Yes!
 - **Electromagnetic Waves**

Maxwell's Equations (almost)

$$\oint_{A_{closed}} \vec{E} \cdot d\vec{A} = \frac{Q_{encl}}{\epsilon_0}$$

Charges are the source of
Electric Flux through close surface

$$\xi = \oint_{L_{closed}} \vec{E} \cdot d\vec{l} = -\frac{d\Phi_B}{dt}$$

Changing magnetic field creates
an electric field

$$\oint_{A_{closed}} \vec{B} \cdot d\vec{A} = 0$$



There are no magnetic monopoles

$$\oint_{L_{closed}} \vec{B} \cdot d\vec{l} = \mu_0 I_{encl}$$

Moving charges create magnetic field

- Connection between electric and magnetic phenomena
- But not symmetric
- -> James Clerk Maxwell (~1860)

The missing piece

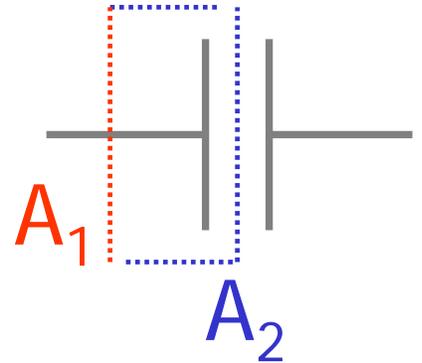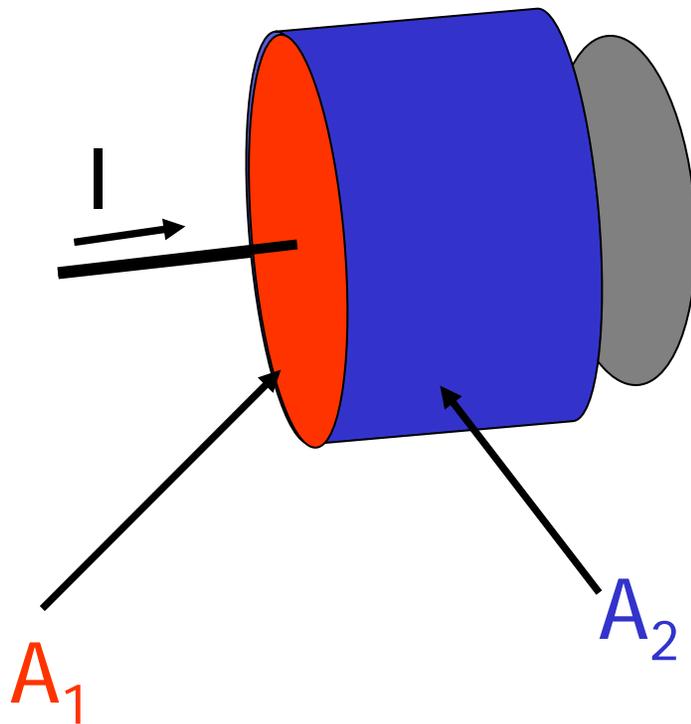


$$\oint_{L_{\text{closed}}} \vec{B} \cdot d\vec{l} = \mu_0 \int_{A_1} \vec{J}_1 d\vec{A}$$

$$\oint_{L_{\text{closed}}} \vec{B} \cdot d\vec{l} = \mu_0 \int_{A_2} \vec{J}_2 d\vec{A} \quad \swarrow = 0!$$

Displacement Current

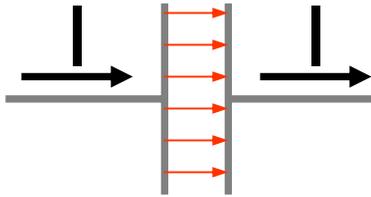- Ampere's Law broken – How can we fix it?



$$Q = C V$$

Displacement Current $I_D = \epsilon_0 d\Phi_E/dt$

Maxwell's Equations

$$\oint_{A_{\text{closed}}} \vec{E} \cdot d\vec{A} = \frac{Q_{\text{encl}}}{\epsilon_0}$$

$$\oint_{L_{\text{closed}}} \vec{E} \cdot d\vec{l} = -\frac{d\Phi_B}{dt}$$

$$\oint_{A_{\text{closed}}} \vec{B} \cdot d\vec{A} = 0$$

$$\oint_{L_{\text{closed}}} \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{encl}} + \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$$

- Symmetry between E and B
 - although there are no magnetic monopoles
- Basis for radio, TV, electric motors, generators, electric power transmission, electric circuits etc

Maxwell's Equations

$$\oint_{A_{\text{closed}}} \vec{E} \cdot d\vec{A} = \frac{Q_{\text{encl}}}{\epsilon_0}$$

$$\oint_{L_{\text{closed}}} \vec{E} \cdot d\vec{l} = -\frac{d\Phi_B}{dt}$$

$$\oint_{A_{\text{closed}}} \vec{B} \cdot d\vec{A} = 0$$

$$\oint_{L_{\text{closed}}} \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{encl}} + \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$$

1/c²

- M.E.'s *predict* electromagnetic waves, moving with speed of light
- Major triumph of science

Maxwell's Equations

$$\oint_{A_{\text{closed}}} \vec{E} \cdot d\vec{A} = \frac{Q_{\text{encl}}}{\epsilon_0}$$

$$\oint_{L_{\text{closed}}} \vec{E} \cdot d\vec{l} = -\frac{d\Phi_B}{dt}$$

$$\oint_{A_{\text{closed}}} \vec{B} \cdot d\vec{A} = 0$$

$$\oint_{L_{\text{closed}}} \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{encl}} + \mu_0 \epsilon_0 \frac{d\Phi_E}{dt}$$

1/c²

- Symmetry between E and B
 - although there are no magnetic monopoles
- Basis for radio, TV, electric motors, generators, electric power transmission, electric circuits etc