

Lecture 11: Basic Josephson Junctions

Outline

1. Quantum Tunneling
2. Josephson Tunneling
3. Josephson current-phase and current-voltage relations
4. Basic Josephson Junction lumped element
5. AC Josephson Effect
6. DC voltage standard

October 18, 2005

Massachusetts Institute of Technology
6.763 2005 Lecture 11



The Nobel Prize in Physics 1973

"for their experimental discoveries regarding tunneling phenomena in semiconductors and superconductors, respectively"

"for his theoretical predictions of the properties of a supercurrent through a tunnel barrier, in particular those phenomena which are generally known as the Josephson effects"

Image removed for copyright reasons.

Please see: p.138 of Giaever's 1973

Nobel lecture: <http://nobelprize.org/physics/laureates/1973/giaever-lecture.pdf>

Images removed for copyright reasons.

Please see:

<http://www.nobel.se/physics/laureates/1973>

Leo Esaki

1/4 of the prize
Japan

IBM Thomas J. Watson Research Center
Yorktown Heights, NY, USA

b. 1925

Ivar Giaever

1/4 of the prize
USA

General Electric Company
Schenectady, NY, USA

b. 1929
(in Bergen, Norway)

Brian David Josephson

1/2 of the prize
United Kingdom

University of Cambridge
Cambridge, United Kingdom

b. 1940

<http://www.nobel.se/physics/laureates>

Massachusetts Institute of Technology

6.763 2005 Lecture 11



Tunneling between a normal metal and another normal metal or a superconductor

Image removed for copyright reasons.

Please see: p. 140 of Giaever's 1973 Nobel lecture:

<http://nobelprize.org/physics/laureates/1973/giaever-lecture.pdf>

Image removed for copyright reasons.

Please see: p. 142 of Giaever's 1973 Nobel lecture:

<http://nobelprize.org/physics/laureates/1973/giaever-lecture.pdf>



Tunneling between two superconductors

Image removed for copyright reasons.

Please see: p. 148 of Giaever's 1973 Nobel lecture:

<http://nobelprize.org/physics/laureates/1973/giaever-lecture.pdf>

Image removed for copyright reasons.



Tunneling Summary: We are only concerned with the Josephson Tunneling in a *Basic Junction*

Image removed for copyright reasons.

Please see: Figure 8.1, page 394, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
 Addison-Wesley, 1991. ISBN: 0201183234.

Image removed for copyright reasons.

Please see: Figure 8.2, page 395, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
 Addison-Wesley, 1991. ISBN: 0201183234.

Image removed for copyright reasons.

Please see: Figure 8.3, page 396, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
 Addison-Wesley, 1991. ISBN: 0201183234.



In the superconducting electrodes:

The Supercurrent Equations govern the electrodes,

$$\mathbf{J}_s(\mathbf{r}, t) = -\frac{1}{\Lambda} \left(\mathbf{A}(\mathbf{r}, t) + \frac{\Phi_o}{2\pi} \nabla\theta(\mathbf{r}, t) \right)$$

Image removed for copyright reasons.
 Please see: Figure 8.4, page 399, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
 Addison-Wesley, 1991. ISBN: 0201183234.

$$\frac{\partial}{\partial t} \theta(\mathbf{r}, t) = -\frac{1}{\hbar} \left(\frac{\Lambda \mathbf{J}_s^2}{2n^*} + q^* \phi(\mathbf{r}, t) \right)$$

Even in the absence of E&M fields, a gradient of the phase can cause a current and the time change of that phase can cause a voltage. For example, for a constant current \mathbf{J}_o , at the boundaries we find

$$\mathbf{J}_s(\pm a, t) = -\frac{\Phi_o}{2\pi\Lambda} \nabla\theta(\pm a, t) = \mathbf{J}_o \quad \& \quad \frac{\partial}{\partial t} \theta(\pm a, t) = -\frac{1}{\hbar} \left(\frac{\Lambda \mathbf{J}_o^2}{2n^*} \right) = -\frac{\mathcal{E}_o}{\hbar}$$

So that the wavefunction in the electrode is $\Psi(\mathbf{r}, t) = \Psi(\mathbf{r}) e^{-i(\mathcal{E}_o t/\hbar)}$



In the insulator

The current must be continuous, so it must flux through the insulating barrier; a process which is not allowed classically. But quantum mechanically the superelectrons can tunnel through the insulating barrier as a supercurrent with zero voltage. This is the Josephson current.

Because the supercurrent equation does not hold in the insulating region, the full macroscopic wave equation must be used to find Ψ in the insulating region, with the boundary conditions given by the wavefunction at the electrodes.

Image removed for copyright reasons.
Please see: Figure 8.4, page 399, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
Addison-Wesley, 1991. ISBN: 0201183234.

$$i\hbar \frac{\partial}{\partial t} \Psi(\mathbf{r}, t) = \frac{1}{2m^*} \left(\frac{\hbar}{i} \nabla - q^* \mathbf{A}(\mathbf{r}, t) \right)^2 \Psi(\mathbf{r}, t) + q^* \phi(\mathbf{r}, t) \Psi(\mathbf{r}, t) + \underbrace{V(x)}_{\text{Tunneling Potential Barrier}} \Psi(\mathbf{r}, t)$$

Tunneling Potential Barrier

Massachusetts Institute of Technology
6.763 2005 Lecture 11



Tunneling through the Barrier

The energy of the superelectron is less than the barrier height, so that no classical particles flow.

$$-\frac{\hbar^2}{2m^*} \nabla^2 \Psi(\mathbf{r}) = \underbrace{(\epsilon_0 - V_0)}_{\text{constant}} \Psi(\mathbf{r}) \quad \text{for } |x| \leq a$$

Image removed for copyright reasons.
Please see: Figure 8.5, page 400, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
Addison-Wesley, 1991. ISBN: 0201183234.

Therefore, in the insulating region

$$\Psi(x) = C_1 \cosh x/\zeta + C_2 \sinh x/\zeta$$

$$\text{Where } \zeta \equiv \sqrt{\frac{\hbar^2}{2m^*(V_0 - \epsilon_0)}} \quad \text{so that}$$

$$J_s = \frac{2q^*}{m^*} \text{Re} \left\{ \Psi^* \frac{\hbar}{i} \nabla \Psi \right\} = \frac{q^* \hbar}{m^* \zeta} \text{Im} \{ C_1^* C_2 \}$$

Massachusetts Institute of Technology
6.763 2005 Lecture 11



Tunneling through the Barrier

$$J_S = \frac{2q^*}{m^*} \operatorname{Re} \left\{ \Psi^* \frac{\hbar}{i} \nabla \Psi \right\} = \frac{q^* \hbar}{m^* \zeta} \operatorname{Im} \{ C_1^* C_2 \}$$

At the boundaries.

$$\Psi(-a) = \sqrt{n_1^*} e^{i\theta_1} \quad \& \quad \Psi(+a) = \sqrt{n_2^*} e^{i\theta_2}$$

Image removed for copyright reasons.
Please see: Figure 8.5, page 400, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
Addison-Wesley, 1991. ISBN: 0201183234.

So that

$$C_1 = \frac{\sqrt{n_1^*} e^{i\theta_1} + \sqrt{n_2^*} e^{i\theta_2}}{2 \cosh(a/\zeta)} \quad \& \quad C_2 = -\frac{\sqrt{n_1^*} e^{i\theta_1} - \sqrt{n_2^*} e^{i\theta_2}}{2 \sinh(a/\zeta)}$$

Therefore,

$$J_S = J_C \sin(\theta_1 - \theta_2)$$

with
$$J_C = \frac{e \hbar \sqrt{n_1 n_2}}{m \zeta \sinh(2a/\zeta)}$$

Massachusetts Institute of Technology

6.763 2005 Lecture 11



Josephson Current-Phase relation

$$J_S = J_C \sin(\theta_1 - \theta_2)$$

Image removed for copyright reasons.
Please see: Figure 8.4, page 399, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
Addison-Wesley, 1991. ISBN: 0201183234.

In the presence of an electromagnetic field, the Josephson current-phase relation generalizes to

$$J_S(\mathbf{r}, t) = J_C(y, z, t) \sin \varphi(y, z, t)$$

where the *gauge-invariant phase* is defined as

$$\varphi(y, z, t) = \theta_1(y, z, t) - \theta_2(y, z, t) - \frac{2\pi}{\Phi_0} \int_1^2 \mathbf{A}(\mathbf{r}, t) \cdot d\mathbf{l}$$

Which is invariant under $\mathbf{A}' = \mathbf{A} + \nabla \chi$, $\theta' = \theta + \frac{q^*}{\hbar} \chi$, $\phi' \equiv \phi - \frac{\partial \chi}{\partial t}$

Massachusetts Institute of Technology

6.763 2005 Lecture 11



Josephson Voltage-Phase relation

The *gauge-invariant phase* is

$$\varphi(y, z, t) = \theta_1(y, z, t) - \theta_2(y, z, t) - \frac{2\pi}{\Phi_0} \int_1^2 \mathbf{A}(\mathbf{r}, t) \cdot d\mathbf{l}$$

Image removed for copyright reasons.

The rate of change of the *gauge-invariant phase* is

Please see: Figure 8.4, page 399, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
 Addison-Wesley, 1991. ISBN: 0201183234.

$$\frac{\partial \varphi}{\partial t} = \frac{\partial \theta_1}{\partial t} - \frac{\partial \theta_2}{\partial t} - \frac{2\pi}{\Phi_0} \frac{\partial}{\partial t} \int_1^2 \mathbf{A}(\mathbf{r}, t) \cdot d\mathbf{l}$$

At the boundary in the electrodes,

$$\frac{\partial}{\partial t} \theta(\mathbf{r}, t) = -\frac{1}{\hbar} \left(\frac{\Lambda J_S^2}{2n^*} + q^* \phi(\mathbf{r}, t) \right) \quad \text{so that}$$

$$\frac{\partial \varphi}{\partial t} = -\frac{1}{\hbar} \left(\frac{\Lambda}{2n^*} \underbrace{[J_S^2(-a) - J_S^2(a)]}_0 + q^* \underbrace{[\phi(-a) - \phi(a)]}_{\int_1^2 -\nabla \phi \cdot d\mathbf{l}} \right) - \frac{2\pi}{\Phi_0} \frac{\partial}{\partial t} \int_1^2 \mathbf{A}(\mathbf{r}, t) \cdot d\mathbf{l}$$

Therefore, $\frac{\partial \varphi}{\partial t} = \frac{2\pi}{\Phi_0} \int_1^2 \left(-\nabla \phi - \frac{\partial \mathbf{A}}{\partial t} \right) \cdot d\mathbf{l}$ or $\frac{\partial \varphi(y, z, t)}{\partial t} = \frac{2\pi}{\Phi_0} \int_1^2 \mathbf{E}(\mathbf{r}, t) \cdot d\mathbf{l}$

Massachusetts Institute of Technology

6.763 2005 Lecture 11



Basic Lumped Junctions

$$\mathbf{J}_S(\mathbf{r}, t) = \mathbf{J}_C(y, z, t) \sin \varphi(y, z, t)$$

$$\varphi(y, z, t) = \theta_1(y, z, t) - \theta_2(y, z, t) - \frac{2\pi}{\Phi_0} \int_1^2 \mathbf{A}(\mathbf{r}, t) \cdot d\mathbf{l}$$

Image removed for copyright reasons.

Please see: Figure 8.4, page 399, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
 Addison-Wesley, 1991. ISBN: 0201183234.

$$\frac{\partial \varphi(y, z, t)}{\partial t} = \frac{2\pi}{\Phi_0} \int_1^2 \mathbf{E}(\mathbf{r}, t) \cdot d\mathbf{l}$$

Image removed for copyright reasons.

Please see: Figure 8.6, page 406, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
 Addison-Wesley, 1991. ISBN: 0201183234.

$$\varphi(t) = \theta_1(t) - \theta_2(t) - \frac{2\pi}{\Phi_0} \int_1^2 \mathbf{A}(\mathbf{r}, t) \cdot d\mathbf{l}$$

I_c is the *critical current*

Massachusetts Institute of Technology

6.763 2005 Lecture 11



Energy in a Basic Josephson Junction

The energy W_J in the basic junction is

$$W_J = \int_0^{t_0} i v dt$$

Image removed for copyright reasons.
Please see: Figure 8.6, page 406, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
Addison-Wesley, 1991. ISBN: 0201183234.

Use the Josephson relations to write as

$$W_J = \int_0^{t_0} (I_c \sin \varphi') \left(\frac{\Phi_0}{2\pi} \frac{d\varphi'}{dt} \right) dt = \frac{\Phi_0 I_c}{2\pi} \int_0^\varphi \sin \varphi' d\varphi'$$

$$\text{Therefore, } W_J = \frac{\Phi_0 I_c}{2\pi} (1 - \cos \varphi)$$


Image removed for copyright reasons.

Please see: Figure 8.7, page 407, from Orlando, T., and K. Delin.
Foundations of Applied Superconductivity. Reading, MA:
Addison-Wesley, 1991. ISBN: 0201183234.

Massachusetts Institute of Technology
6.763 2005 Lecture 11



AC Josephson Effect

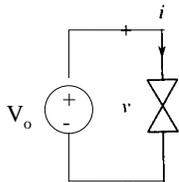

$$i = I_c \sin \varphi$$

$$v = \frac{\Phi_0}{2\pi} \frac{d\varphi}{dt}$$

The voltage source is DC with $v=V_0$, so that

$$\varphi(t) = \varphi(0) + \frac{2\pi}{\Phi_0} V_0 t$$

The resulting current is ac!

$$\begin{aligned} i &= I_c \sin \left(\frac{2\pi}{\Phi_0} V_0 t + \varphi(0) \right) \\ &= I_c \sin (2\pi f_J t + \varphi(0)) \end{aligned}$$


$$\text{The Josephson frequency is } f_J = \frac{V_0}{\Phi_0} = \frac{2e}{h} V_0 = 483.6 \times 10^{12} V_0 \text{ (Hz)}$$

A dc voltage of 10 μ V causes an oscillation frequency of about 5 GHz, a Josephson microwave oscillator. But with a typical I_c of 1 mA, this oscillator delivers a very small power of the order of 10 nW. Therefore need many synchronous oscillators.

Massachusetts Institute of Technology
6.763 2005 Lecture 11



AC and DC voltage drives

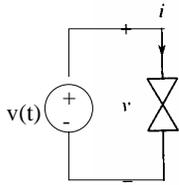

$$i = I_c \sin \varphi$$

$$v = \frac{\Phi_0}{2\pi} \frac{d\varphi}{dt}$$

$$\text{Let } v(t) = V_o + V_s \cos \omega_s t$$

Then the gauge-invariant phase is

$$\varphi(t) = \varphi(0) + \frac{2\pi}{\Phi_0} V_o t + \frac{2\pi V_s}{\Phi_0 \omega_s} \sin \omega_s t$$

The current is FM-like: $i = I_c \sin \left(\varphi(0) + \frac{2\pi}{\Phi_0} V_o t + \frac{2\pi V_s}{\Phi_0 \omega_s} \sin \omega_s t \right)$

Use the Fourier-Bessel series to express the current as a Fourier series


$$i = I_c \sum_{n=-\infty}^{\infty} (-1)^n \left[J_n \left(\frac{2\pi V_s}{\Phi_0 \omega_s} \right) \right] \sin [(2\pi f_J - n\omega_s)t + \varphi(0)]$$

A dc current will occur when $2\pi f_J = n \omega_s$, that is, $V_o = n \left(\frac{\Phi_0}{2\pi} \right) \omega_s$

Massachusetts Institute of Technology
6.763 2005 Lecture 11



Principle of the DC Voltage Standard

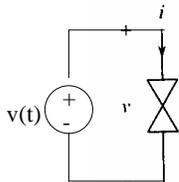

$$i = I_c \sin \varphi$$

$$v = \frac{\Phi_0}{2\pi} \frac{d\varphi}{dt}$$

$$V_o = n \left(\frac{\Phi_0}{2\pi} \right) \omega_s$$


An ac voltage of 1 GHz applied across the junction will give a dc current, at $V_o = 0$ and at dc voltages of integral multiples of $2\mu\text{V}$.

The principle of the dc Volt: Put 5000 Josephson junctions in series, and apply a fixed frequency, which can be done very accurately, and measure the interval of the resulting dc voltages that occur at precise voltage intervals.

Massachusetts Institute of Technology
6.763 2005 Lecture 11



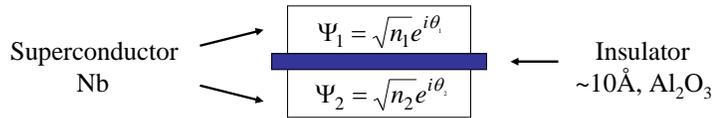Summary: Basic Josephson Junction ($I < I_c$)




- Josephson relations:
- Behaves as a nonlinear inductor:

$$I = I_c \sin \varphi$$

$$V = \frac{\Phi_0}{2\pi} \frac{d\varphi}{dt}$$

$$\varphi = \theta_2 - \theta_1$$
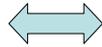
$$- \frac{2\pi}{\Phi_0} \int \vec{A}(r, t) \cdot d\vec{l}$$



$$V = L_J \frac{dI}{dt},$$

where $L_J = \frac{\Phi_0}{2\pi I_c \cos \varphi}$

Φ_0 = flux quantum

483.6 GHz / mV

Massachusetts Institute of Technology

6.763 2005 Lecture 11

